

4D Tracking – ASIC


11/17/2021

Bojan Markovic

Towards 4D tracking and calorimetry in deep submicron technologies

- Research 4D (space and time) architectural front-end solutions in 28nm and 22nm FinFET for next generation trackers and calorimeters
- Enables higher spatial resolution and sub-bunch timing resolution, while sustain higher radiation doses
- Critical for resolving pile-ups in future high luminosity colliders operating in extreme radiation environments

High Luminosity implications

 

Highly segmented hybrid pixel detectors with precision timing (28nm)
+
Fast sensors (LGADs)



4D tracking and calorimetry


- PI B. Markovic (TID), Co-PI A. Pena Perez (TID)
- Co-Is: Kenney (TID), A. Schwartzman (FPD), Su Dong (FPD), C. Vernieri (FPD)
- Resources from TID-ID IC & Sensors
- **5 months FTE (\$200k)**
- **M&S (\$40k)**
- Long term R&D (scope defined for Q2-Q4 2022)

- Continue engaging with the broader community collaboration around 28nm and 22nm (CERN, LBNL, FNAL)
- Establish 28nm and 22nm FinFET design flows (mostly done)
- Continue the design and layout test structures for technology characterization
- Continue the design and layout prototype of pixel timing blocks and ADCs
- Fab a first 28nm prototype (opportunity for joint fab run with LBNL and FNAL)


Propagation Delay: Inverter

□ Inverter:

• Schematic:

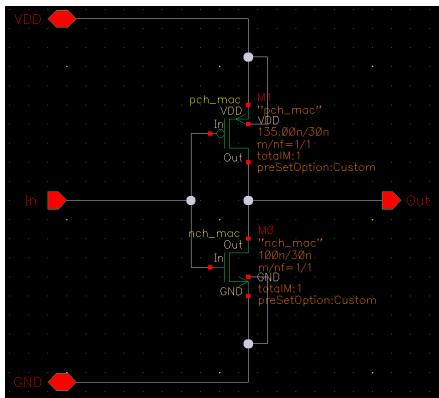


• Layout:

 

Propagation Delay

× ~2

 


$t_{pRCX} \sim 12 - 25ps$


*A Buffer is made of 2 inverters thus the corresponding delay would be 24-50ps

DCVSL Delay Cell

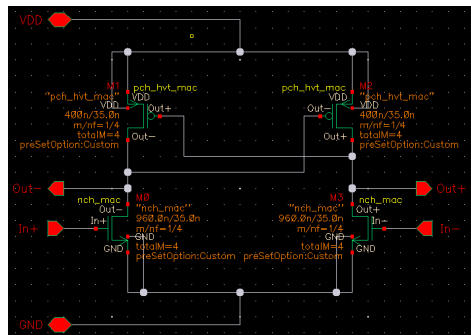
□ Differential Cascode Voltage Switch Logic (DCVSL) Implementation:



• Layout 1:

 

• Layout 2:



 


Layout 1:
× ~3.5

Layout 2:
× ~2.5


$t_{pRCX} \sim 40 - 70ps$

$t_{pRCX} \sim 30 - 50ps$

   


Voltage-Controlled Delay Cells

Current-Starved Delay Cell:

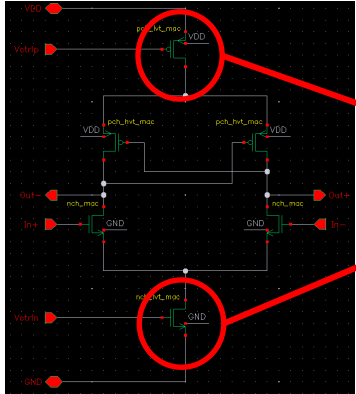

Delay controlled thro current


Shunt-Capacitor Delay Cell:

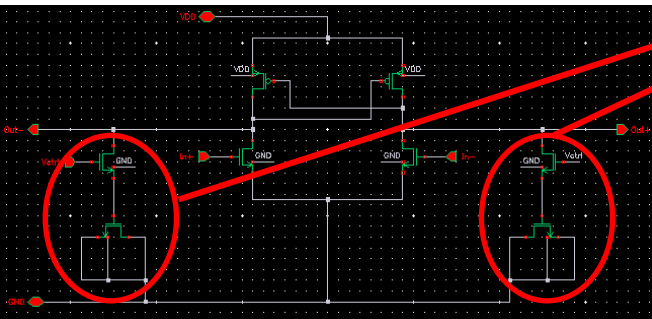

Delay controlled thro load


Current-Starved Delay Cell - SCH

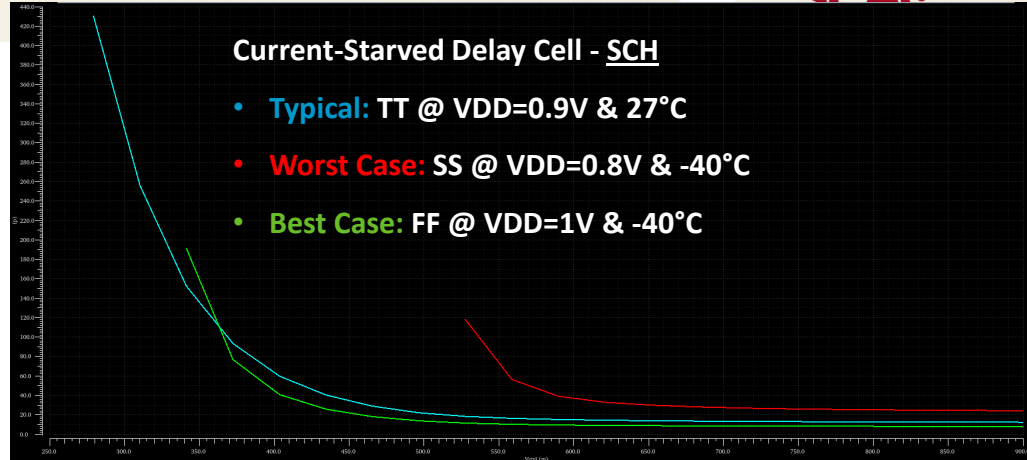- **Typical:** TT @ VDD=0.9V & 27°C
- **Worst Case:** SS @ VDD=0.8V & -40°C
- **Best Case:** FF @ VDD=1V & -40°C




Shunt-Capacitor Delay Cell - SCH

 - **Typical:** TT @ VDD=0.9V & 27°C
- **Worst Case:** SS @ VDD=0.8V & -40°C
- **Best Case:** FF @ VDD=1V & -40°C




Voltage-Controlled Delay Cell

Current-Starved Delay Cell:

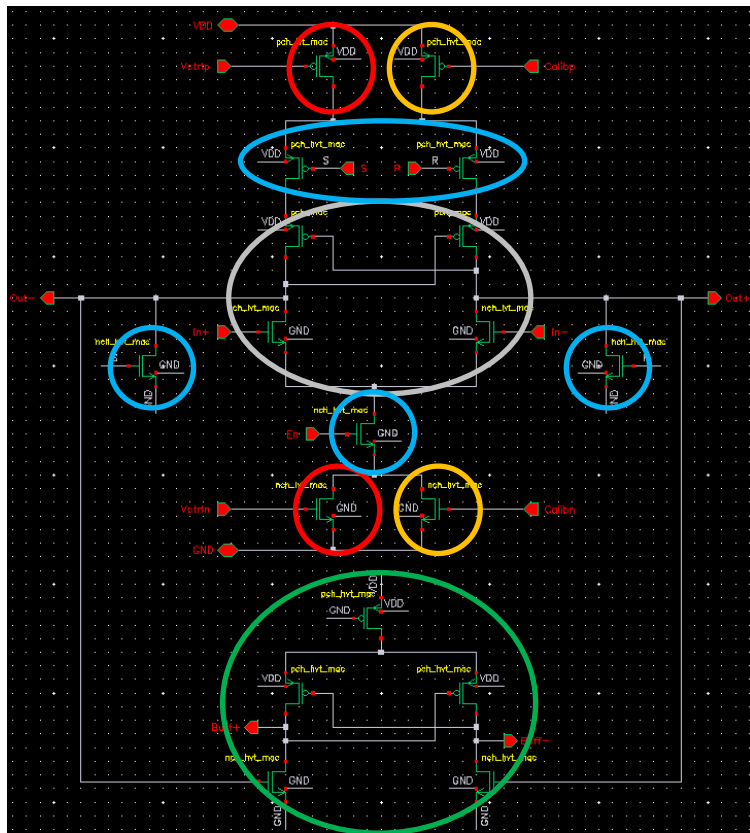


 - DCVSL core transistors
- Voltage Controlled Delay
- Calibration / Trimming
- Cell Logic Controls (Disable; Set; Reset)
- Output Buffers for access to the delay line state




Voltage-Controlled Delay Cells

❑ Current-Starved Delay Cell:


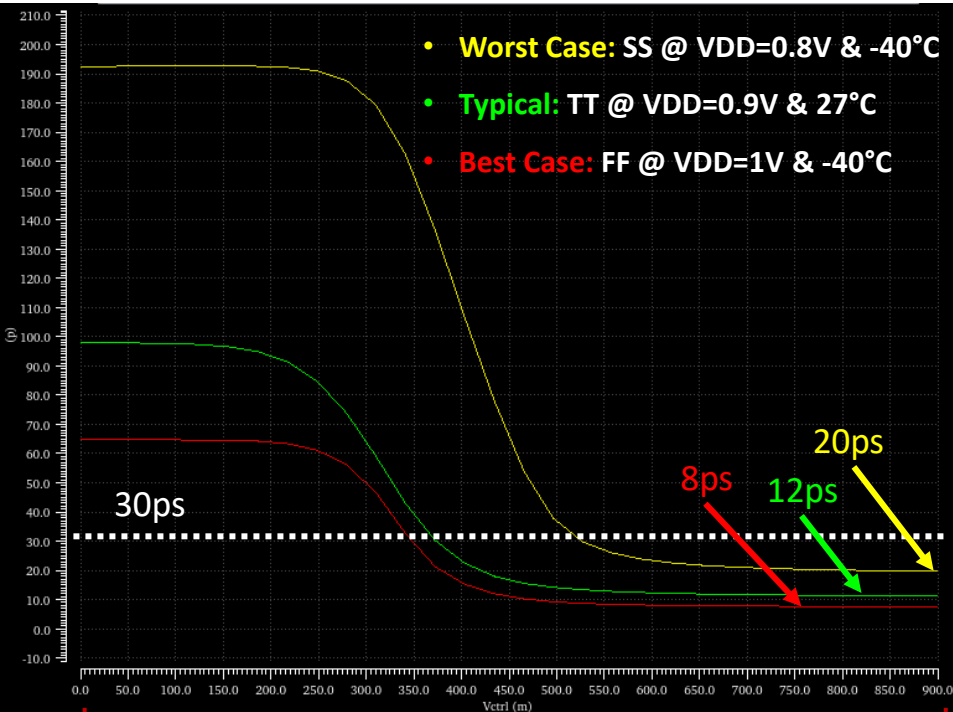


❑ Shunt-Capacitor Delay Cell :

 


Layout



Layout:

  

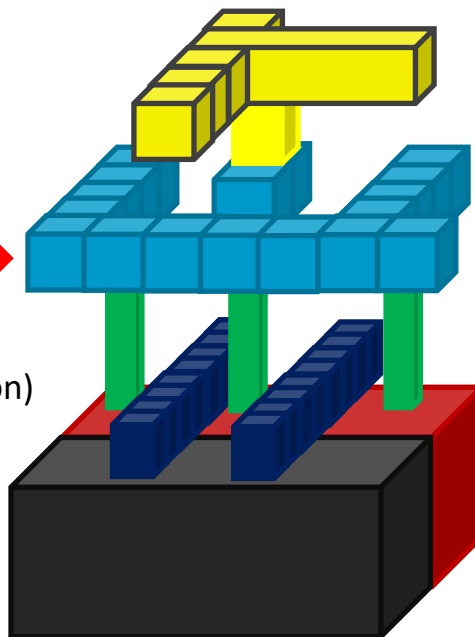- Transistor Active Area (Diffusion)
- Transistor Gate (Polysilicon)
- Contact (Poly/Diff to M1)
- Metal 1
- Via 1 (M1 to M2 connection)
- Metal 2





Schematic:

 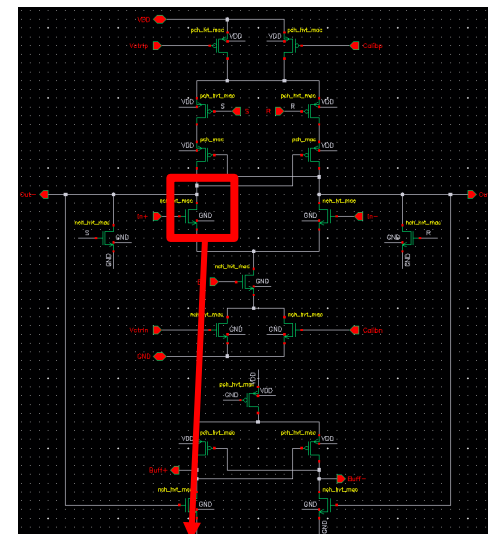


Layout: Parasitics



Layout:

  

 - Transistor Active Area (Diffusion)
- Transistor Gate (Polysilicon)
- Contact (Poly/Diff to M1)
- Metal 1
- Via 1 (M1 to M2 connection)
- Metal 2




Schematic:

 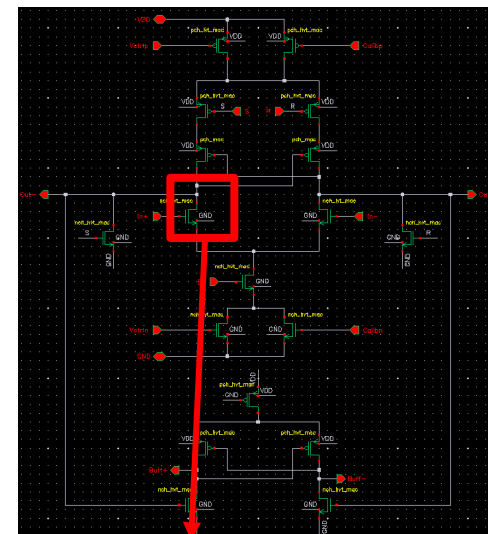


Voltage-Controlled Delay Cell

 Layout Parasitics Extracted (RCX) Simulation:



Layout:

 

Schematic:

