

Timing Circuits for HEP experiments


HEPIC Summer Week 2022

Bojan Markovic – markovic@slac.stanford.edu


28 June 2022

Detector Front-End: what are we measuring?


Event Detection:

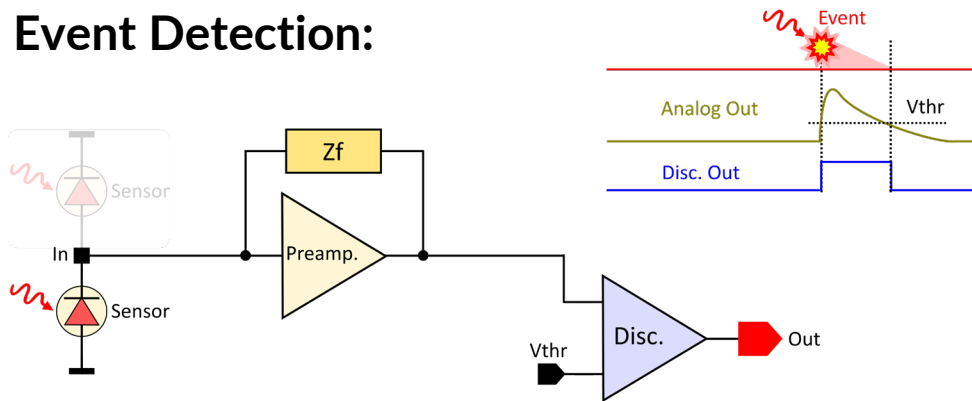


Event Counting:

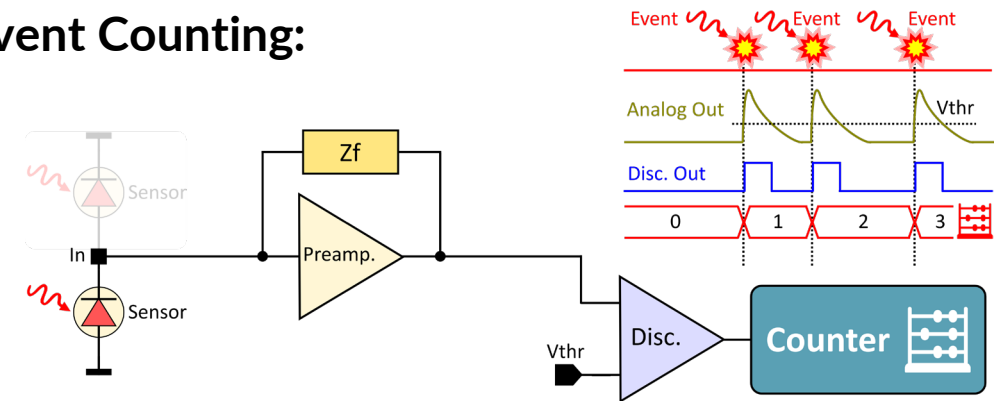

Energy Measurement:

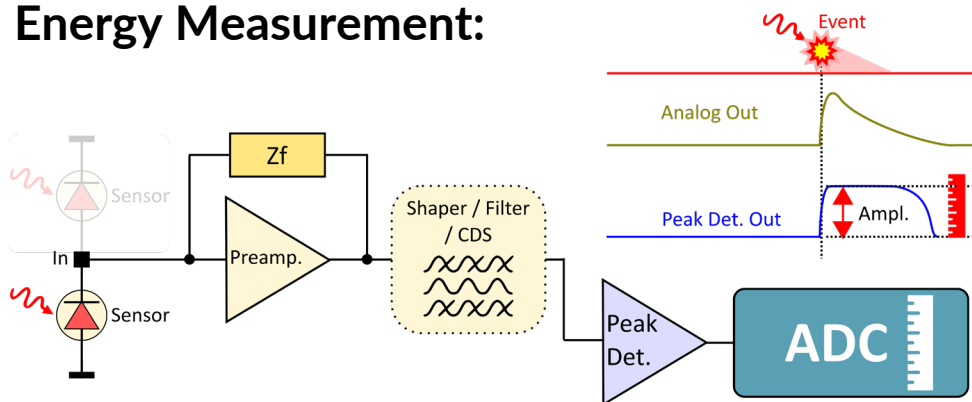


Time Measurement:

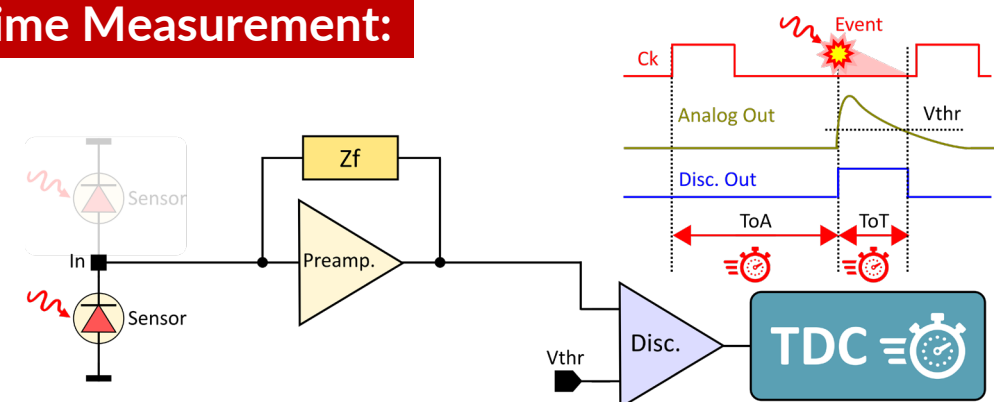

- ToA = Time-of-Arrival [ToF = Time-of-Flight]
- ToT = Time-over-Threshold
- TDC = Time-to-Digital Converter

Time Measurement

- ❑ **Time Measurement** is a loose term as time has no physical properties to measure. What we are really measuring is the duration separating two events, thus a more accurate term is **Time Interval Measurement**.
- ❑ Examples of ways of keeping track of passage of time throughout history include: sunrise/sunset, phases of the moon, sundials, water clocks, sandglasses, pendulum clocks, all the way to today's quartz clocks and atomic clocks.
- ❑ Nowadays official sources of time are provided by caesium atomic clocks, such as the ones operated by National Institute of Standards and Technology (NIST).
- ❑ The international standard (SI) unit of time [official definition]: *the second, symbol s , is defined by taking the fixed numerical value of the cesium frequency $\Delta\nu_{Cs}$, the unperturbed ground-state hyperfine transition frequency of the cesium-133 atom, to be 9,192,631,770 when expressed in the unit Hz, which is equal to s^{-1} .*
- ❑ Electronic high-precision time measurement circuits are called by different names: Time Interval Meters (TIM), time counters, time digitizers, **Time-to-Digital Converters (TDC)**.

 



Time-to-Digital Converters (TDC)

TDC applications in HEP:

- Systems with hundreds of thousands channels or more, distributed across large area; time precision/stability across whole system is critical
 - Detector/Sensor time resolution sets the requirements for the TDC
- Drift time in gas-based tracking detectors:
 - Low resolution: $\sim 1\text{ns}$
 - Examples: ATLAS and CMS muon drift tubes
 - Timing/TOF detectors:
 - High resolution: $10\text{ps} - 100\text{ps}$
 - Examples: ATLAS HGTD, CMS MTD, ALICE TOF

Other TDC application include:

  
- communication systems (frequency synthesis, ADPLL, CDR, ...);
- distance measurements (LiDAR, 3D imaging, ...);
- biomedical imaging (TOF PET, FLIM, ...);
- photon science (COLTRIMS, ...);
- general instrumentation (jitter measurement, ...);



ATLAS High-Granularity Timing Detector (HGTD) for HL-LHC upgrade



Analog Waveform Sampling + DSP post-processing

 - ❑ Picosecond time resolution can be extracted using high-speed sampling of analog waveform followed by digital signal processor (DSP) post-processing performing matching to a known pulse shape:




- ❑ For applications with hundreds/thousands of channels/pixels, the use of high-speed waveform sampling with DSP processing becomes cost and power prohibitive.
- ❑ To simplify timing measurements, **discriminators** are used to translate analog signals into digital ones, preserving only timing information of interest (losing analog amplitude/shape information)

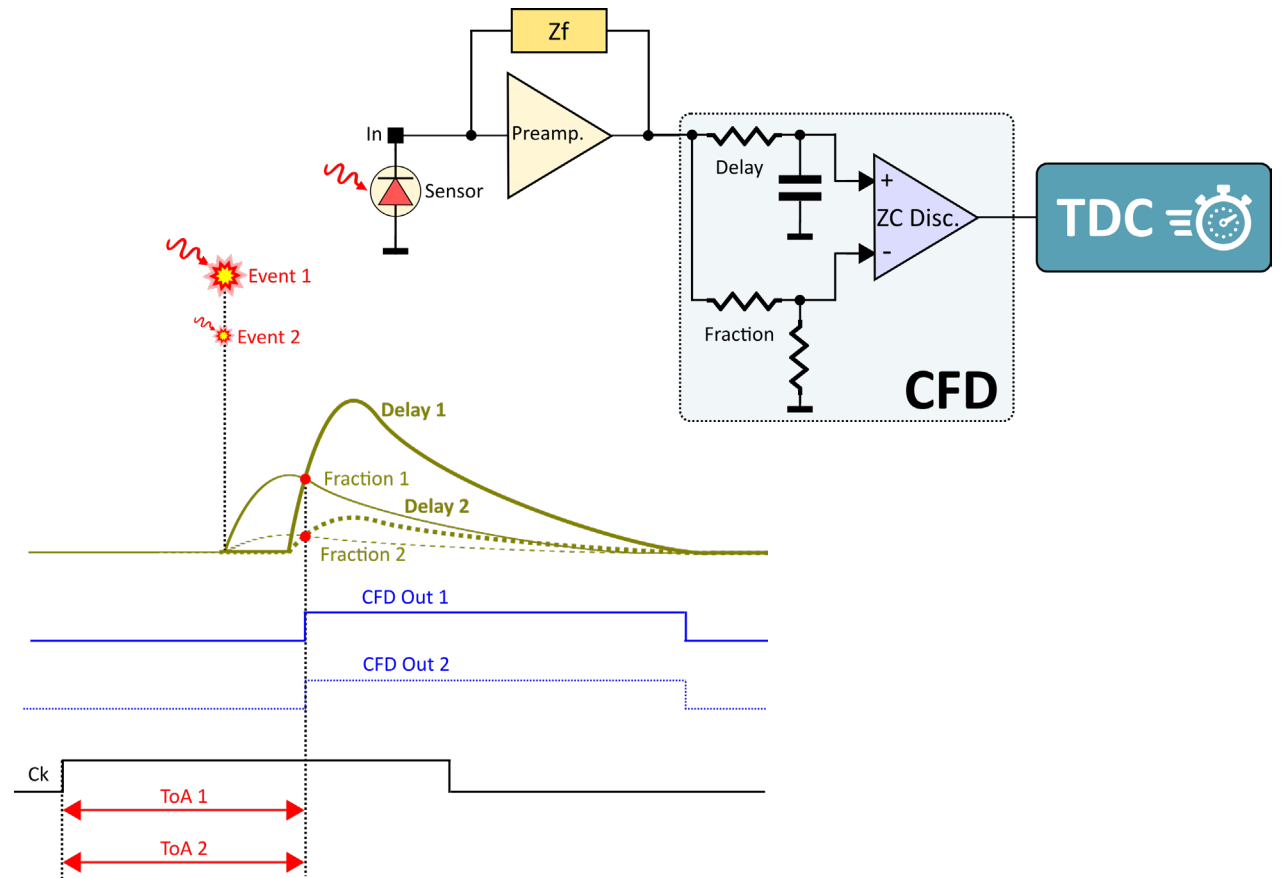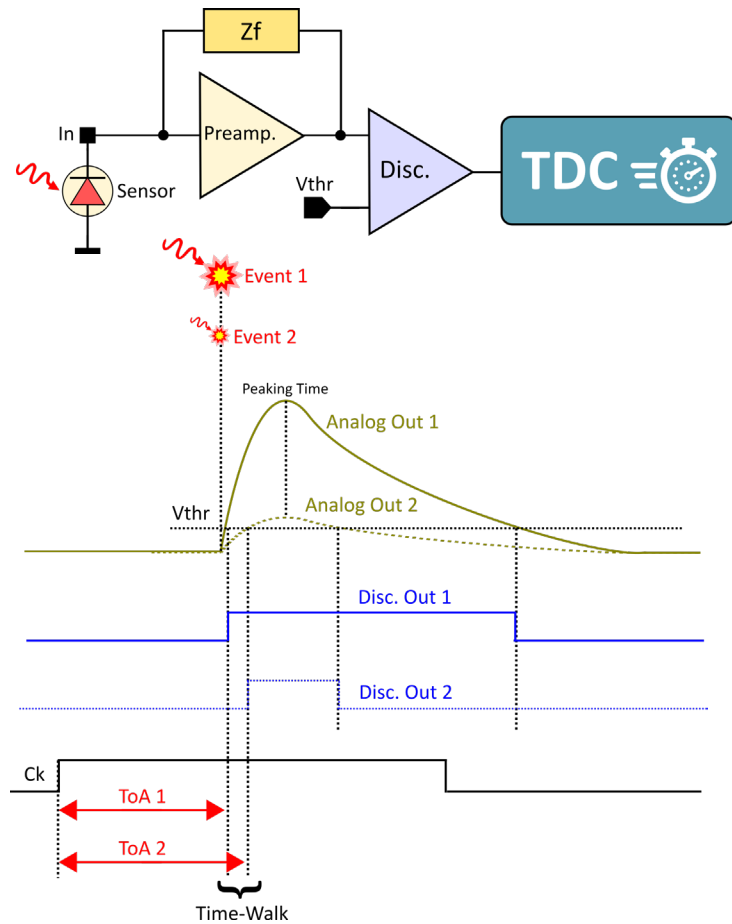Time-Walk, Constant Fraction Discriminator (CFD)




- Constant Fraction Discriminators (CFD) are not simple to implement in channel-dense ICs.

Time-Walk, Time-over-Threshold (TOT)

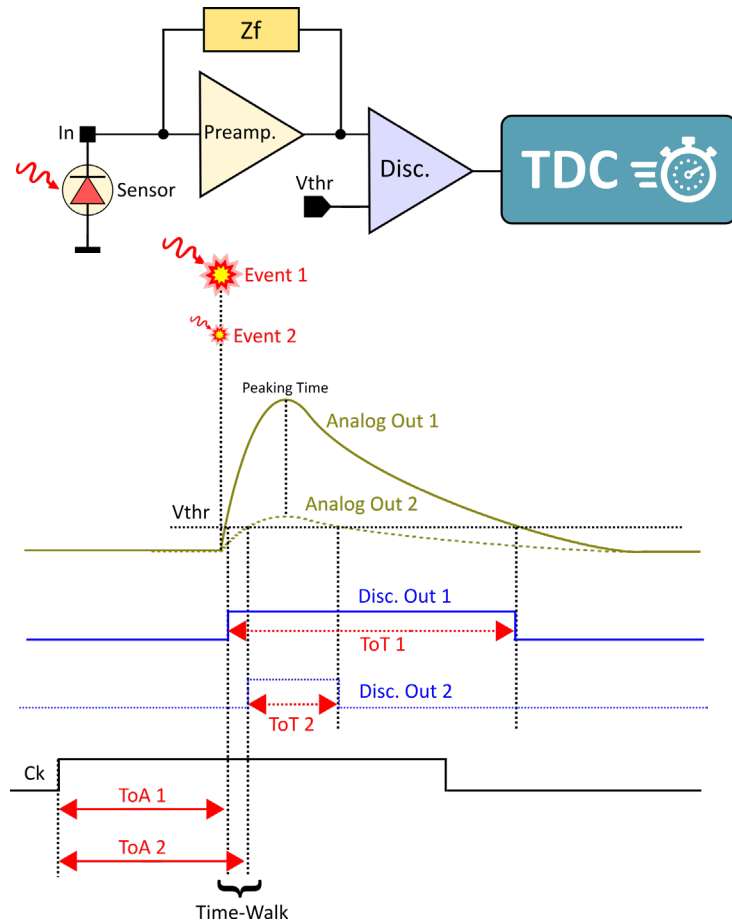

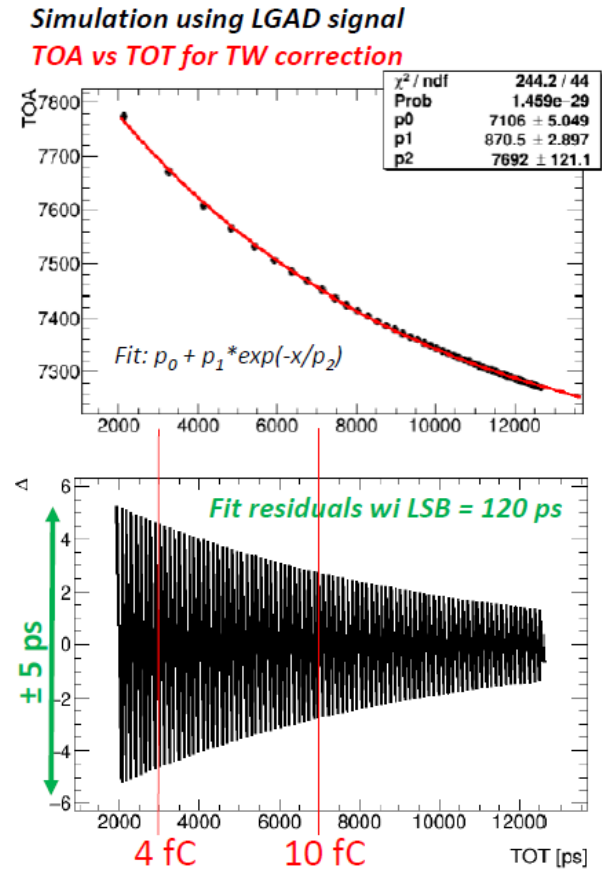- Altiroc (front-end ASIC for ATLAS HGTD detector) - example of estimation of TW correction accuracy:





- Constant Fraction Discriminators (CFD) are not simple to implement in channel-dense ICs; in HEP designs, most often ToT measurement (i.e., an indirect coarse measurement of amplitude) is used for offline Time Walk correction. [Other ways of dealing with Time Walk exist, but are rarely used]

Inputs of a TDC


❑ Time interval (T) to be measured is defined by:

- Width of an input pulse signal (**PulseIN**)
- Time elapsed between two input steps/pulses (**START** and **STOP**)

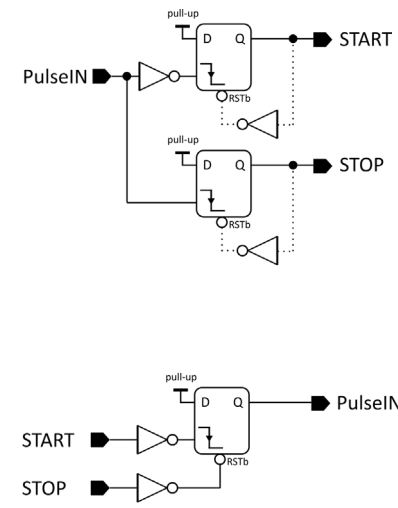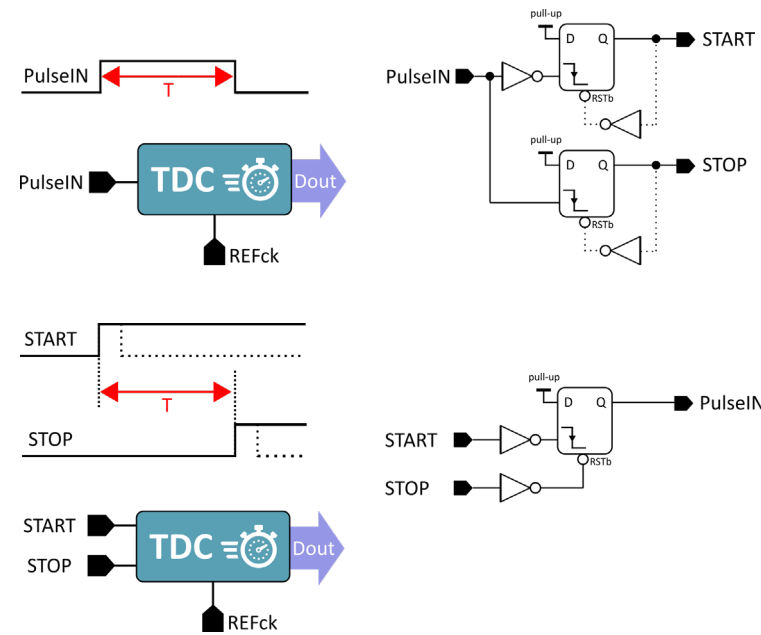❑ Measurement is referred/calibrated to a high accuracy reference clock (quartz/atomic clock)



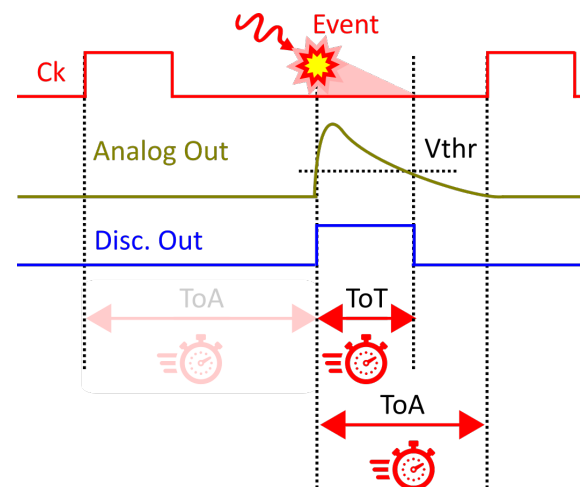
Easily interchangeable; all following TDC architectures can be implemented using either representation



- ToA – time elapsed between discriminator output rise time and clock edge
- ToT – pulse-width of discriminator output

TDC Performance Metrics

- ❑ **Resolution:** quantization step of the conversion, i.e. LSB [ps, ns]
- ❑ **Single-Shot Precision (Jitter):** statistical variation of results for measurement of the same time-interval; expressed as standard deviation (rms) or full width at half maximum (FWHM) [ps, ns]
- ❑ **Dynamic Range (Measurement Range):** maximum time interval that can be measured [ns]
- ❑ **Conversion Time (Dead Time):** minimum time between end of one conversion and the start of next conversion [ps, ns]
- ❑ **Conversion Non-Linearities (INL and DNL):** deviation of the conversion characteristics from the ideal/fitted one [%LSB]
- ❑ **Power Consumption** [mW]
- ❑ **Area** [μm^2]
- ❑ **Technology** [nm]
- ❑ **Radiation Tolerance** (specific to HEP applications) [TID: Mrad, Grad]

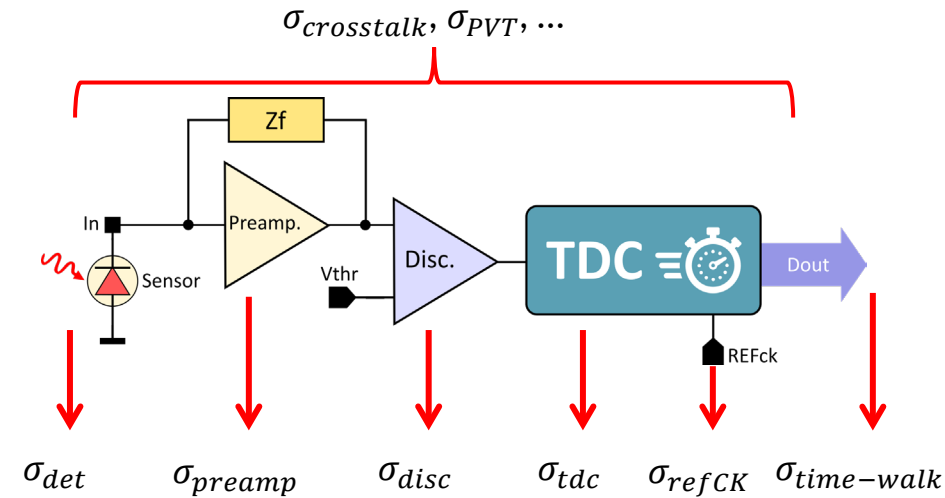

$$\sigma_{\text{single-shot}} = \sqrt{\sigma_{\text{det}}^2 + \sigma_{\text{preamp}}^2 + \sigma_{\text{disc}}^2 + \sigma_{\text{refCK}}^2 + \sigma_{\text{tdc}}^2 + \dots}$$

$$\sigma_{\text{tdc}} \geq \sigma_q = \frac{\text{LSB}}{\sqrt{12}}$$

$$\sigma_{\text{av}} = \frac{\sigma_{\text{single-shot}}}{\sqrt{N_{\text{samples}}}}$$


Counter

- Simplest method of measuring time intervals is by using a counter.
- Resolution is given by the period of reference clock:
LSB = T_{ck} (1GHz clock → LSB = 1ns)


$$\sigma_{tdc} = \frac{T_{CK}}{\sqrt{12}}$$

- Range is defined by number of bits of the counter
- PROS:** simplicity, reliability, easily extendable range
- CONS:** resolution limited by clock frequency (not practical for resolutions lower than 1ns)
- Usually employed as a 'coarse' stage to extend the measurement range

- Local counter in each channel:


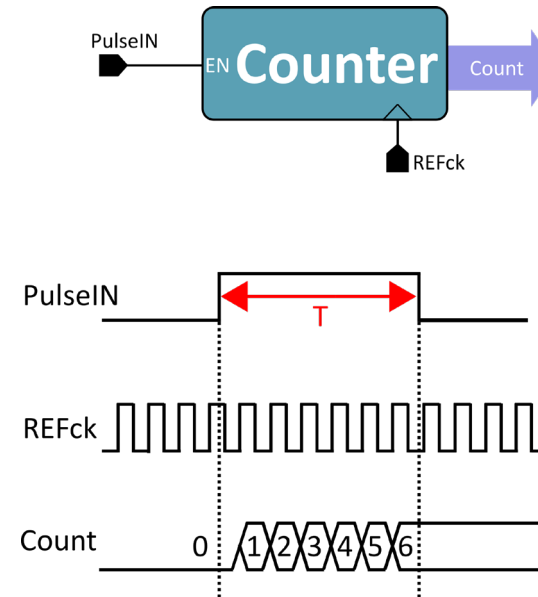


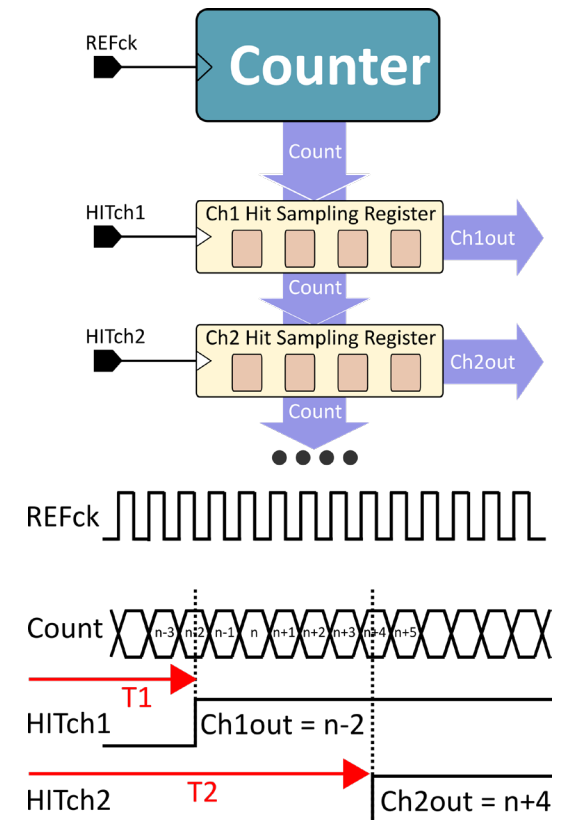- Global counter with sampling per channel (grey code and/or synchronization of HIT to CK necessary):



Multistage/Interpolating/Nutt-method TDC

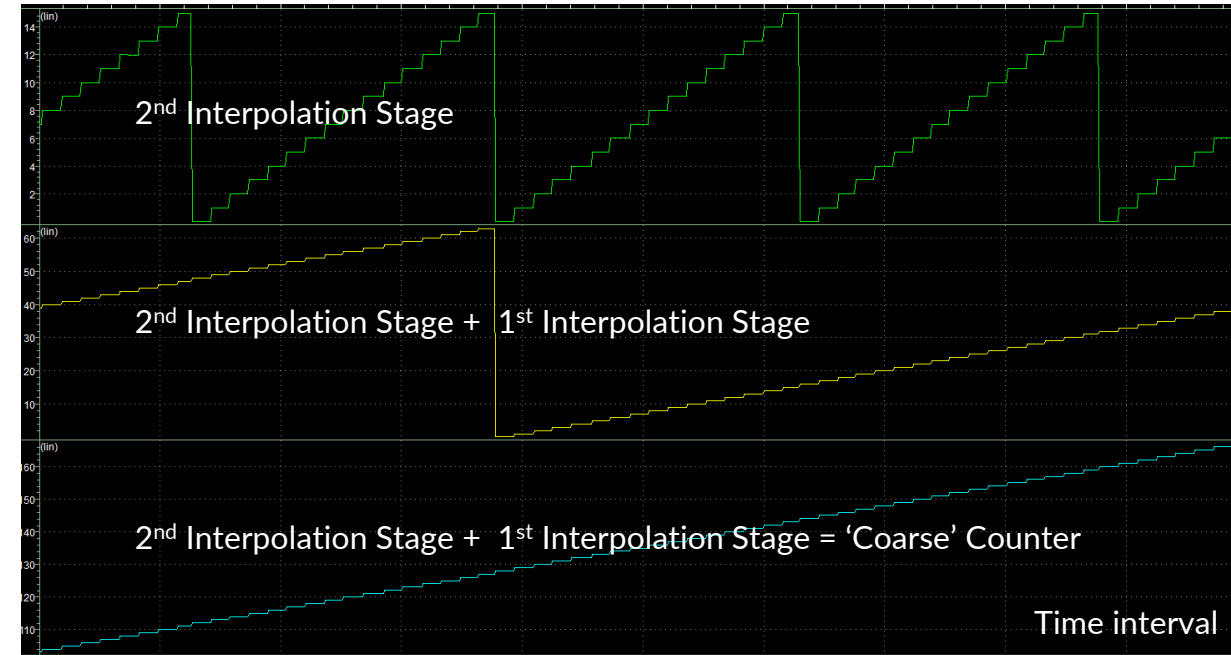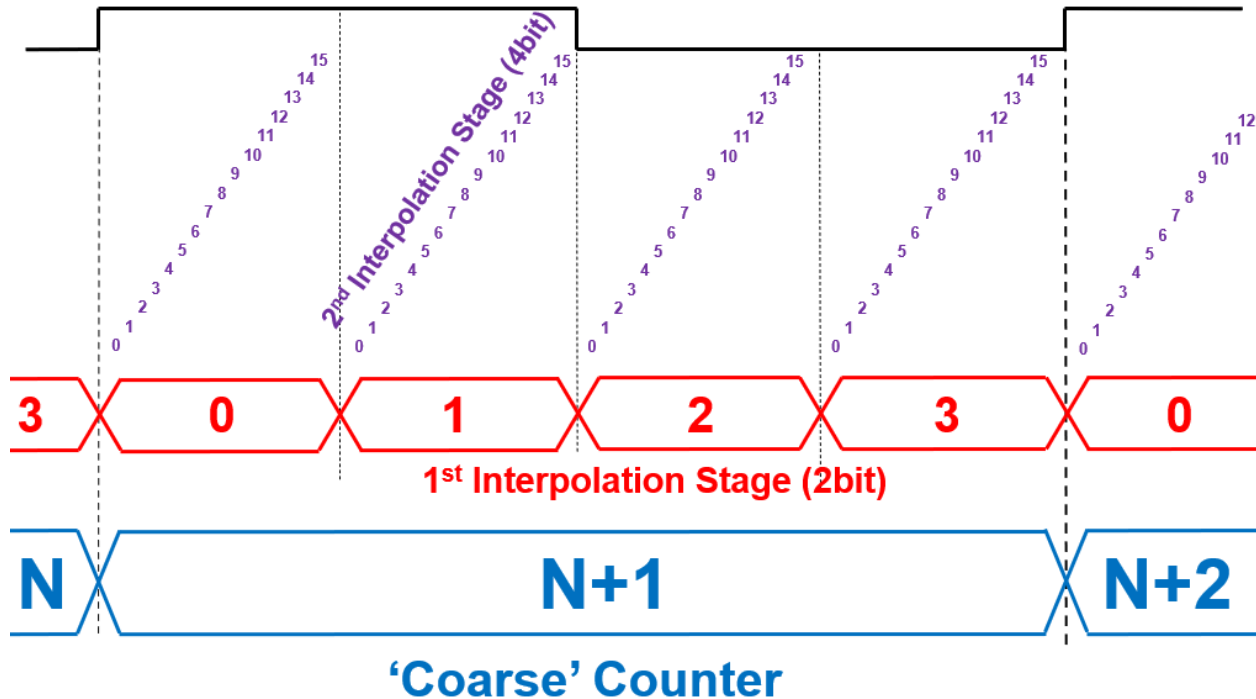
- Most multistage/interpolating TDCs (sometimes referred to as Nutt method TDCs) use counters as a 'coarse' stage to extend the dynamic range, while some of the 'fine' (sub-ns) measurement methods, described in following slides, are used as interpolators to provide high resolution:



Indirect/Analog 'Fine' Measurement Methods

❑ This methods perform an indirect conversion of time to digital code by passing through an intermediate step of conversion to an analog voltage.

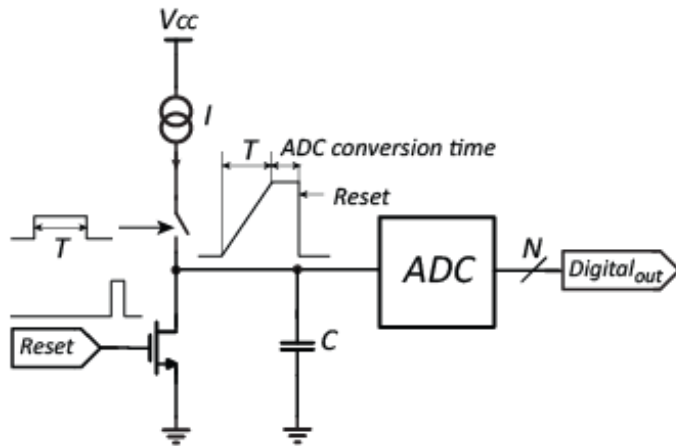
❑ Time-to-Amplitude Converter (TAC) followed by ADC:



- Charging a capacitor with constant current during time interval T performs the conversion to analog voltage that can then be digitized by an ADC. Moves the complexity to ADC domain.
- **CONS:** requires and ADC.

❑ Architectures used extensively in past but not very suitable for implementation in modern scaled technologies and applications requiring hundreds/thousands of channels/pixels.

 
❑ Dual-Slope Pulse Stretching followed by a Counter:




- Charging a capacitor during time interval T and discharging it with much smaller current “stretches” the interval so that it can be accurately measured with a basic counter (similar to dual-slope ADC)
- **CONS:** long conversion time.

Direct/Digital 'Fine' Measurement Methods: Pulse Shrinking


❑ Pulse Shrinking:

 

❑ Cyclic Pulse Shrinking:

 

 6-bit conversions requires 64 cells and 64 flip-flops in the regular pulse-stretching method; cyclic configuration can use just 4 cells and 4+4=8 flip-flops



- Unequal rise/fall times between two inverters that compose the elementary cell (buffer) perform shrinking of the pulse-width by the quantity:

$$LSB = (t_1^{fall} + t_2^{rise}) - (t_1^{rise} + t_2^{fall})$$

- This LSB can theoretically be arbitrarily small (not limited by technology logic propagation delay)
- Dynamic range (DR) is given by number of elementary cells (N) multiplied by LSB (thermometric scale → area inefficient):

$$DR = N \cdot LSB$$


- Cyclic configuration allows to extend the dynamic range by delegating the MSB part of the conversion result to a counter (binary representation → area efficient). Still DR is limited by total propagation delay of the loop:

$$DR = N \cdot t_p \quad \text{where } t_p \text{ is cell propagation delay and } t_p > LSB$$



- While LSB can be smaller than technology propagation delay, pulse stretching is used less often than Vernier delay lines due to difficulty of maintaining the rise/fall time ratios with PVT variations.

Direct/Digital 'Fine' Measurement Methods: Time Amplifiers

 - Amplifies the time interval relaxing the LSB requirements of the following stage (counter or another 'fine' time measurement method like delay lines etc.)




 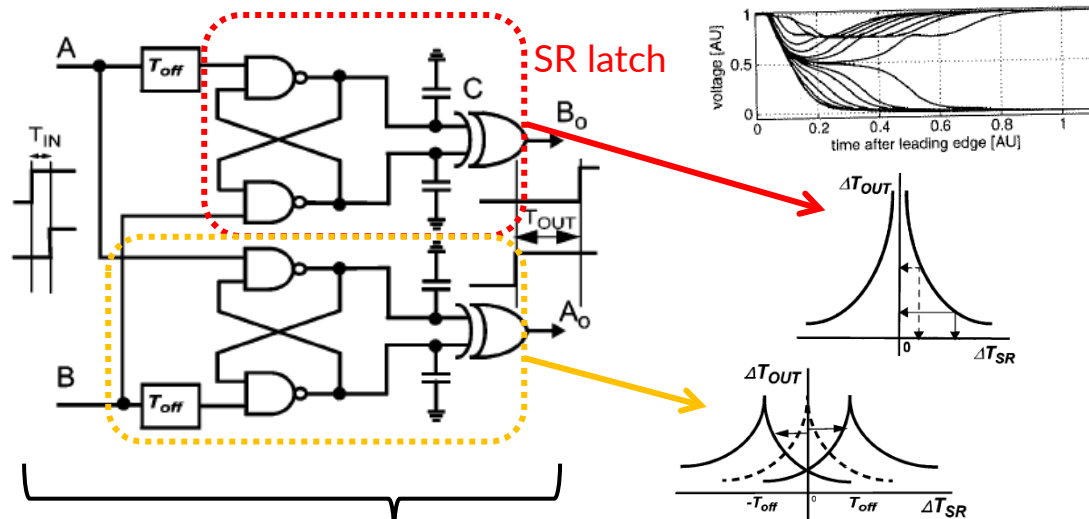- SR latch based TA** – exploits the input dependent propagation delay of a SR latch in metastable region:




- CONS:** very limited linear range; gain not well predictable \rightarrow necessitates calibration; hard to use in practice

 - Cross-coupled Delay Line TA** – delay cells with two possible propagation delays (low t_L and high t_H); two delay lines where cells in one switch the delay of corresponding cell in the other line from low to high delay:



Delay Cell example:

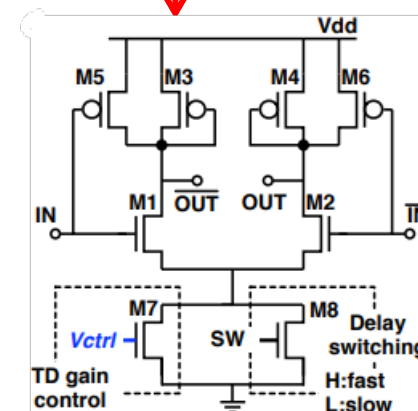


$$Gain = \frac{t_H}{t_L}$$

- DLL used to fix propagation delays against PVT variations
- CONS:** long dead-time

Direct/Digital 'Fine' Measurement Methods: Delay Line

Majority of modern TDCs is based on some variation of a Delay-Line structure.

Regular (Tapped) Delay Line:

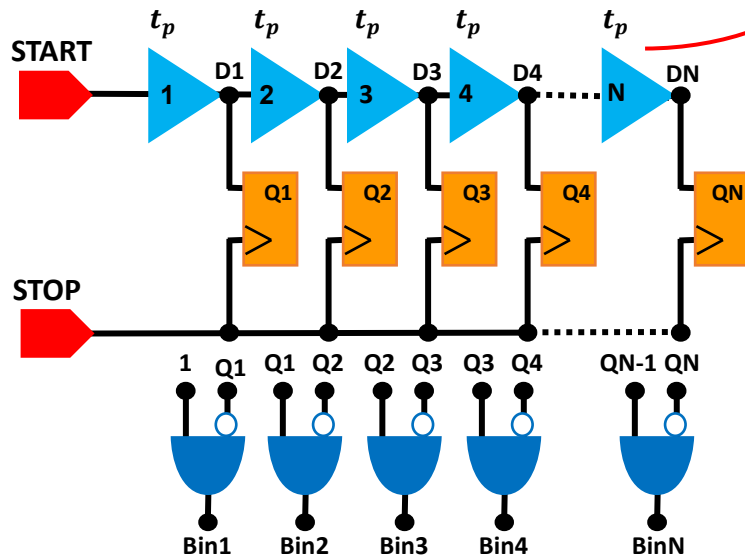


TDC resolution given by the propagation delay of the elementary cell:

$$LSB = t_p$$

$$DR = N \cdot LSB$$


Basic element: Delay Cell

Simple Logic

 

- Used in FPGA TDCs (carry chain mux, etc.)
- Requires constant calibration

Digitally-Controlled Delay Cell:

 


Fully Digital - minimum delay limited by fastest achievable logic propagation delay in target technology

Voltage-Controlled Delay Cell (VCDC):

- Current starved:
 - Shunt capacitor:
-
-
- Delay controlled thru current
- Delay controlled thru load

 Differential delay cell with symmetric loads (Maneatis cell [1]):





- Frequently used in PLL VCOs and DLLs
- Consumes Static Bias Current



[1] J. G. Maneatis, "Low-jitter process-independent DLL and PLL based on self-biased techniques," IEEE J. Solid-State Circuits, vol. 31, no. 11, pp. 1723-1732, Nov. 1996.

Rise & fall times (pmos & nmos strength) do not match well over PVT variations → single inverters are less often used as delay cells; usually series of 2 inverters or differential buffers are used as delay elements → propagation delay doubles

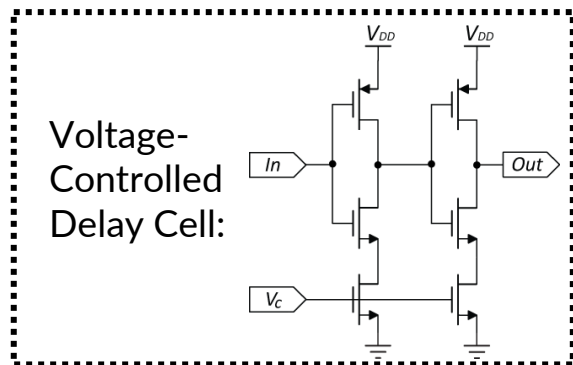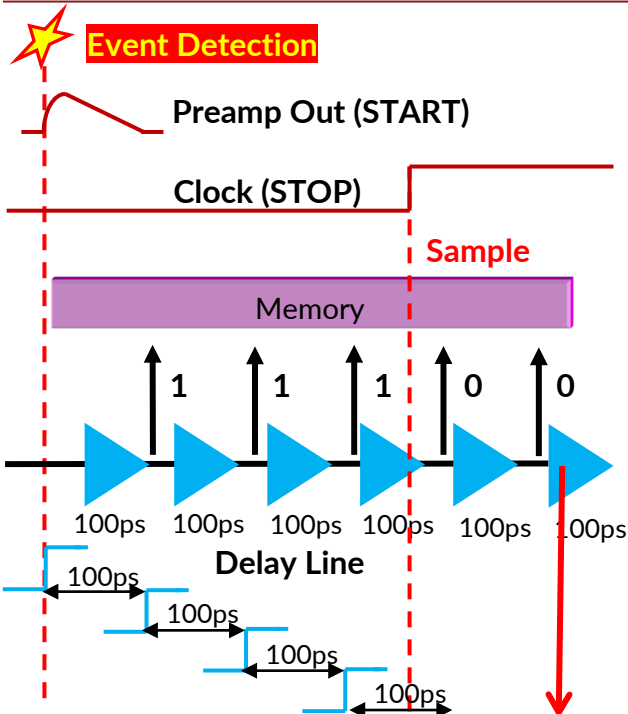VCDC propagation delay control: trimming, PLL, DLL




- Trimming using resistor voltage dividers or DACs – open loop control → delay value varies with PVT variations → necessitates frequent recalibration (usually used for off-chip Vctrl control during prototype characterization)
- Phase-Locked Loops (PLL) - closed loop: PLL acts on Vctrl in order to lock the VCO (Voltage-Controlled Oscillator) frequency to a desired value regardless of PVT variations.

  


$$t_{p_DelayCell} = \frac{1}{f_{VCO} \cdot N_{cellsVCO}}$$

 Voltage-Controlled Delay Cell Characteristic:



 - Delay-Locked Loops (DLL) - closed loop: DLL acts on Vctrl in order to lock delay line propagation delay to the period of input clock regardless of PVT variations.




$$t_{p_DelayCell} = \frac{T_{CK}}{N}$$

- Most widely used method for VCDC delay control;
- Simpler than PLLs; usually one dominant pole;
- Doesn't filter input clock jitter
- False Locking Issue.


Delay Line, Multiphase Clock

- Delay Line per channel/pixel, global DLL generates V_{ctrl} that is propagated to each channel (most common approach for high channel count implementations):

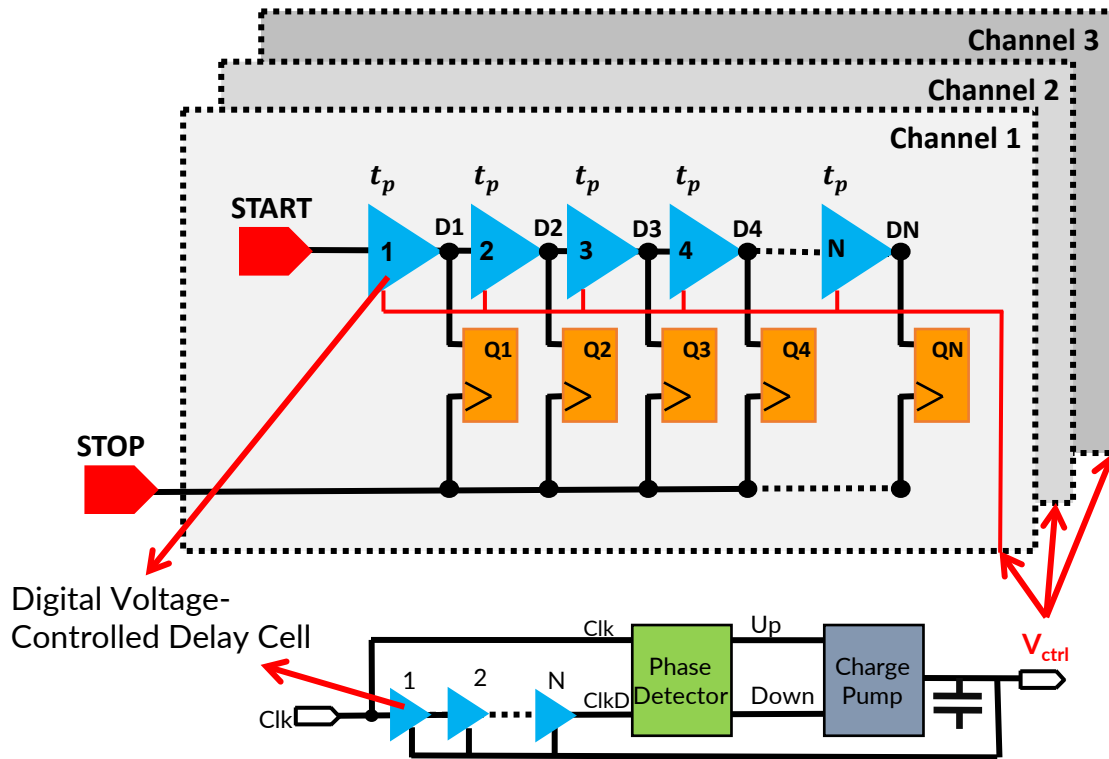
- Mismatch (process, supply) between DLL delay cells and channel delay cells is a possible issue



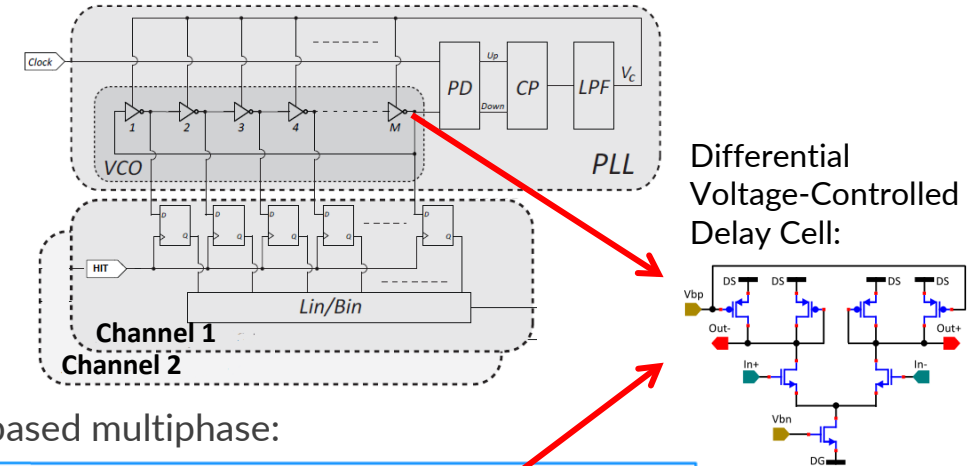- Global DLL or PLL provides multiphase clock that is propagated and sampled in correspondence of each channel/pixel HIT event:
 - PLL-based multiphase:




- DLL-based multiphase:

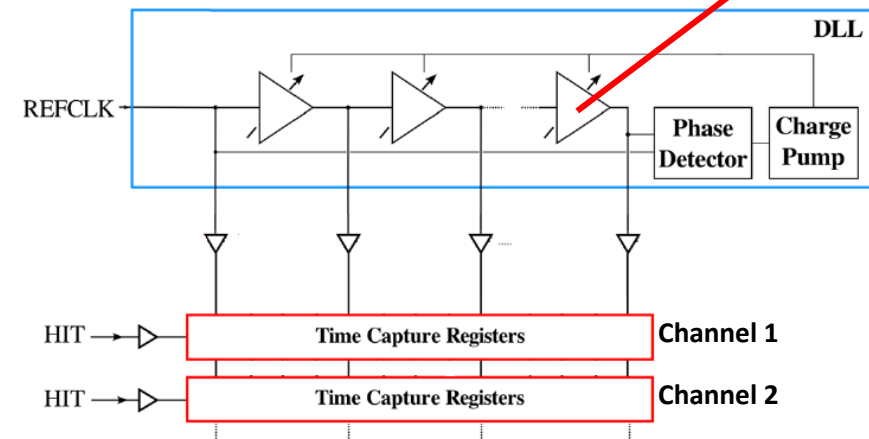


- DLL-multiphase TDC per channel/pixel. Theoretically best delay accuracy but usually power and area prohibitive

Delay Line Configurations


Regular/Linear Delay Line:

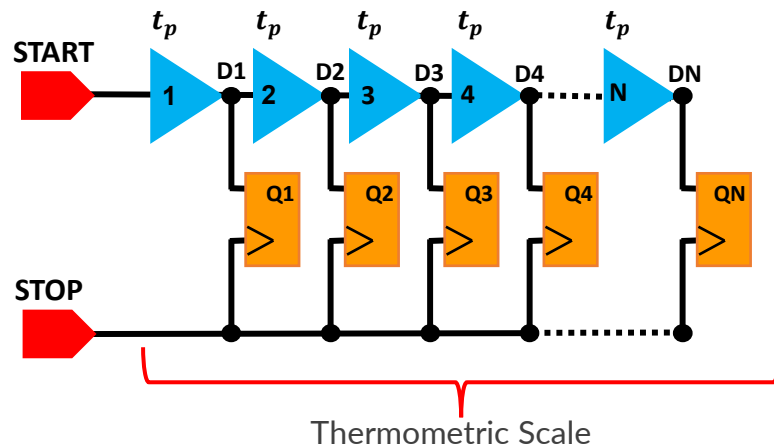

Ring Oscillator:

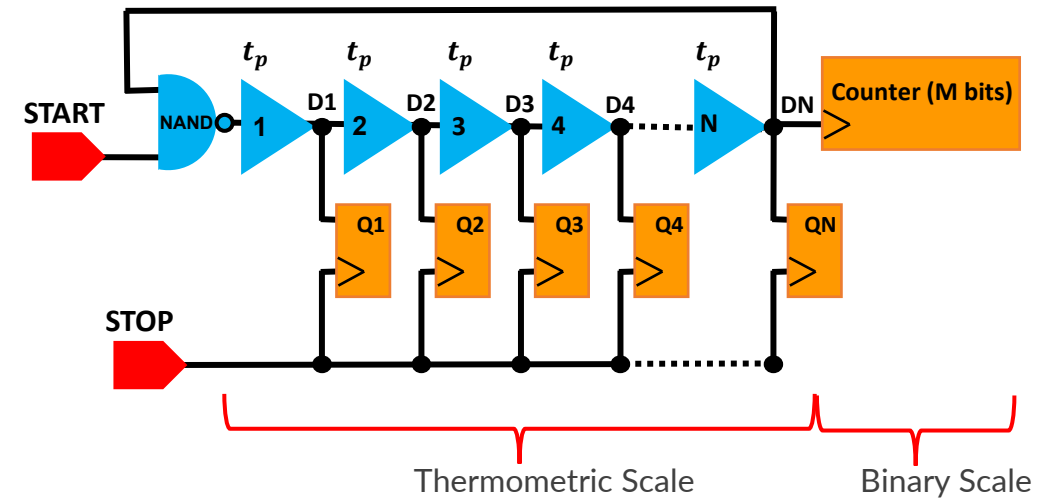

Cyclic Delay Line:

 


- Timing always on the same edge
- Bringing signal back to the input causes non-linearity (wider bin/bins)
- START pulse-width must be lower than $N \cdot t_p$. Unequal rise/fall times cause pulse-shrinking or pulse-stretching → limits maximum number of cycles before the pulse is lost; requires pulse-width regeneration (issue relaxed with differential / pseudo-differential delay cells)



- LSB = t_p DR = $(N + 2^{M+1}) \cdot LSB$
- Timing on both rising and falling edges; unequal rise/fall times introduce non-linearities (issue relaxed/avoided with differential / pseudo-differential delay cells)
 - Bringing signal back to the input causes non-linearity (wider bin/bins)
 - Special versions of the Ring Oscillator:
 - Gated Ring Oscillator (GRO);
 - Switched Ring Oscillator (SRO).
- Perform noise shaping; require repetitive measurement of the time-interval (ADPLL)

Digital Voltage-Controlled Delay Cells

Shunt-Capacitor Delay Cell:

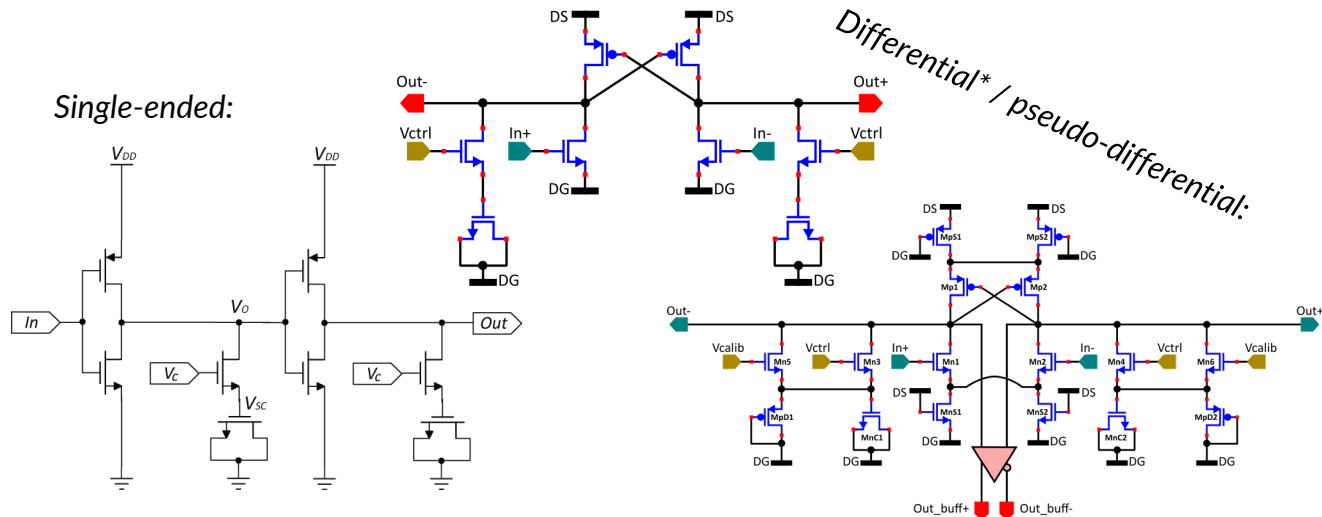


  - Delay controlled thru variable load
- **PROS:** more contained and linear voltage-delay characteristic.
- **CONS:** bigger area.




Current-Starved Delay Cell:




Single-ended:

 

Differential* / pseudo-differential:

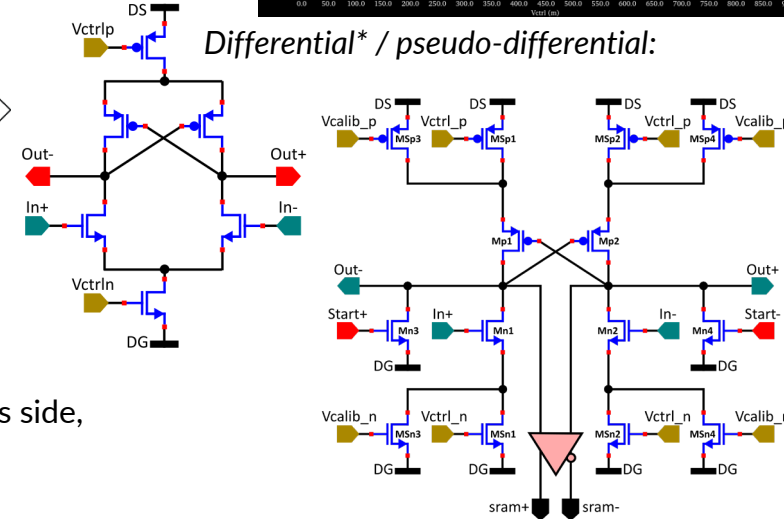


  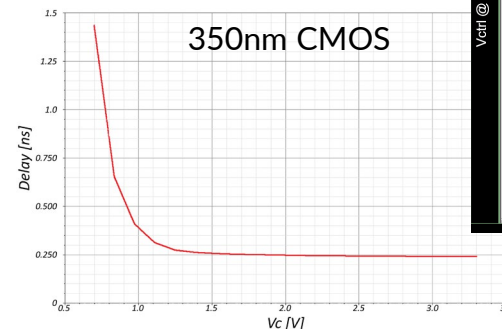- Delay controlled thru variable current (nmos side, pmos side, both)
- **PROS:** smaller area.
- **CONS:** highly non-linear voltage-delay characteristics (less pronounced in newer/scaled technologies)




Direct/Digital 'Fine' Measurement Methods: Sub-gate delay

 Resistive interpolation across neighboring delay cells:



- Rise time > propagation delay
- Parasitic capacitances make this resistive division a mixture of R division and RC delays:
 - Low resistor values required to prevent RC component from dominating;
 - With equal resistances the bins are not evenly spaced; needs optimization of individual resistors
 - Does not fully auto-scale with propagation delay of the cell

Multipath Delay Cells:

 

- Requires constant operation/oscillation or gated ("freezing" of charge on internal nodes) function (i.e. GRO) with repetitive/periodic measurements of the time intervals. Used in ADPLL applications but not very suitable for single-shot measurements with rare events (like most HEP applications).



Vernier Delay Line

- Resolution not based on propagation delay of a single cell but on the difference of propagation delays of two delay cells → LSB smaller than logic gate delay in the target technology is possible





More on the next slide

Vernier Delay Line

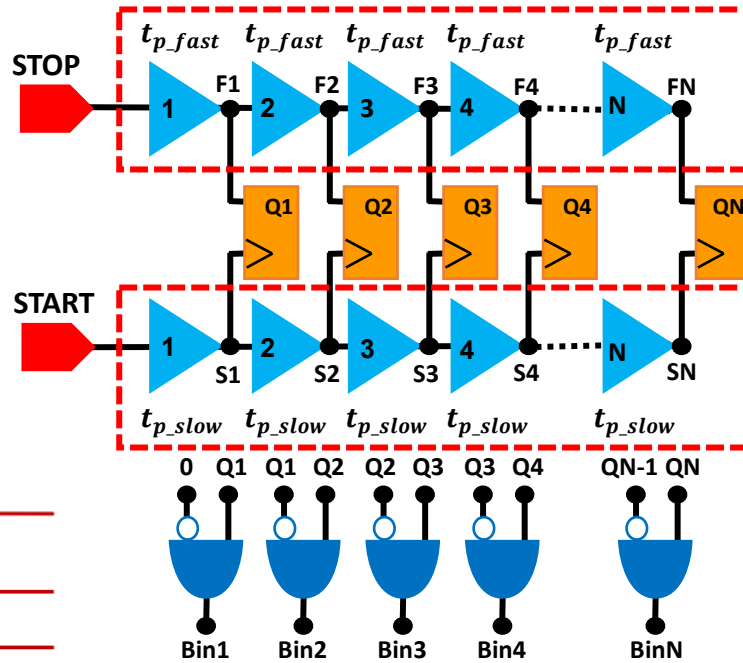 

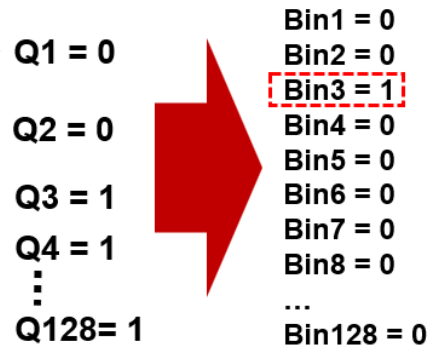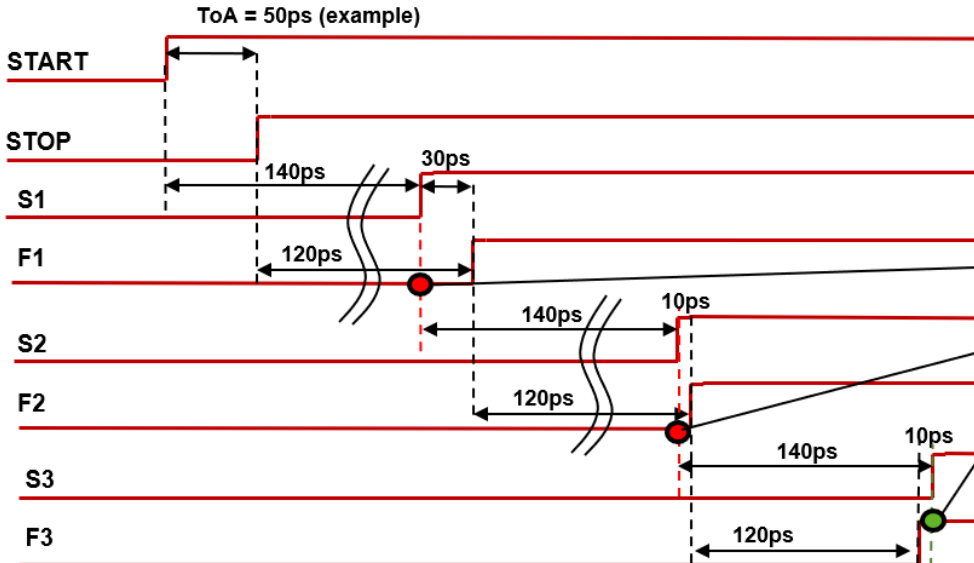- START signal propagates in the Slow Delay Line ($t_{p_slow} > t_{p_fast}$)
- STOP signal propagates in the Fast Delay Line




- The **START** pulse comes first and initializes the TDC operation.
- The **STOP** pulse follows the **START** with a delay that represents the time interval to be digitalized.
- At each tap of the Delay Line the **STOP** signal catches up to the **START** signal by the difference of the propagation delays of cells in Slow and Fast branches, i.e., $t_{p_slow} - t_{p_fast}$ represents the **LSB** of time measurement.
- The number of cells necessary for **STOP** signal to surpass the **START** signal represents the result of TDC conversion.

$$LSB_{TDC} = t_{p_slow} - t_{p_fast}$$


$$DR = N \cdot LSB$$

Vernier Delay Line – Variants:


Cyclic Vernier Delay Line:

 


Vernier Ring Oscillator:

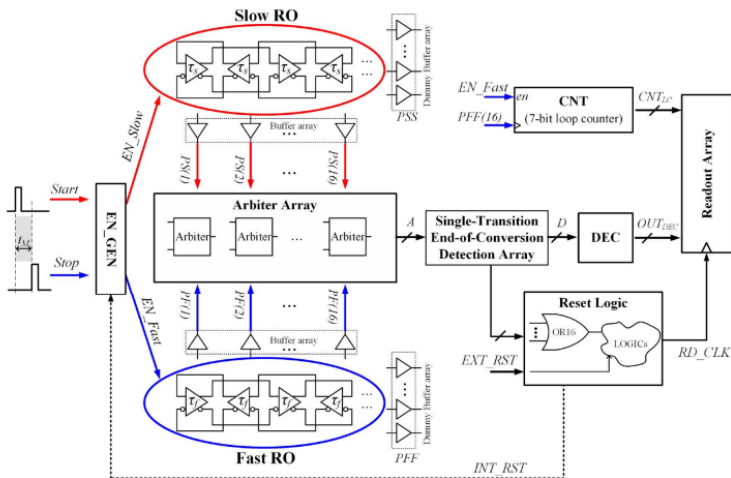

2D Vernier:

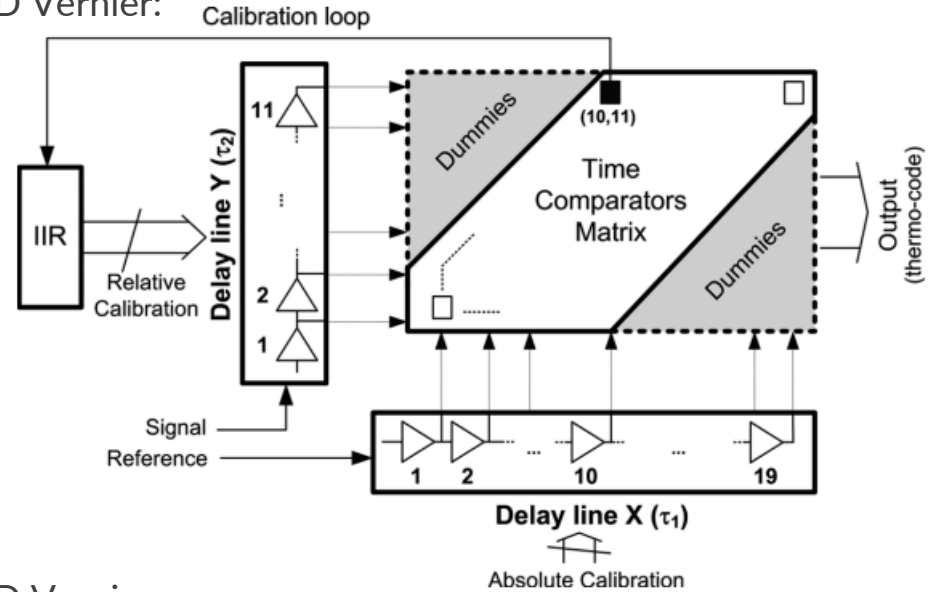


3D Vernier:

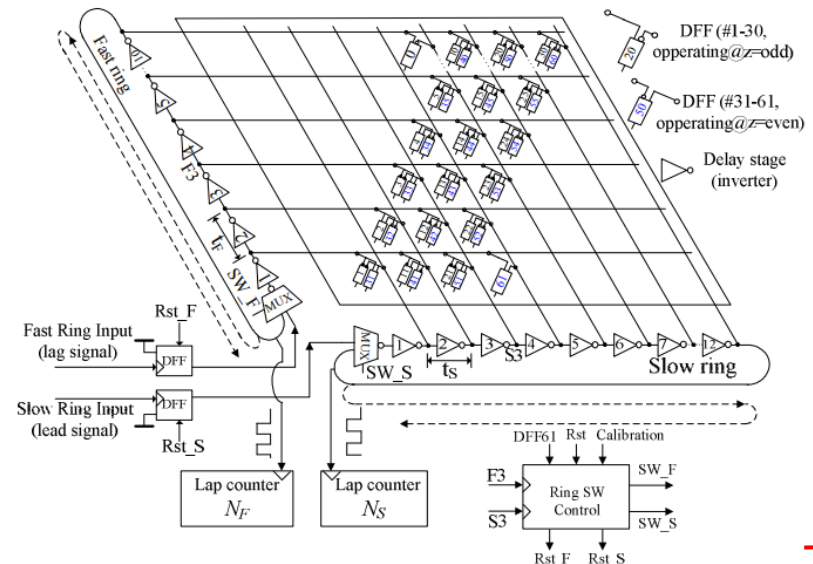


Extends range, lowers area, power consumption and conversion time compared to traditional linear Vernier delay line

Regular VS Vernier Delay Line (1/3)

Regular (Tapped) Delay Line:

 

Vernier Delay Line:

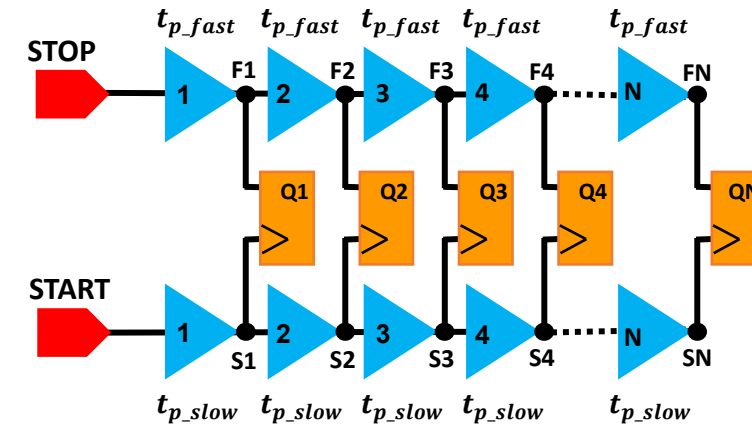

VS

- Simpler
- Resolution (LSB) limited by technology
- Smaller Area
- Shorter Conversion Time (independent on time interval being measured)
- Lower Power Consumption


- More complex
- Resolution (LSB) not limited by technology
- Bigger Area:
 - 2 delay lines instead of one
 - Bigger delay cells due to more stringent mismatch requirements
- Longer Conversion Time (dependent on time interval being measured)
- Higher Power Consumption

Regular VS Vernier Delay Line (2/3)

Regular (Tapped) Delay Line:

Tixel (130nm CMOS; 100ps resolution)


 
Delay Cell Layout [area $\approx 127.6\mu\text{m}^2$]:



Vernier Delay Line:

Altiroc (130nm CMOS; 20ps resolution)

 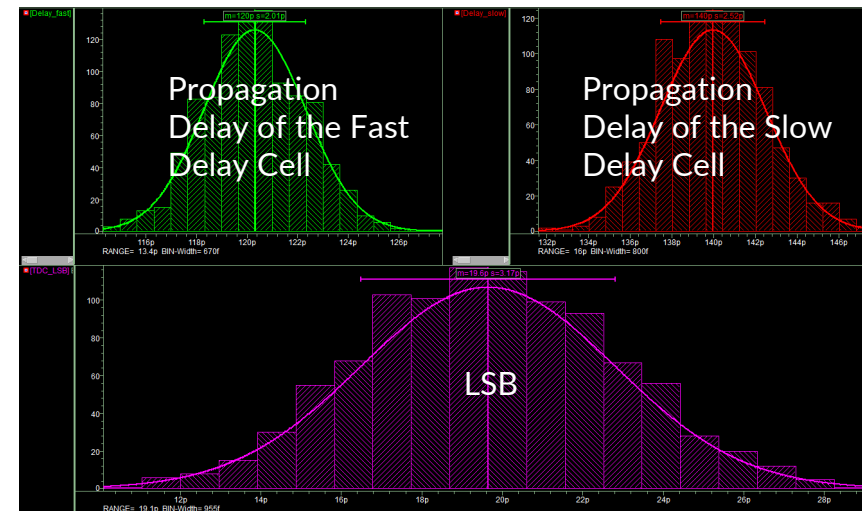Delay Cell Layout [area $\approx 546\mu\text{m}^2$]:




VS

- Simpler
- Resolution (LSB) limited by technology
- Smaller Area
- Shorter Conversion Time (independent on time interval being measured)
- Lower Power Consumption

- More complex
- Resolution (LSB) not limited by technology
- Bigger Area:
 - 2 delay lines instead of one
 - Bigger delay cells due to more stringent mismatch requirements
- Longer Conversion Time (dependent on time interval being measured)
- Higher Power Consumption

Regular VS Vernier Delay Line (3/3)


Regular (Tapped) Delay Line:

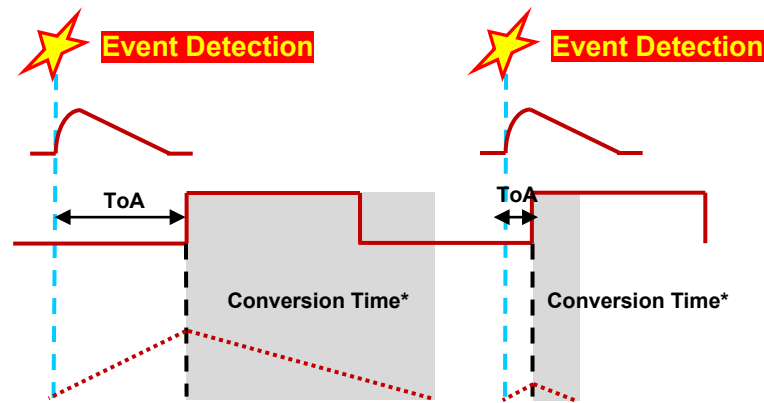

*Similar to Dual-Slope ADC

- Simpler
- Resolution (LSB) limited by technology
- Smaller Area
- Shorter Conversion Time (independent on time interval being measured)
- Lower Power Consumption


Vernier Delay Line:

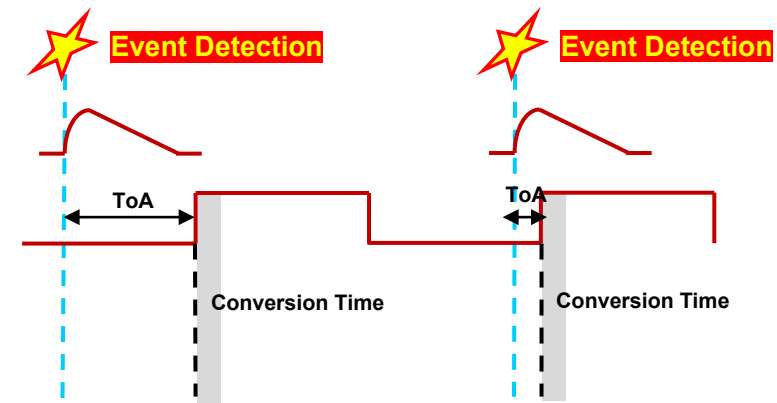


VS

- More complex
- Resolution (LSB) not limited by technology
- Bigger Area:
 - 2 delay lines instead of one
 - Bigger delay cells due to more stringent mismatch requirements
- Longer Conversion Time (dependent on time interval being measured)
- Higher Power Consumption

Examples of different TDC architectures:

 

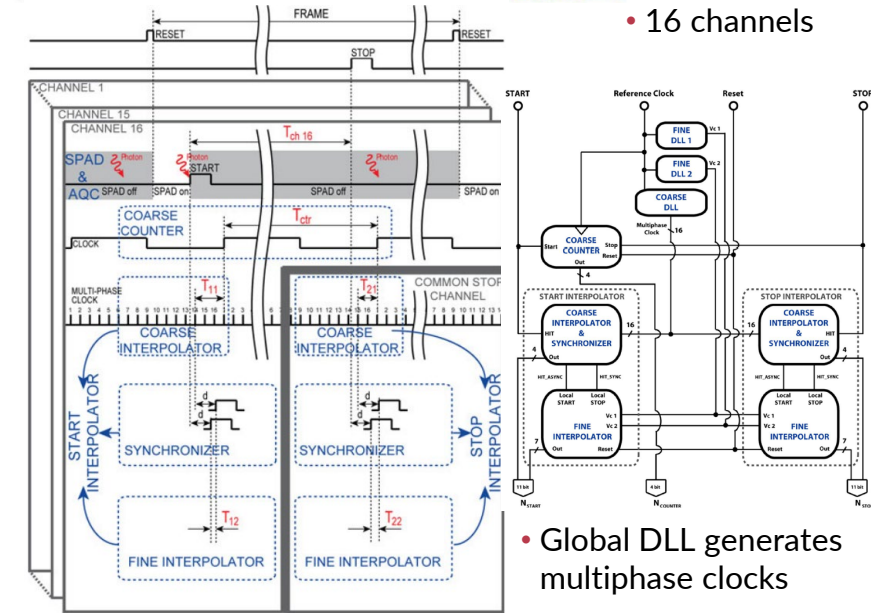
- 350nm CMOS
- Resolution: 10ps
- Range: 160ns
- 16 channels




- Global DLL generates multiphase clocks

- 'Coarse' Counter, multiphase clock sampling (1st interpolation stage) and Cyclic Vernier DI (2nd interpolation stage) per channel
- 2 additional global DLLs for Vernier stage biasing

 D. Tamborini, B. Markovic, F. Villa and A. Tosi, "16-Channel Module Based on a Monolithic Array of Single-Photon Detectors and 10-ps Time-to-Digital Converters," in *IEEE Journal of Selected Topics in Quantum Electronics*, vol. 20, no. 6, pp. 218-225, Nov.-Dec. 2014, Art no. 3802908, doi: 10.1109/JSTQE.2014.2327797.




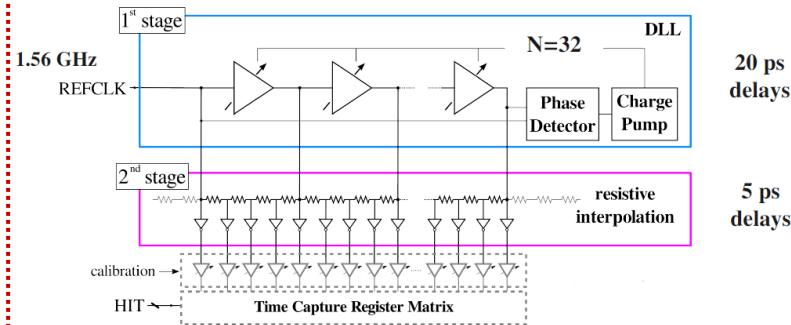- 130nm CMOS
- Resolution: 5ps
- Range: 640ps
- 8 channels



- Global DLL with resistive interpolation generates multiphase clocks
- Multiphase clock sampling per channel

 
L. Perktold and J. Christiansen, "A fine time-resolution ($\ll 3$ ps-rms) time-to-digital converter for highly integrated designs," 2013 *IEEE International Instrumentation and Measurement Technology Conference (I2MTC)*, 2013, pp. 1092-1097, doi: 10.1109/I2MTC.2013.6555583



- 130nm CMOS
- Resolution: 20ps (TOA), 40ps/160ps (TOT)
- Range: 2.5ns TOA, 20n TOT
- 5x5=25 channels (altiroc1)
- 15x15=225 channels (altiroc2)

TOA TDC:


- Cyclic Vernier Delay Line

 

- TOA and TOT TDCs inside each pixel
- 3 Global DLLs

TOT TDC:

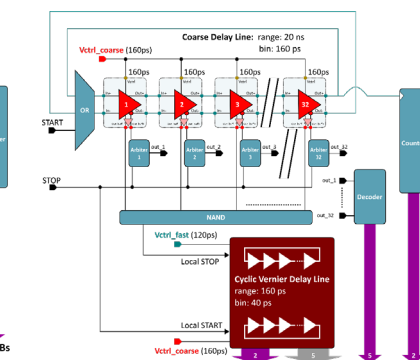- Cyclic Delay Line with Vernier Delay Line interpolation



B. Markovic *et al.*, "ALTIROC1, a 20 ps time-resolution ASIC prototype for the ATLAS High Granularity Timing Detector (HGTD)," 2018 *IEEE Nuclear Science Symposium and Medical Imaging Conference Proceedings (NSS/MIC)*, 2018, pp. 1-3, doi: 10.1109/NSSMIC.2018.8824723

Some design considerations

□ Simpler is better

- Alignment between interpolation stages is not trivial and must be done with the precision of the final resolution.
 - Stacking multiple interpolation stages one after the other allows for reduced area, power consumption and conversion time, but must be done with care (1 or 2 interpolation stages are usually enough; more than 3 is extremely tricky).
- With technology scaling routing/parasitic contributions to propagation delay are becoming more and more pronounced
 - Routing of timing critical signals must be done with care
 - For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances

▪ Perfectly aligned 'Coarse' and 'Fine' Stages:





▪ Effect of offset in the connection between 'Coarse' and 'Fine' stages:




Some design considerations

- Simpler is better
 - Alignment between interpolation stages is not trivial and must be done with the precision of the final resolution.
 - Stacking multiple interpolation stages one after the other allows for reduced area, power consumption and conversion time, but must be done with care (1 or 2 interpolation stages are usually enough; more than 3 is extremely tricky).
- With technology scaling routing/parasitic contributions to propagation delay are becoming more and more pronounced
- Routing of timing critical signals must be done with care
- For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances


□ Layout:

  

 - Transistor Active Area (Diffusion)
- Transistor Gate (Polysilicon)
- Contact (Poly/Diff to M1)
- Metal 1
- Via 1 (M1 to M2 connection)
- Metal 2




□ Schematic:

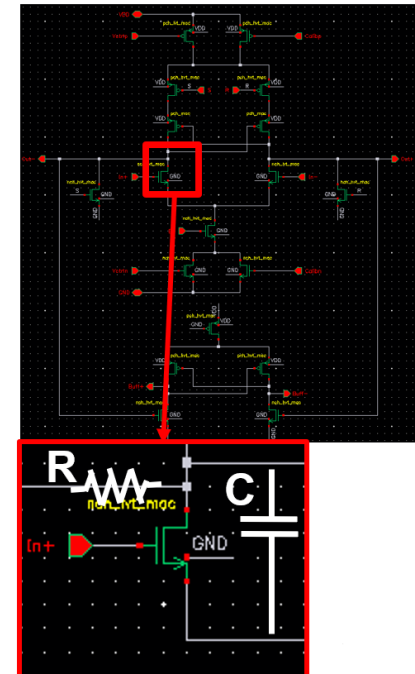


Some design considerations

- ❑ Simpler is better
 - Alignment between interpolation stages is not trivial and must be done with the precision of the final resolution.
 - Stacking multiple interpolation stages one after the other allows for reduced area, power consumption and conversion time, but must be done with care (1 or 2 interpolation stages are usually enough; more than 3 is extremely tricky).
- ❑ With technology scaling routing/parasitic contributions to propagation delay are becoming more and more pronounced
- ❑ Routing of timing critical signals must be done with care
- ❑ For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances

130nm CMOS Delay Cell (SCH):

 


130nm CMOS Delay Cell (RCX):

 

~25% propagation delay increase due to parasitic

28nm CMOS Delay Cell (RCX):

28nm CMOS Delay Cell (SCH):

 


>125% propagation delay increase due to parasitic

Some design considerations

□ Simpler is better

 
- Alignment between interpolation stages is not trivial and must be done with the precision of the final resolution.
- Stacking multiple interpolation stages one after the other allows for reduced area, power consumption and conversion time, but must be done with care (1 or 2 interpolation stages are usually enough; more than 3 is extremely tricky).



□ With technology scaling routing/parasitic contributions to propagation delay are becoming more and more pronounced

□ Routing of timing critical signals must be done with care

 □ For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances



Some design considerations

□ Simpler is better

- Alignment between interpolation stages is not trivial and must be done with the precision of the final resolution.
- Stacking multiple interpolation stages one after the other allows for reduced area, power consumption and conversion time, but must be done with care (1 or 2 interpolation stages are usually enough; more than 3 is extremely tricky).


□ With technology scaling routing/parasitic contributions to propagation delay are becoming more and more pronounced

□ Routing of timing critical signals must be done with care


□ For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances

▪ Statistical Mismatches:

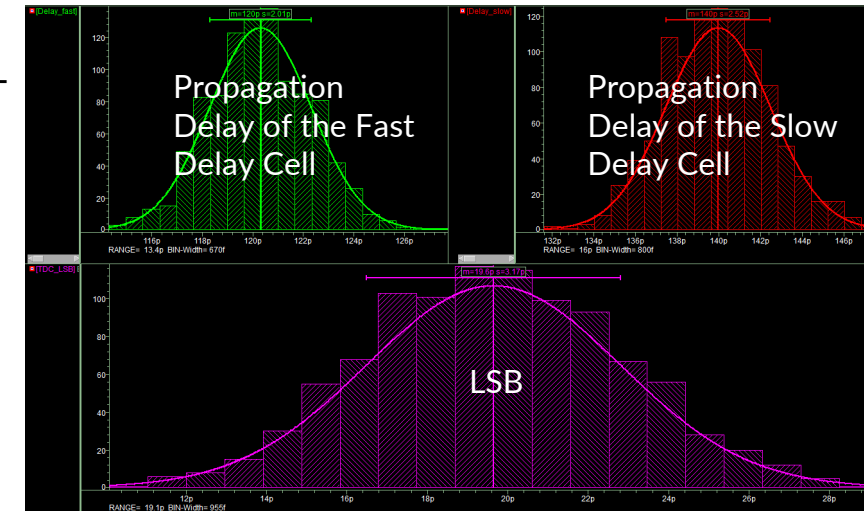- Altiroc Delay Cell Mismatches – Monte-Carlo simulations:



 
- Altiroc measured LSB dispersion per channel:



Some design considerations

- **Altiroc TOT TDC Characterization:**



 
The discontinuity always appears for the same width value and is attributed to a discontinuity of the programmable width generation on the FPGA board



❑ For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances

- **Systematic Mismatches:**


- **Altiroc TOT TDC:**

   

Systematic mismatch shown in parasitic extracted simulation




Some design considerations

- Altiroc TOA TDC Characterization:

 

- Systematic Mismatches:

- Altiroc TOA TDC:

  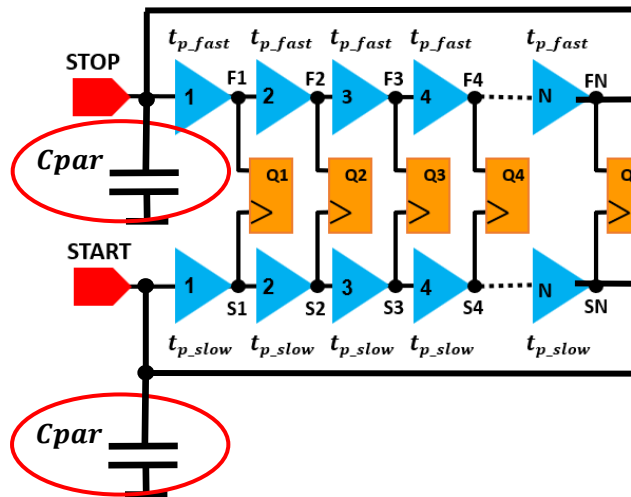


For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances

Some design considerations

- Simpler is better
 - Alignment between interpolation stages is not trivial and must be done with the precision of the final resolution.
 - Stacking multiple interpolation stages one after the other allows for reduced area, power consumption and conversion time, but must be done with care (1 or 2 interpolation stages are usually enough; more than 3 is extremely tricky).
- With technology scaling routing/parasitic contributions to propagation delay are becoming more and more pronounced
- Routing of timing critical signals must be done with care
- For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances


Systematic Mismatches:

 

 B. Markovic, S. Tisa, F. A. Villa, A. Tosi and F. Zappa, "A High-Linearity, 17 ps Precision Time-to-Digital Converter Based on a Single-Stage Vernier Delay Loop Fine Interpolation," in *IEEE Transactions on Circuits and Systems I: Regular Papers*, vol. 60, no. 3, pp. 557-569, March 2013, doi: 10.1109/TCSI.2012.2215737.

START Channel orientation same as bias DLLs

STOP Channel orientation vertically mirrored compared to bias DLLs



Not all systematic mismatches always show in parasitic extracted simulations

Some design considerations

□ Simpler is better


- Alignment between interpolation stages is not trivial and must be done with the precision of the final resolution.
- Stacking multiple interpolation stages one after the other allows for reduced area, power consumption and conversion time, but must be done with care (1 or 2 interpolation stages are usually enough; more than 3 is extremely tricky).

□ With technology scaling routing/parasitic contributions to propagation delay are becoming more and more pronounced

□ Routing of timing critical signals must be done with care


□ For ps-level designs device mismatches (both systematic and statistical) can have major impact on the performances

▪ Systematic Mismatches:

 


- Good layout practice for matching sensitive circuits:

 - Keep gates with the same orientation
- Use even number of fingers per transistor



 
Linearity Improvement: Sliding Scale Technique




[1] C. Cottini, E. Gatti, and V. Svelto, "A new method for analog to digital conversion," Nucl. Instr. Meth., vol. 24, p. 241, Aug. 1963.
 [2] E. Gatti, P. F. Manfredi, and D. Marino, "Analysis and characterization of cyclic-scale compensated analog-to-digital converters," Nucl. Instrum. Methods, vol. 165, no. 2, pp. 225–230, Oct. 1979.

Regular Converter:


Measurement1:

 


Measurement2:

 

Measurement3:

 

Sliding Scale [1][2] / Dithering

 


Result = Tmeas - Tadd

Result = 5 - 0 = 5




Result = 7 - 2 = 5

 


Result = 6 - 1 = 5

Linearity Improvement


- ❑ TDC with scrambling/dithering logic:

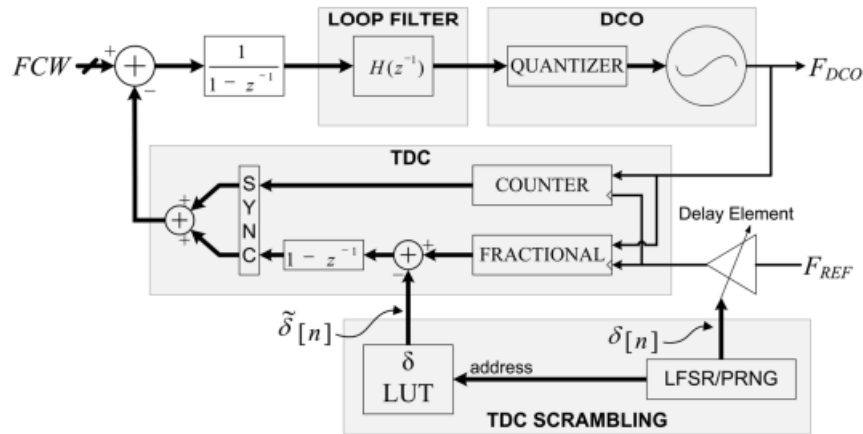

 
- ❑ Wave Union TDC (often used in FPGA implementations to overcome large bin sizes):



 
- ❑ Stochastic TDC (exploits mismatch and jitter to perform dithering):



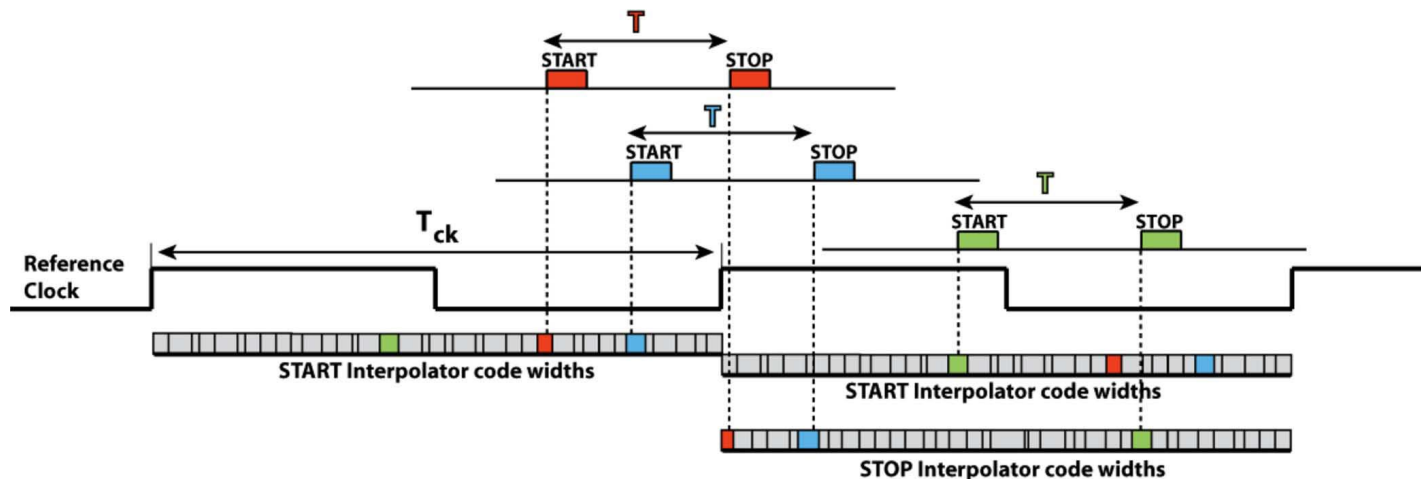- ❑ Asynchronous START and STOP signals (requires 2 interpolators):




 HEP timing ASIC example: Altiroc ASIC for ATLAS HGTD




High-Granularity Timing Detector (HGTD) for ATLAS Phase II

 - High-Luminosity Large Hadron Collider (HL-LHC) beginning in 2026
- on average 200 interaction per bunch crossing ➔ Pile-up challenge
- High-Granularity Timing Detector (HGTD) for pile-up mitigation



- Placed in the **forward region**, between the **Inner Tracker** and the **endcap of EM Calorimeter**
- **2 disks, 2 layers/disk** containing **modules with sensors** and on-detector **electronics**
- Time resolution: **30 ps**
- Granularity ($< 10\%$ Occupancy): **1.3 x 1.3 mm²**
- **50 μ m thick Low Gain Avalanche Diodes (LGAD)** n-on-p Si detectors

HGTD electronics: general architecture

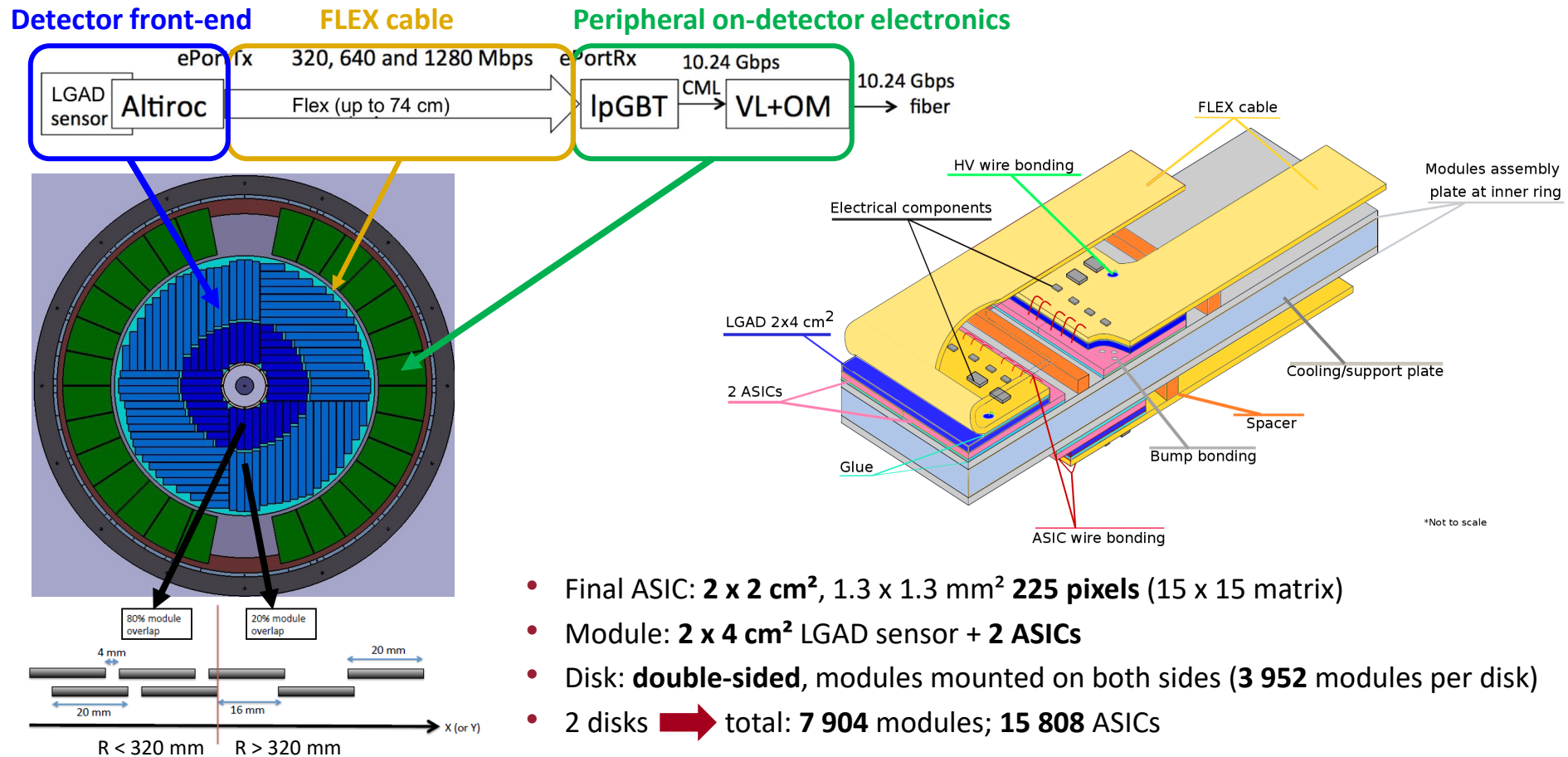

- Final ASIC: **2 x 2 cm²**, 1.3 x 1.3 mm² **225 pixels** (15 x 15 matrix)
- Module: **2 x 4 cm²** LGAD sensor + **2 ASICs**
- Disk: **double-sided**, modules mounted on both sides (**3 952 modules per disk**)
- 2 disks ➔ total: **7 904 modules; 15 808 ASICs**

ASIC requirements

- **ALTIROC (ATLAS LGAD Timing Read-Out Circuit) – Front-End ASIC for LGAD sensor readout and time-measurement** of each hit of events selected by L0/L1 trigger with a resolution smaller than **30 ps/MIP**

Key requirement: Time resolution per track, combining multiple hits, is 30 ps at the start of lifetime to 50 ps after 4000 fb⁻¹ => Time resolution /hit must be < 35 ps at start and 70 ps at the end of lifetime.

Maximum jitter (σ_{elec})	25 ps at 10 fC at the start of the HL-LHC and 70 ps for 4 fC at the end
TDC contribution	< 10 ps
Time walk contribution	< 10 ps
Clock contribution	< 15 ps

TDC conversion time	< 25 ns
---------------------	---------

Clock phase adjustment	100 ps
------------------------	--------

PAD size	1.3 x 1.3 mm ² x 50 μ m => Cdet = 4 pF
ASIC size and channels /ASIC	2x2 cm ² 15x15=225 channels/ASIC
Single PAD noise (ENC)	< 3000 e- or 0.5 fC
Minimum threshold	2 fC
Dynamic range	4 fC to 50 fC

TID Tolerance	2 MGy (inner modules replaced after each 1000 fb ⁻¹ , middle ring after 2000 fb ⁻¹)
Full chip SEU probability	< 5 % / hour

Trigger rate (latency)	1 MHz L0 (10 μ s) or 0,8 MHz L1 (35 μ s)
------------------------	--


e-link driver bandwidth	320 Mbit/s, 640 Mbit/s and 1,28 Gbit/s
-------------------------	--

Voltage and Power dissipation per ASIC	1.2V and 300 mW cm ⁻² => 1.2 W/ASIC (225 ch) or 4.4 mW/channel and 200 mW for the common part
--	--

Main contributors to time resolution

$$\sigma_{hit}^2 = \sigma_{Landau}^2 + \sigma_{clock}^2 + \sigma_{elec}^2$$


 
with $\sigma_{elec}^2 = \sigma_{Time\ walk}^2 + \sigma_{jitter}^2 + \sigma_{TDC}^2$




ASIC designed in CMOS 130 nm

ALTIROC1 architecture

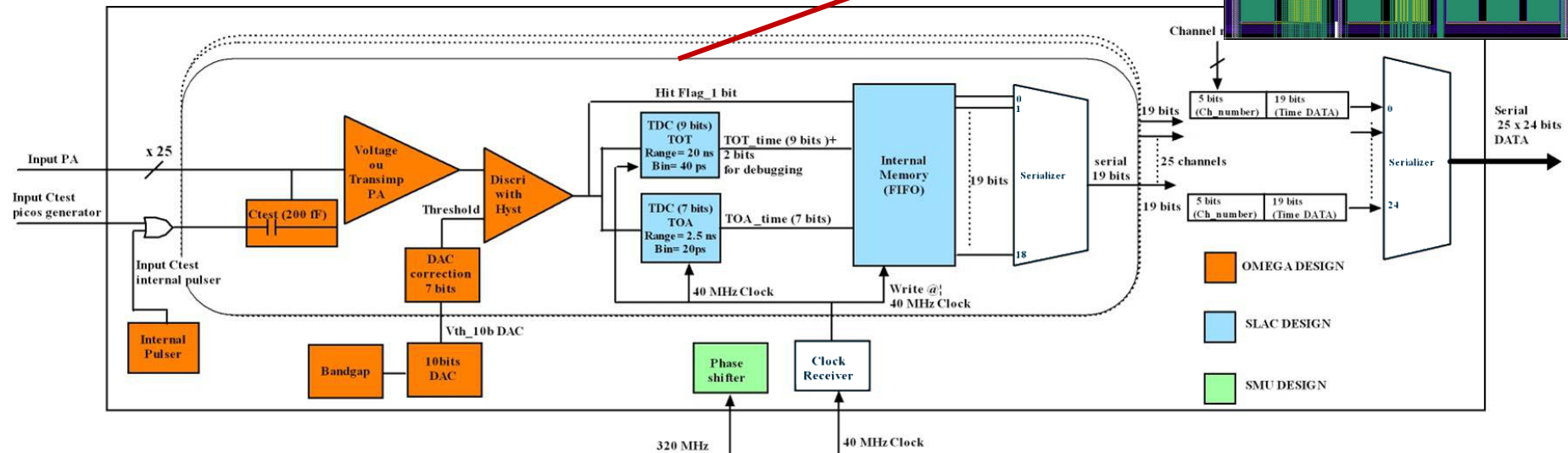 - **ALTIROC1** = Second ALTIROC ASIC prototype with **25 complete FE channels** to readout **5 x 5** sensor cells of **1.3 mm x 1.3 mm** (6.5 mm x 6.5 mm) + **Phase shifter**
- 3 Labs involved: **OMEGA (analog Part & Full-chip Integration)**, **SLAC (Digital part: TDCs, DLLs & FIFO)**, **SMU (Phase shifter)**
- ASIC size: **7 x 7.5 mm²**, fabricated in **TSMC 0.13 μm CMOS** technology



ALTIROC2 architecture

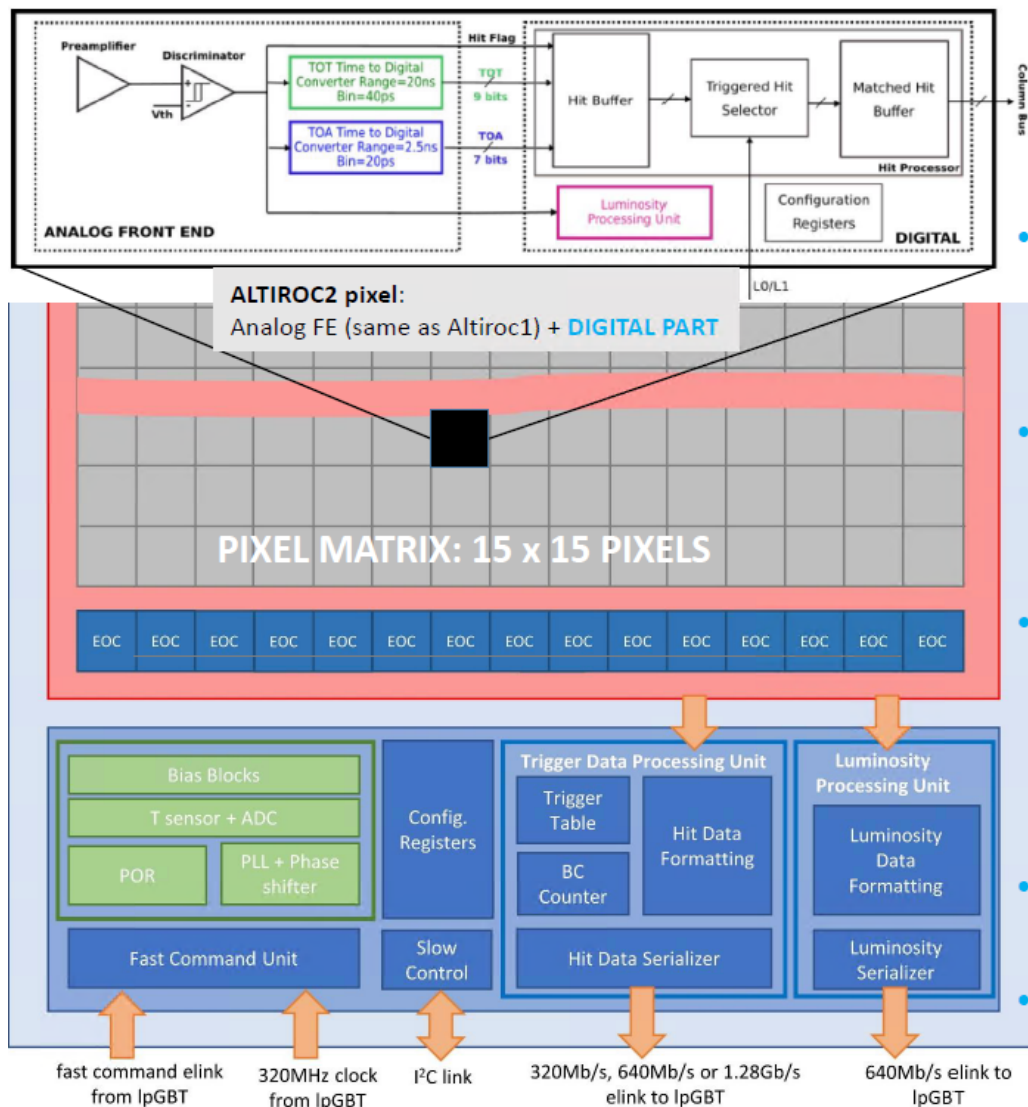


ALTIROC2 (225 ch): Pixel digital part


- **Hit buffer:** SRAM 1536 x 19 bits
 - Circular buffer to store timing data for each BC, until a trigger arrives
 - Data= Hit and TOT and TOA bits, only in case of hit to save power
 - Control unit to handle R/W pointers
- **Trigger Hit Selector =**
 - Each received trigger associated to a trigger tag
 - If data stored in Hit buffer related to received trigger, TOA/TOT data + trig tag stored into Matched Hit Buffer
- **Matched Hit Buffer:** 32 positions FIFO
 - Control Unit: looks for data related to a trigger event when requested by the End Of Column
 - Matched flag handled through a priority OR chain. Pixel at the top of the column with highest priority
 - Synchronous readout at 40 MHz
- **Luminosity process unit**
 - checks if hits are within 2 programmable windows
- **I2C configuration registers**

All these digital blocks are integrated in Altipix prototype, first tests in July 2020

TOA TDC



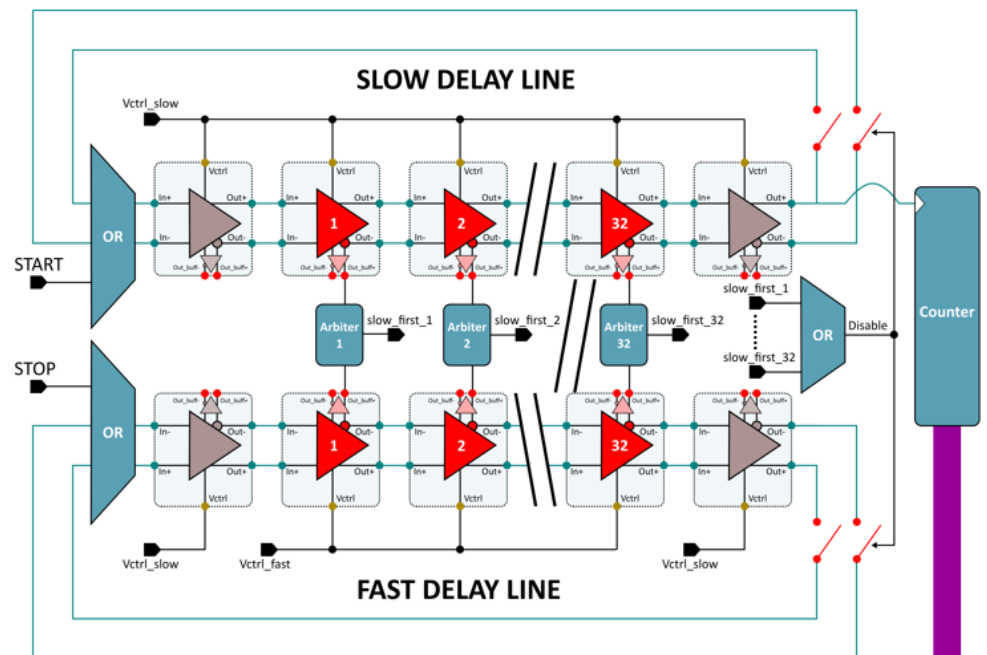


 - Cycling configuration used in order to reduce the total number of Delay Cells.
- Resolution: 20ps
- Range: 2.5ns
- 7 bits



TOT TDC

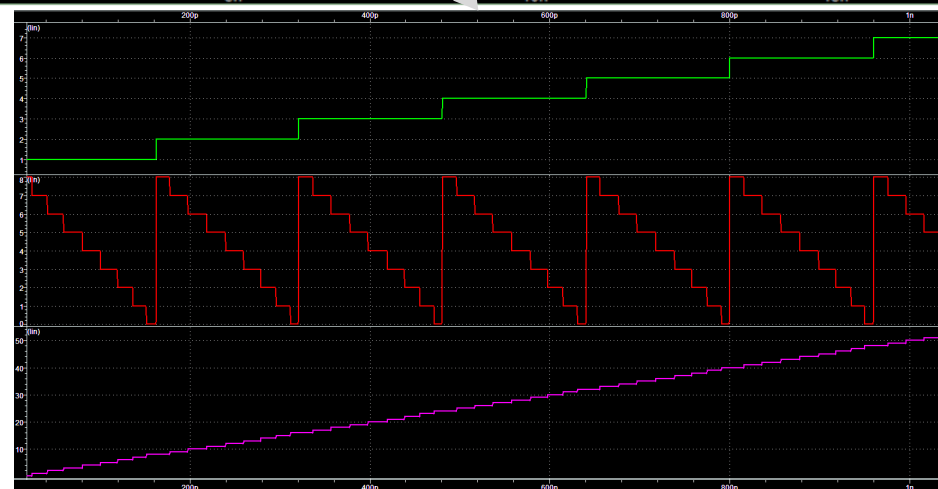
 
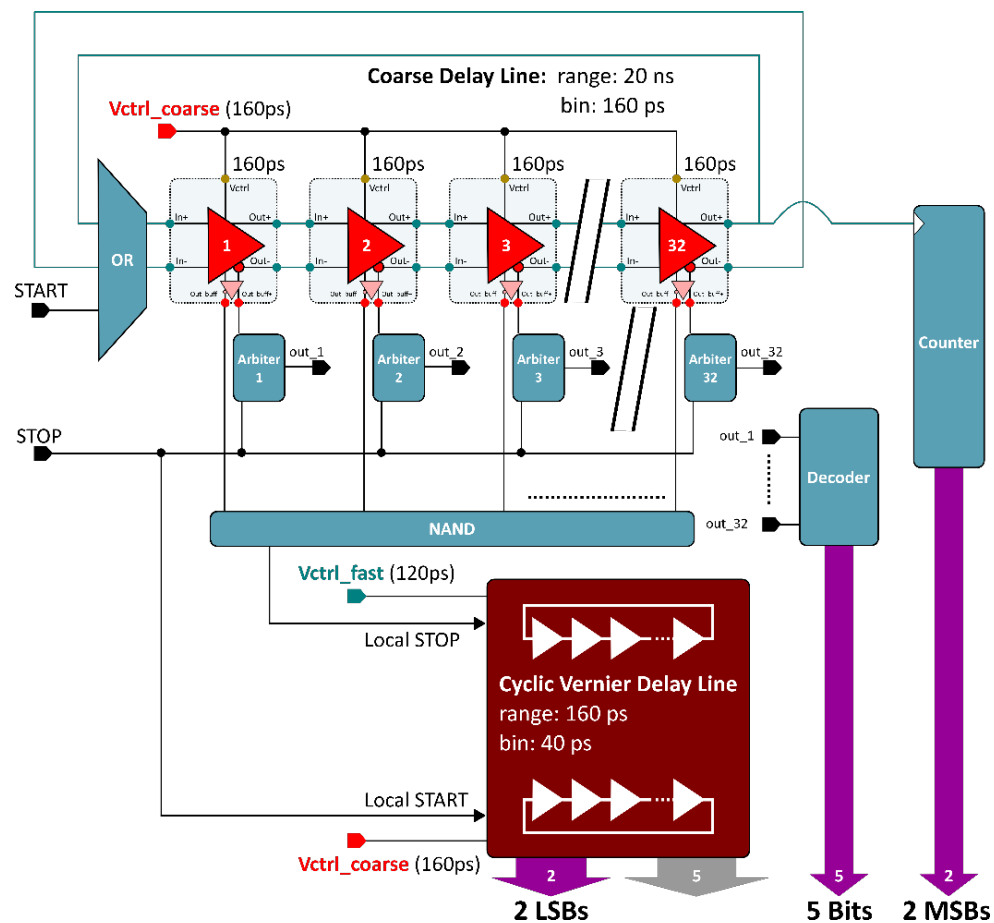
- Delay Line with Vernier Delay Line Interpolation




Altiroc1 Testbench (1/2)

TESTBENCH





- ALTIROC1_V1, ALTIROC1_V2: testbench measurements (ASIC alone or with sensor), irradiation tests, testbeam
- Setup: ASIC board (ASIC alone or bump bonded onto sensor) + FPGA board
- Charge injection (0 up to 50 fC) using ASIC **internal calibration pulser** controlled by `cmd_pulse` input, generated by the FPGA, synchronous to 40 MHz clock
- ASIC alone: $C_d=4$ pF can be set by SC to mimic sensor capacitor
- **External trigger**, width and delay tunable by 10 ps steps : used to characterize the TOA and TOT TDC alone
- **Tests at system level:** need to add **interface board to filter FPGA signals (3 MHz noise DC DC converters)** => V_{th} could be set $< 2fC$

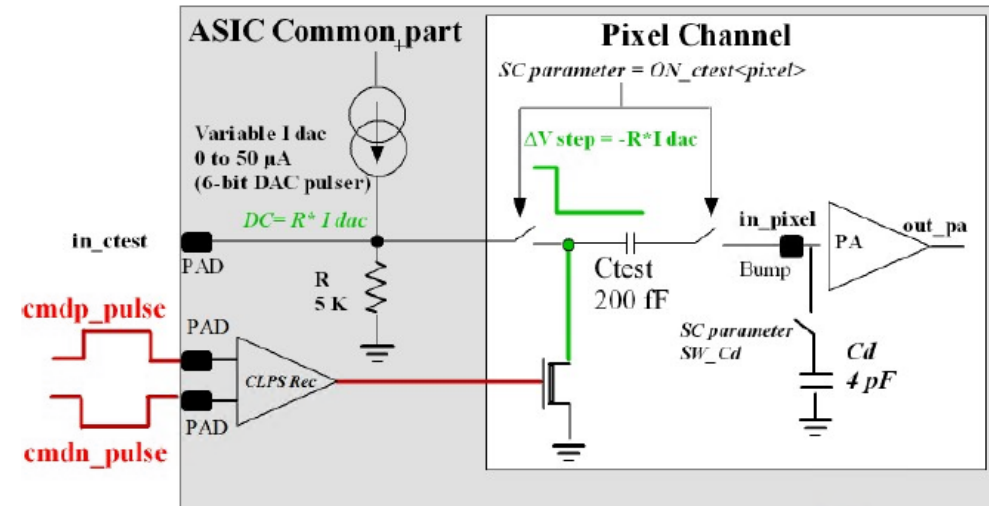  


Altiroc1 Testbench (2/2)

 



Altiroc1 Characterization (1/4)

    


Altiroc1 Characterization (2/4)

 



Altiroc1_V2: TOT vs Qinj

 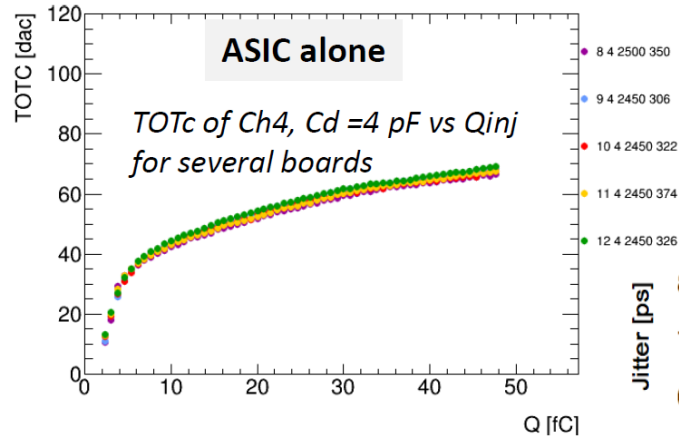


Altiroc1_V2: TOA vs delay

 

  Altiroc1_V3: Jitter vs channel (ASIC alone)





 Altiroc1_V3: Jitter vs channel (ASIC + sensor)



Altiroc1 Characterization (3/4)

Altiroc1_V2: TEST BEAM measurement

 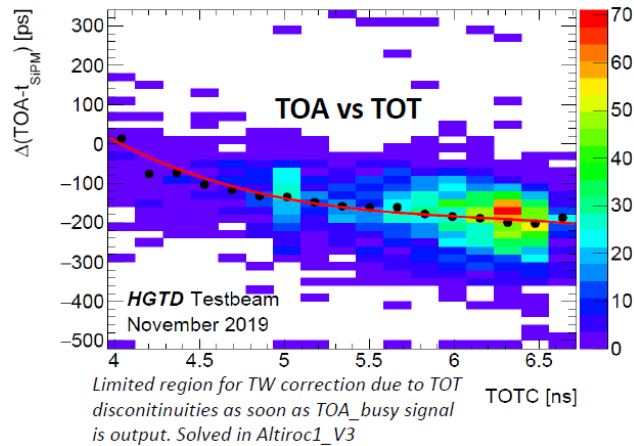


Time resolution = 46 ps \Rightarrow electronics jitter 39 ps after subtracting Landau fluctuations (25 ps) $\sigma_{hit}^2 = \sigma_{Landau}^2 + \sigma_{clock}^2 + \sigma_{elec}^2$
 New interface boards designed after this TB \Rightarrow jitter should be reduced by 35 % and so electronic jitter contribution should be 26 ps in testbeam (36 ps for time resolution)

Altiroc1 Characterization (4/4)


Irradiations tests with Altiroc1_V1 (June 28- July 8, 2019)

CERN facility, TID up to 340 Mrad, requirement: 200 Mrad max

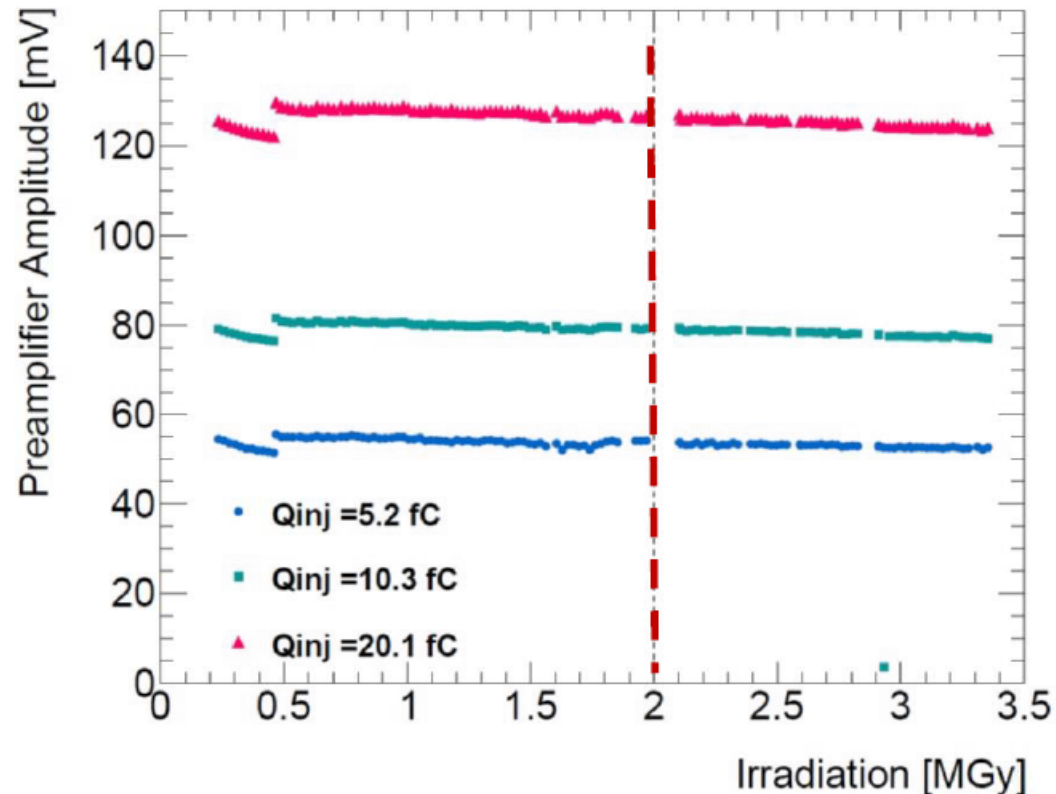Preamp amplitude for various input charges



 
Jitter measurement on scope (not measured with TDC)



Conclusion

- ❑ Many different architecture and methods for time-to-digital conversion exist.
- ❑ Counters are usually employed together with 'fine' measurement techniques to achieve long ranges together with ps-level resolution.
- ❑ 'Fine' measurement techniques include:
 - Analog techniques (TAC+ADC; Dual-Slope Pulse Stretching + Counter)
 - Pulse Shrinking
 - Time Amplifiers (SR latch based or Cross-Coupled Delay Line)
 - Delay Line / Multiphase Clocks
 - Delay Interpolation: resistive divider, multipath cells
 - Vernier Delay Lines (cyclic, ring oscillator, 2D, 3D)
 - Linearity improvement: sliding scale, wave union, stochastic
- ❑ Delay Elements are usually implemented as Voltage-Controlled Delay Cells (Current-Starved or Shunt-Capacitor) and their delay is stabilized against PVT variations using DLLs or PLLs
- ❑ Interfaces between interpolation stages, signal routing, effects of mismatches are critical at ps resolution levels
- ❑ TDCs are part of a bigger (HEP) system; performances at the system level are what counts!

Thank you for your *TIME!*

 

TOM GAULD for NEW SCIENTIST