



**BERKELEY LAB**

Bringing Science Solutions to the World



U.S. DEPARTMENT OF  
**ENERGY**

Office of Science

# Introduction to Analog-to-Digital Converters

HEPIC Summer School

Carl Grace 6/21/2023

**Lawrence Berkeley National Laboratory**



# Lawrence Berkeley National Laboratory

## MOST DIVERSE US NATIONAL LABORATORY

### Key Strengths

Physical Sciences, Computing,  
Biosciences, Earth and Energy  
Sciences, Materials, and  
Nanotechnology




## EXCELLENCE & DIVERSITY

3500 employees  
1000 students  
1750 visiting researchers
 
## NATIONAL USER FACILITIES

- Advanced Light Source
- National Energy Research Scientific Computing Center
- Energy Sciences Network
- Joint Genome Institute
- Molecular Foundry (including National Center for Electron Microscopy)




## 14 NOBEL PRIZES


Most recent: 2020 Nobel Prize in  
Chemistry for co-discovery of  
CRISPR gene editing (Prof. Jennifer  
Doudna)
 
# Fun Fact

LBNL may be the only workplace where you can **write your address in elements!**



 All discovered by LBNL along with 12 other elements!



Plutonium discovered in 1940 at LBNL

Radiation hazard trefoil invented in 1946 at LBNL





 
# Agenda

- ADC Overview
- ADC Specifications
- ADC Architectures
- ADCs for High-Energy Physics
- Design Study: Oversampling ADC


Focus will be on ADC architectures relevant to HEP



# ADC Overview




# What are ADCs?

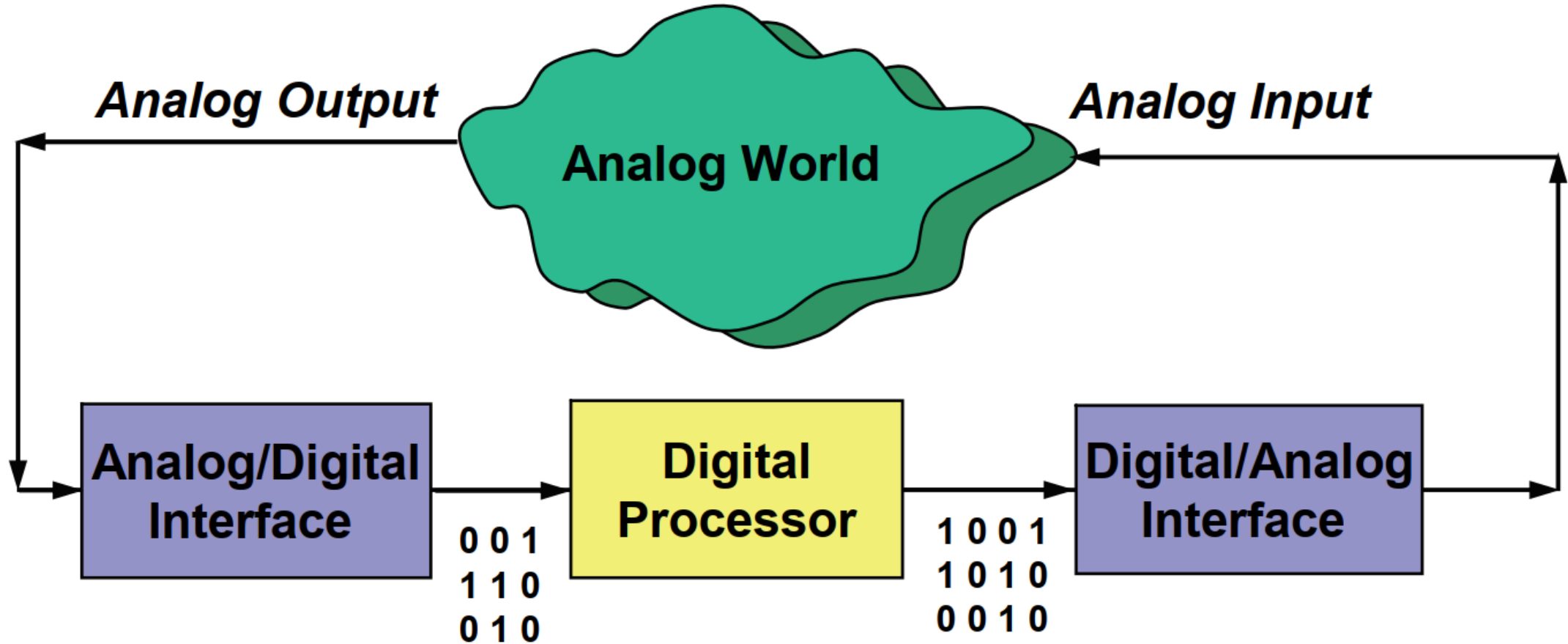

Analog-to-Digital Converters (ADCs) provide the link between the analog world and digital processing

In HEP, detector outputs are usually analog (e.g. charge pulses) and ADCs pace experimental improvements

# ADC Applications

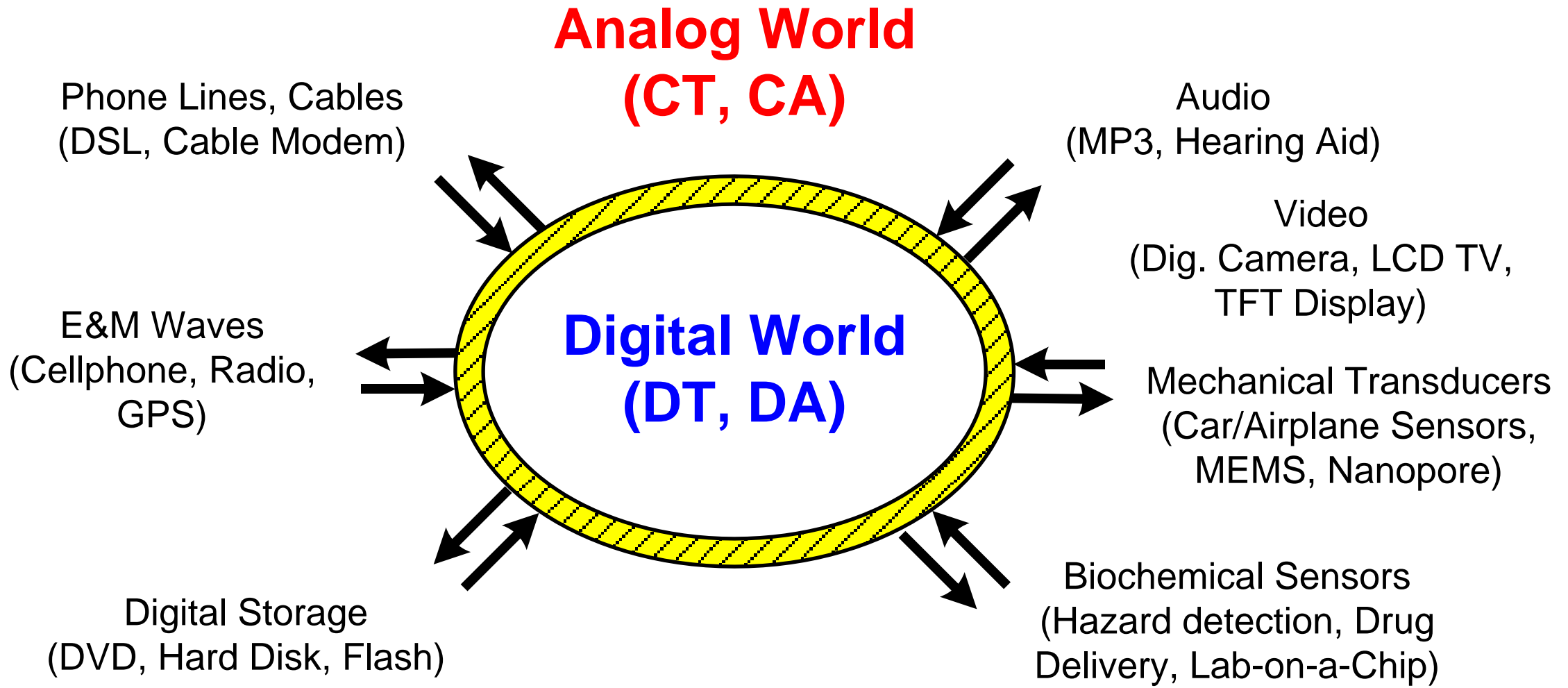


Paul Gray (UCB)

# ADC Applications

Resolution:  $\log_2$  of quantization levels

Sampling Rate: number of conversions/sec

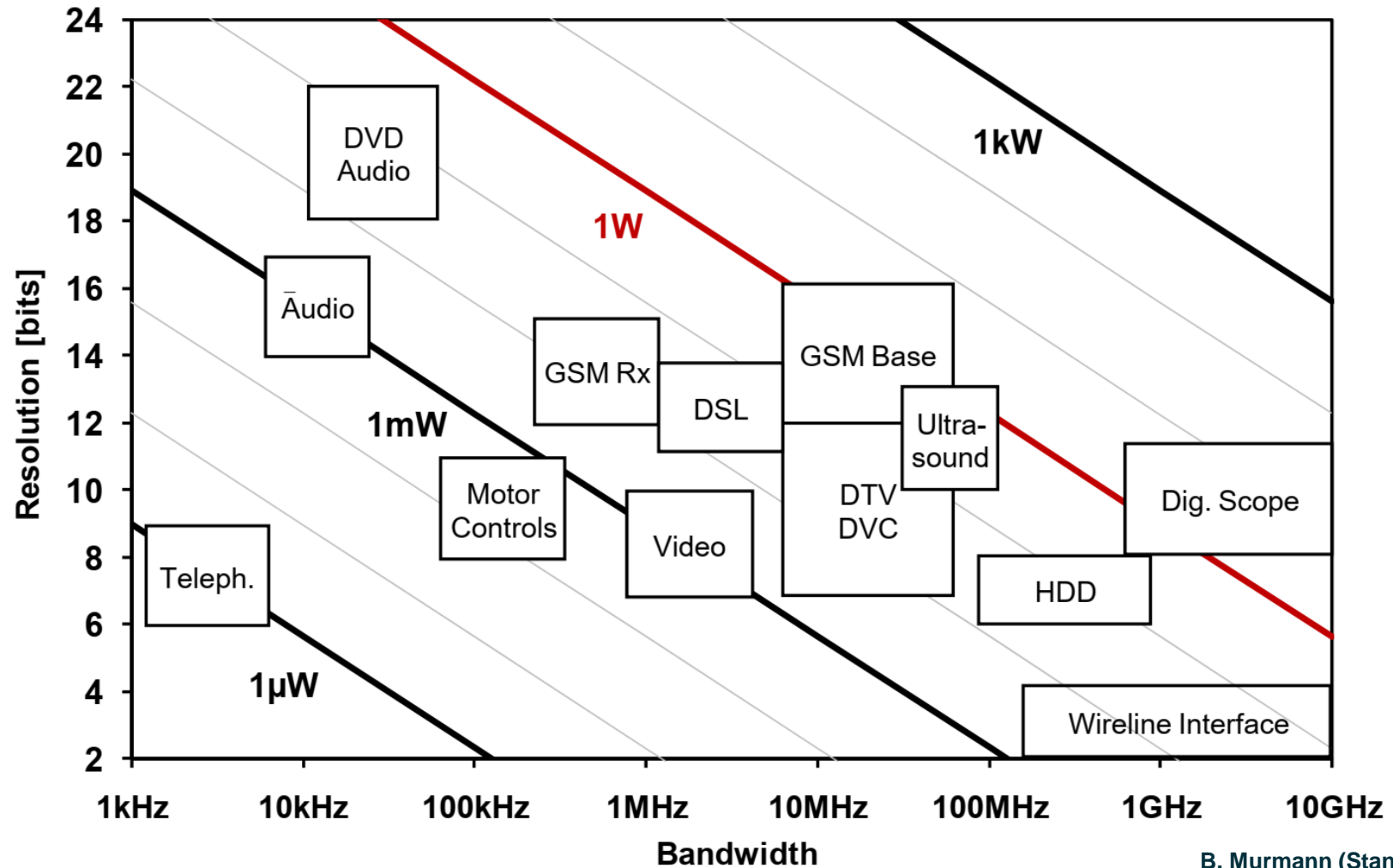Bandwidth: Sampling Rate / 2 (stay tuned!)




B. Murmann (Stanford)


Huge application space → many complementary ADC techniques


 
# ADC Applications (cellular phone example)



Ericsson CH388  
(Hybrid, 1995)

 


Past

Berkana GSM/GPRS Ericsson Bluetooth  
(CMOS, 2005)

Present



Future

 

CMOS? or  
something else?




Y. Chui (UTD)
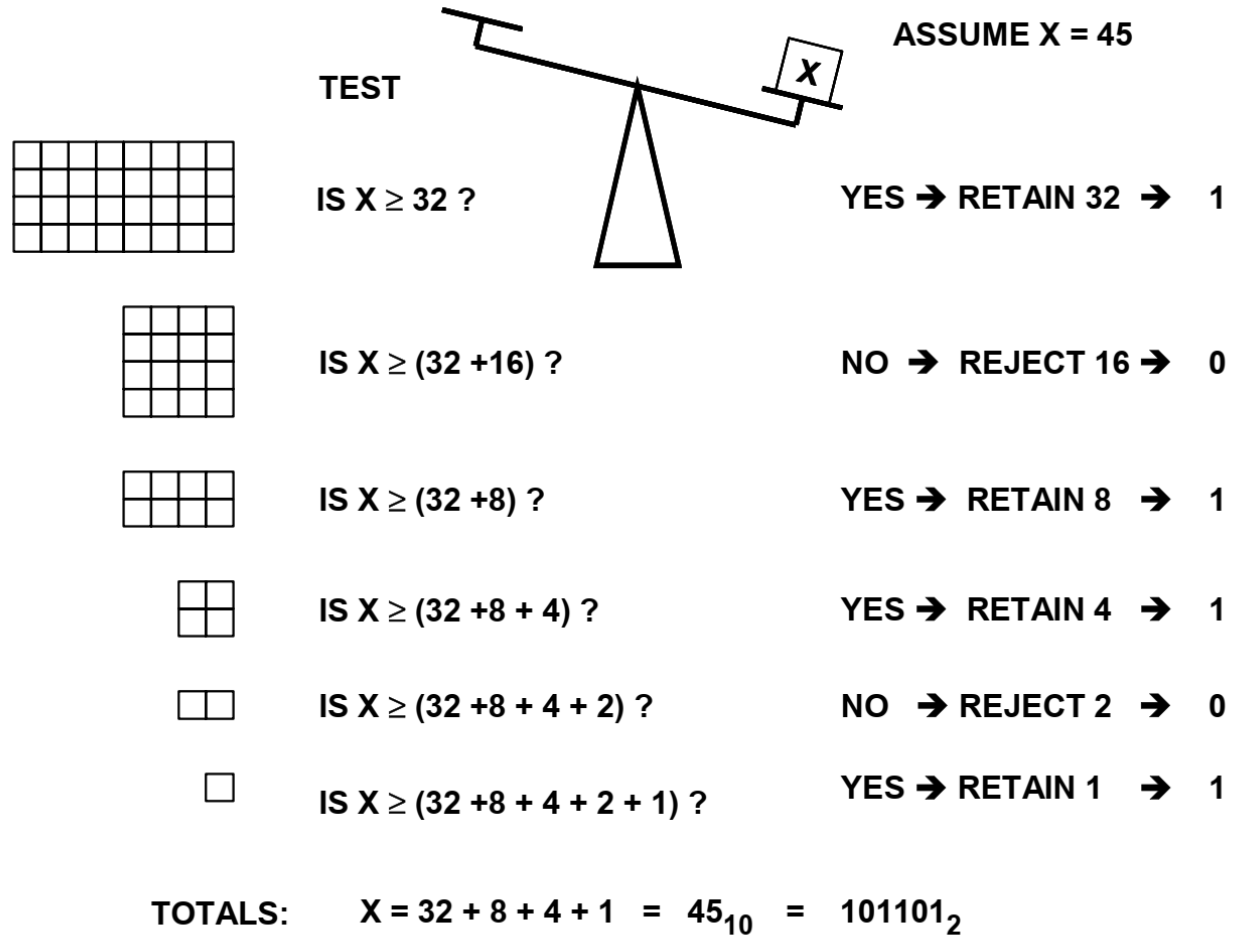
# What exactly is Analog-to-Digital Conversion?


Analog-to-Digital conversion is essentially a ruler that can be used to measure an unknown quantity to some level of accuracy

This is an ancient algorithm to determine weights (for example in a metal assay). Today this algorithm is called Successive Approximation (and the leading ADC technique uses this algorithm still).



Analog Devices

# Steps of Analog-to-Digital Conversion

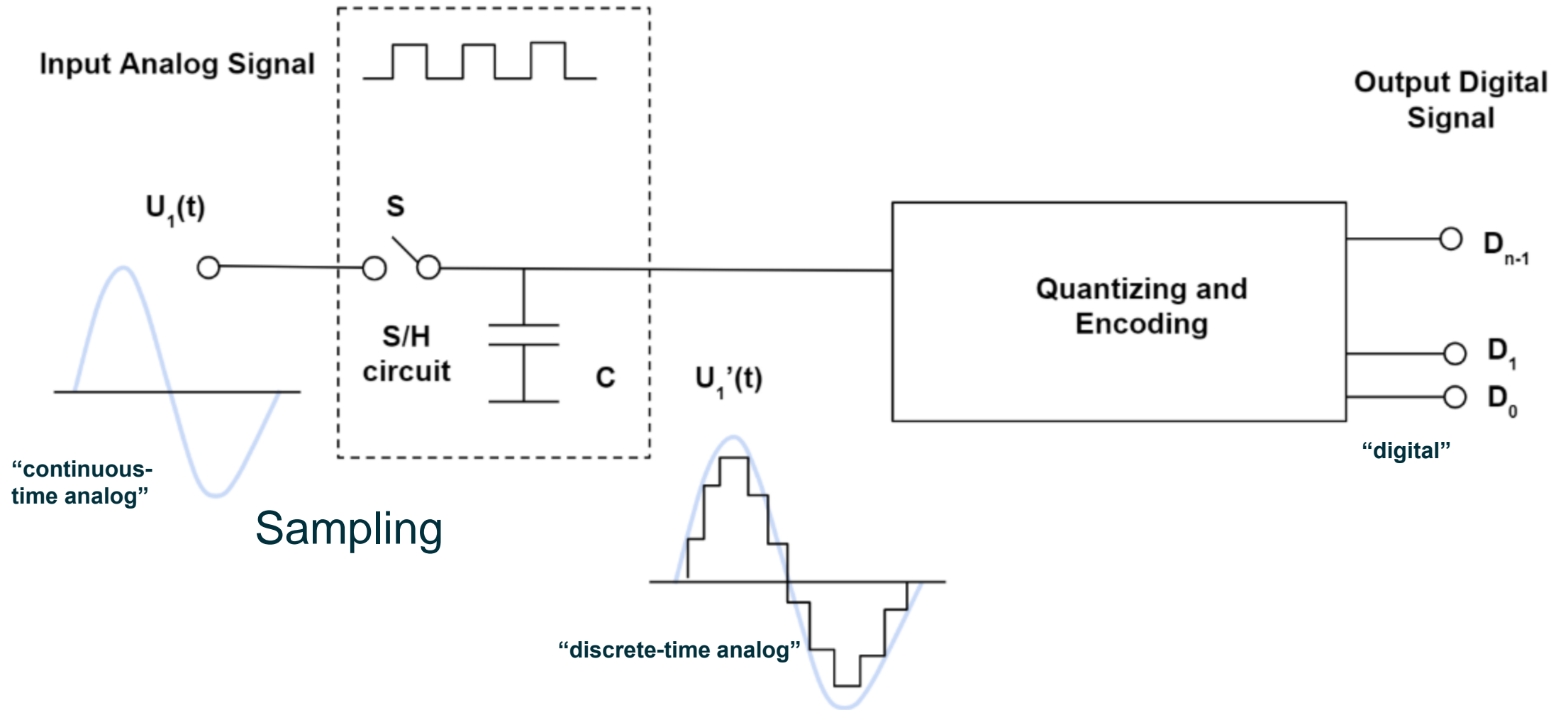


# Sampling & Aliasing

How fast do you need to sample?

Shannon-Nyquist Theorem:

If a system uniformly samples an analog signal at a rate that exceeds the signal's highest frequency by at least a factor of two, the original analog signal can be perfectly recovered from the discrete values produced by sampling.

## Aliasing

 




No aliasing if  $f_{\text{sample}} > 2 f_{\text{max}}$   
where  $f_{\text{max}}$  is the maximum  
frequency in your input signal.

Did you sample the **red**  
curve? Or the **blue** curve?



   
# Sampling & Aliasing

$$Y(\omega) = \frac{1}{T_S} \sum_{-\infty}^{\infty} X(\omega - n\omega_s)$$



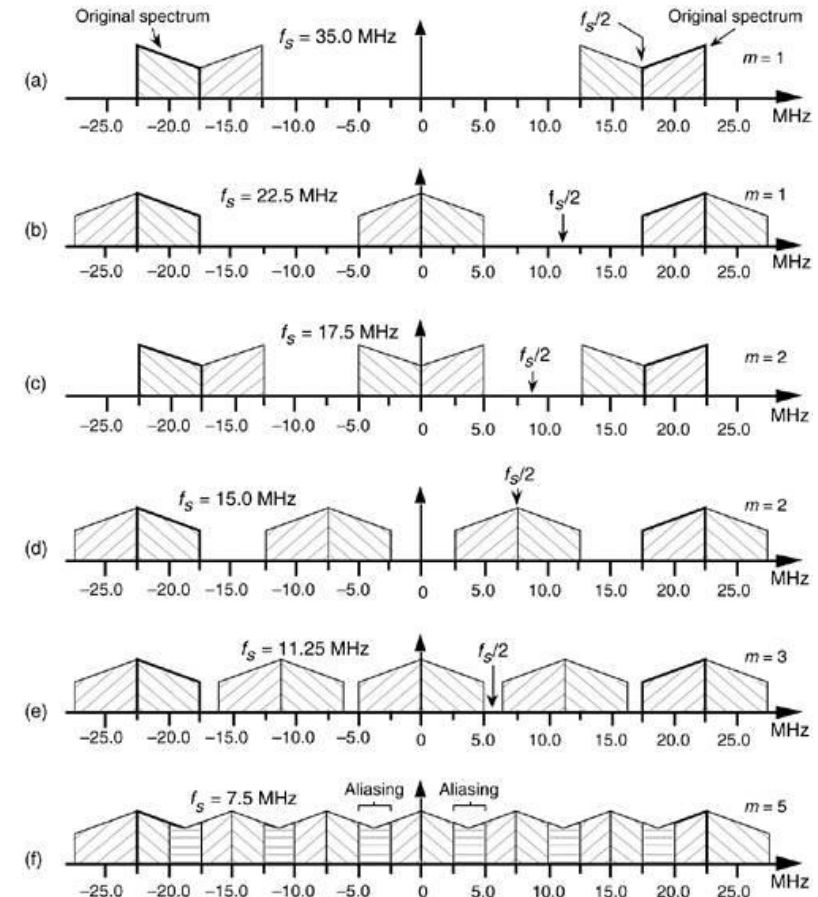
Sometimes aliasing is a *feature*. For example you can demodulate a bandpass signal “for free” using aliasing



R. Lyons

**Important:** sometimes you don't care about aliasing. It depends on the application. But once your data is aliased, that's it.

# Quantization and Encoding

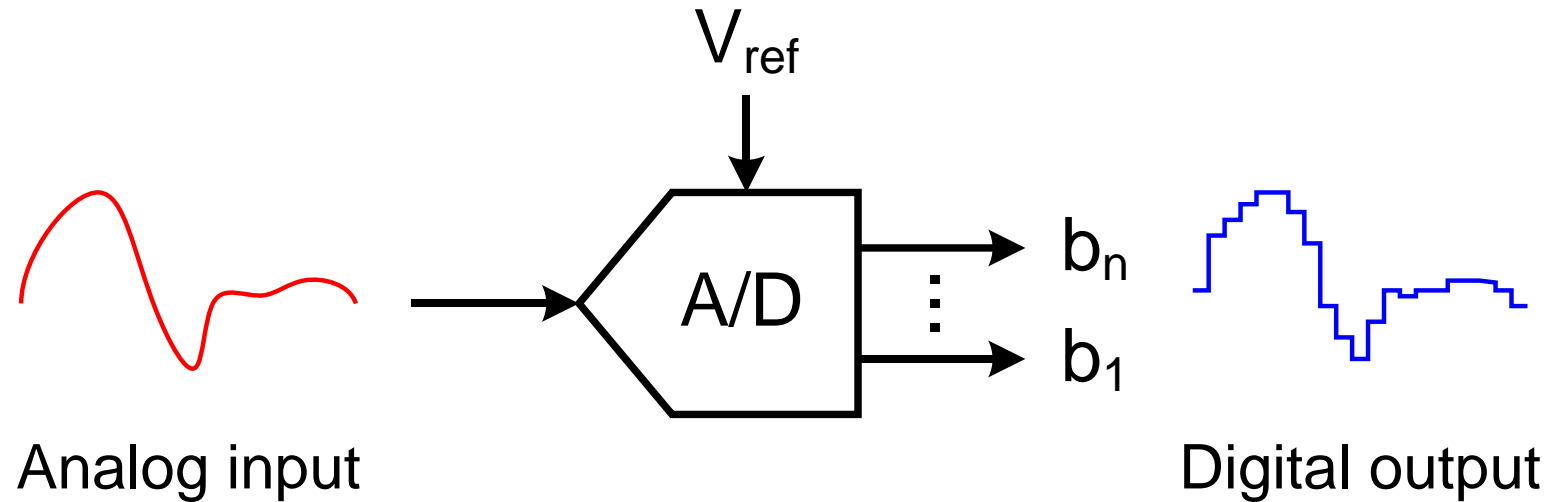

Y. Chui (UTD)

$$D_{out} = 2^n \frac{V_{in}}{V_{ref}}$$

Resolution:  $\log_2$  of quantization levels

Sampling Rate: number of conversions/sec

**Important!** Every ADC has *three* inputs. The analog input, the reference, and the power supply.

# ADC Specifications



# Key ADC Specifications (there are many others...)

## Performance Parameters:

- Sampling Rate
- Resolution
- Analog Bandwidth: Different from sampling rate! Can be more or less (e.g. subsampling applications)
- Power Dissipation
- Die Area

## Static:

- Linearity
- Noise
- Offset (Typically don't care, sometimes you do...)
- Gain Error (Typically don't care)

## Dynamic:

- Signal-to-Noise-Plus Distortion (SNDR)
- Spurious-Free Dynamic Range (SFDR)
- Total Harmonic Distortion (THD)
- Effective Number of Bits (ENOB)




First commercial ADC. 11b, 50 kS/s  
\$8500 in 1954 (\$96,000 today!)



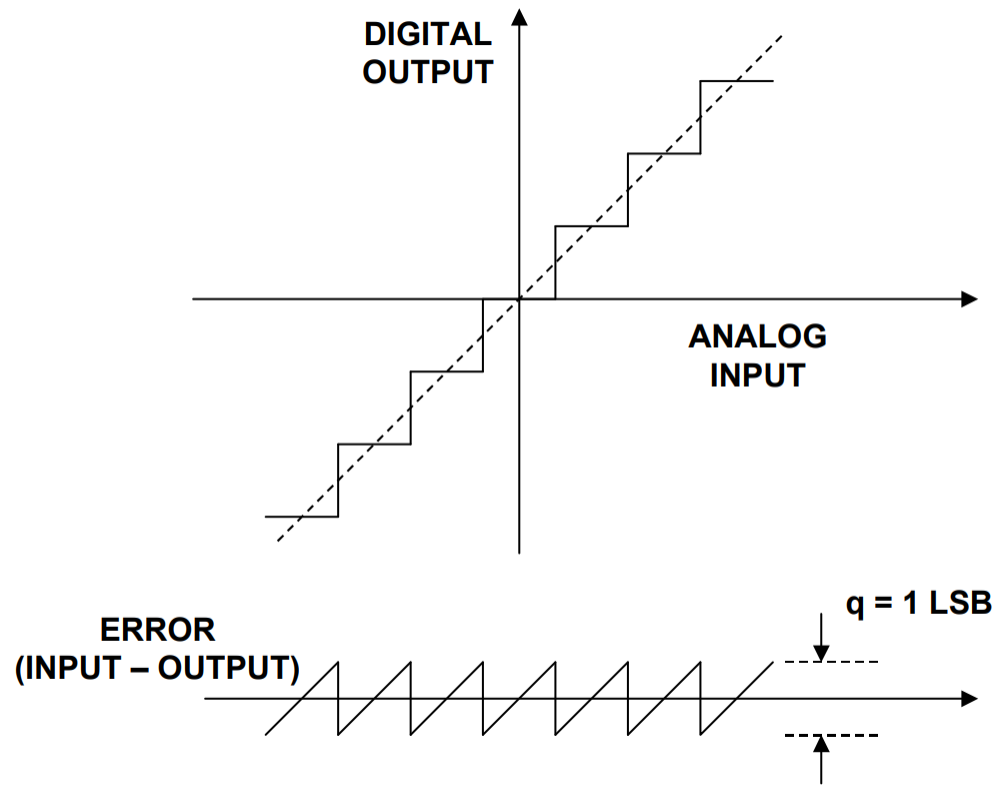
# ADC Noise - Quantization

Two main ADC noise sources: **quantization** noise, and thermal noise

Quantization: inherent uncertainty in mapping from continuous to discrete domain due to size of code



Analog Devices

 

$$e(t) = st, -\frac{q}{2s} < t < \frac{q}{2s}$$


$$\overline{e^2(t)} = \frac{s}{q} \int_{-q/2s}^{q/2s} (st)^2 dt = \frac{q^2}{12}$$

$$\text{rms quantization noise} = \sqrt{\overline{e^2(t)}} = \frac{q}{\sqrt{12}}$$
 
# ADC Noise - Thermal

Two main ADC noise sources: quantization noise, and **thermal** noise

Thermal: noise generated by resistances in the circuit (rms level determined by capacitors when sampled)



$$\overline{v_n^2} = (4kTR_{ON}) \int_0^{\infty} \left| \frac{1}{1 + j2\pi f R_{ON} C} \right|^2 df = \frac{4kTR_{ON}}{4R_{ON}C} = \frac{kT}{C}$$

Thermal noise depends on sampling capacitance. Fundamental tradeoff between noise, speed, and power


$$\text{Total rms noise} = \sqrt{\overline{e_n^2} + \overline{v_n^2}}$$

Most efficient when they are equal
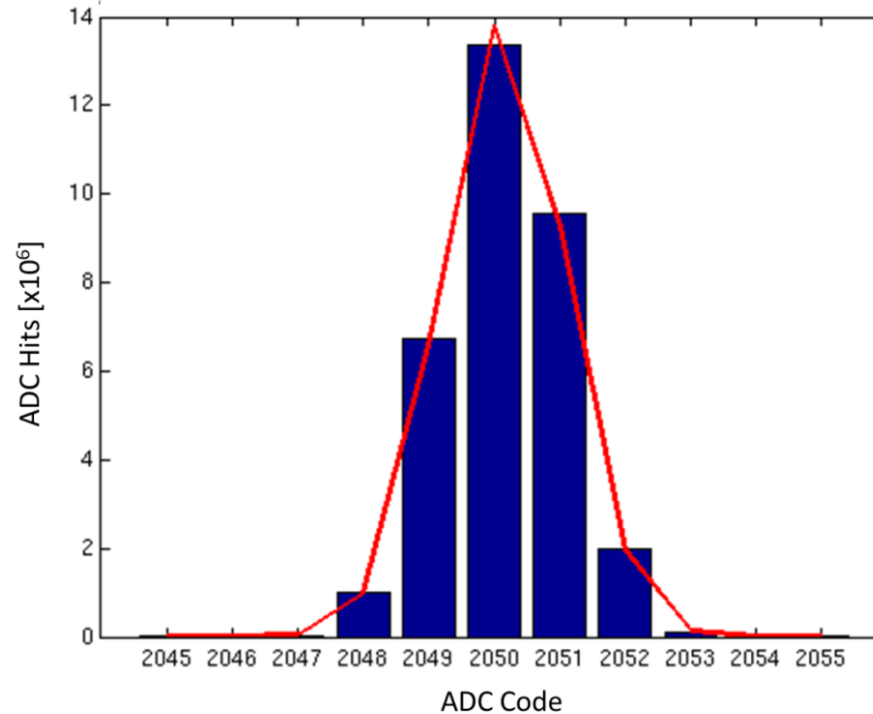
# ADC Noise – example measurement

Idle Channel Test – disconnect (or connect to filtered DC value) and record some codes

By the Central Limit Theorem, we can expect the noise is Gaussian. If it isn't, that's a *clue*.



12-bit ADC

Width is about six codes, so  
Rms noise about 0.9 LSB

(peak to peak =  $6.6\sigma$ )



Offset: two LSBs

# ADC Static Linearity

Often a key specification, and defines the accuracy of the ADC (as opposed to raw resolution)

Two main static linearity measurements: Differential Nonlinearity and Integral Nonlinearity

Simpler in practice than they seem.

  

$$DNL(i) = \frac{\text{binwidth}(i) - LSB}{LSB}$$

$$LSB = \frac{V_{FS}}{2^N}$$

$$INL(i) = \sum_{n=0}^i DNL(n)$$



# Testing ADC Static Linearity

Knowing how to test an ADC is critical, because it:

1. informs your design choices
2. testing techniques can often be adapted to simulation

General approach:

1. apply test signal with known probability density function (PDF)
2. Create histogram of measured ADC codes
3. Map measured probability mass function to expected PDF
4. Interpret per-code deviations as DNL and sum DNL to get INL


Example:

Ramp Based Testing: Apply a ramp to ADC input. PDF is uniform (simple!)

DNL for each code is simply count for that code minus average count (simple!)

Don't need many codes - about  $1/([\text{DNL resolution}] * \text{number of codes})$ . For 10b @ 0.01 LSB  $\rightarrow$  102400 counts

 Catch: difficult to generate a linear ramp, and typically you want your test signal to be 10X more linear than ADC. Most commercial ramp generators aren't better than 0.1% linear (at best!)




# Testing ADC Static Linearity

Solution sine-wave-based testing

It is much easier to generate a linear sine than ramp → can heavily filter

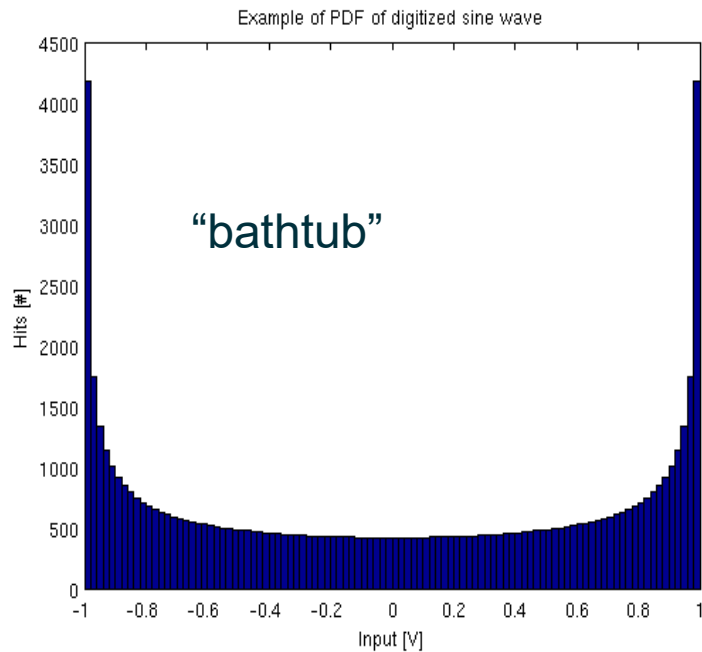PDF of sine is more complicated than ramp



$$pdf(V) = \frac{1}{\pi\sqrt{A^2 - V^2}}$$

Number of samples needed: 
$$N_{samp} = \frac{\pi 2^{N-1} z_{\alpha/2}^2}{\beta^2}$$

$\alpha/2$  = confidence level

$\beta$  = desired DNL resolution

$N$  = number of ADC codes

Many more samples needed.

# ADC Dynamic Performance

**SNDR:** Captures both noise and nonlinearity into a single measure.

Assuming a full-scale sine wave input, SNDR is:

$$SNDR = \frac{2^N}{2\sqrt{2} \left( \frac{1 + v_n}{\sqrt{12}} + \frac{DNL}{\sqrt{3}} \right)}$$

**SFDR:** Difference between input tone and highest harmonic.

Rule of thumb for estimating SFDR:

$$SFDR \approx \frac{2^B}{INL}$$

**THD:** Ratio of power of fundamental to sum of powers of all harmonics


$$THD = \frac{\sum_{n=2}^n P_n}{P_1}$$

**ENOB:** Number of bits of ideal ADC that gives same SNDR as ADC under test.

When quantization = thermal, ENOB = N-1

$$ENOB = \frac{SNDR - 1.76 + 20 \log_{10} \left( \frac{V_{FS}}{V_{input}} \right)}{6.02}$$

# ADC Dynamic Performance – example plot

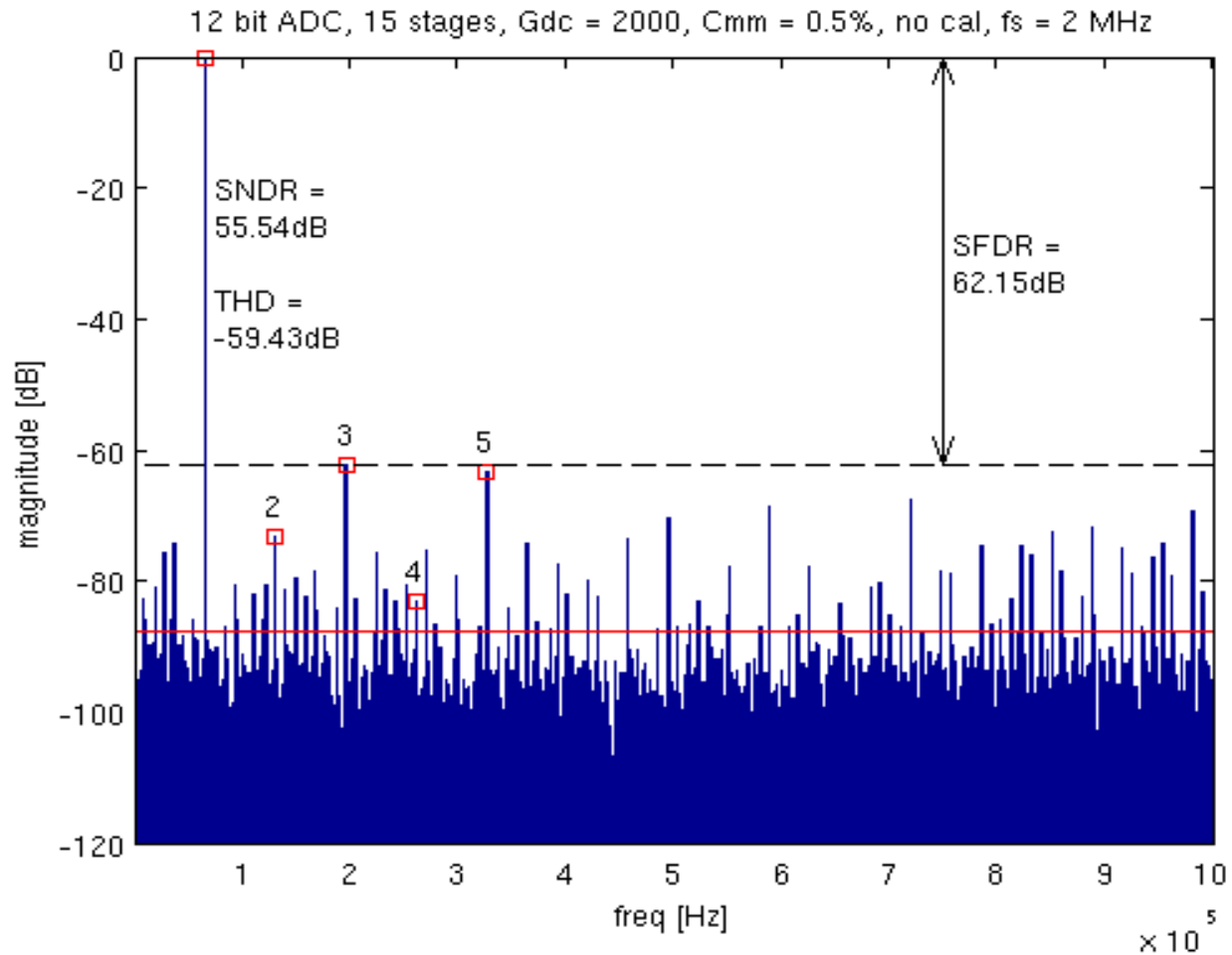



Here,  $ENOB = (55.54 - 1.76)/6.02 = 8.9$  bits

# ADC Dynamic Performance – Coherent Sampling

General technique: apply pure sine wave to ADC and take FFT of resulting output codes

Vitally important that all power of input tone is in single FFT bin → Coherent Sampling
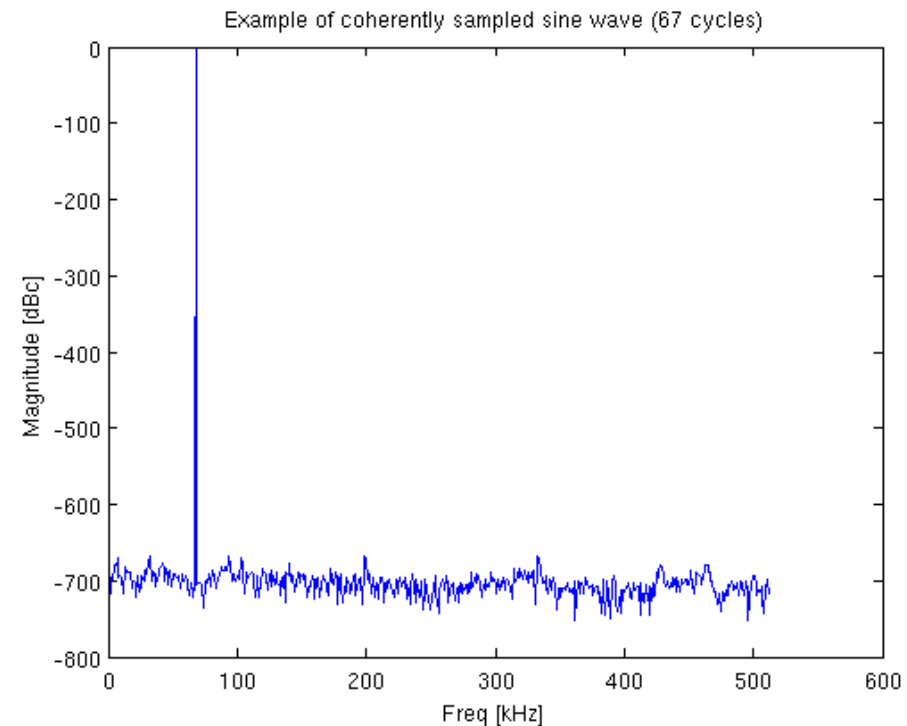 
$$f_{in} = \frac{N_{cycles}}{N_{samples}} f_s$$




Tip: pick  
prime # of  
cycles



# ADC Testing Takeaways

1. Make sure your reference & power are significantly more stable than your ADC
2. Make sure your test signal is significantly more linear than your ADC
3. Make sure your board and input have extremely low noise during noise tests
4. Make sure you use coherent sampling for dynamic testing
5. Make sure you lock both the signal generator and the ADC clock to the same time base


# ADC Performance Space

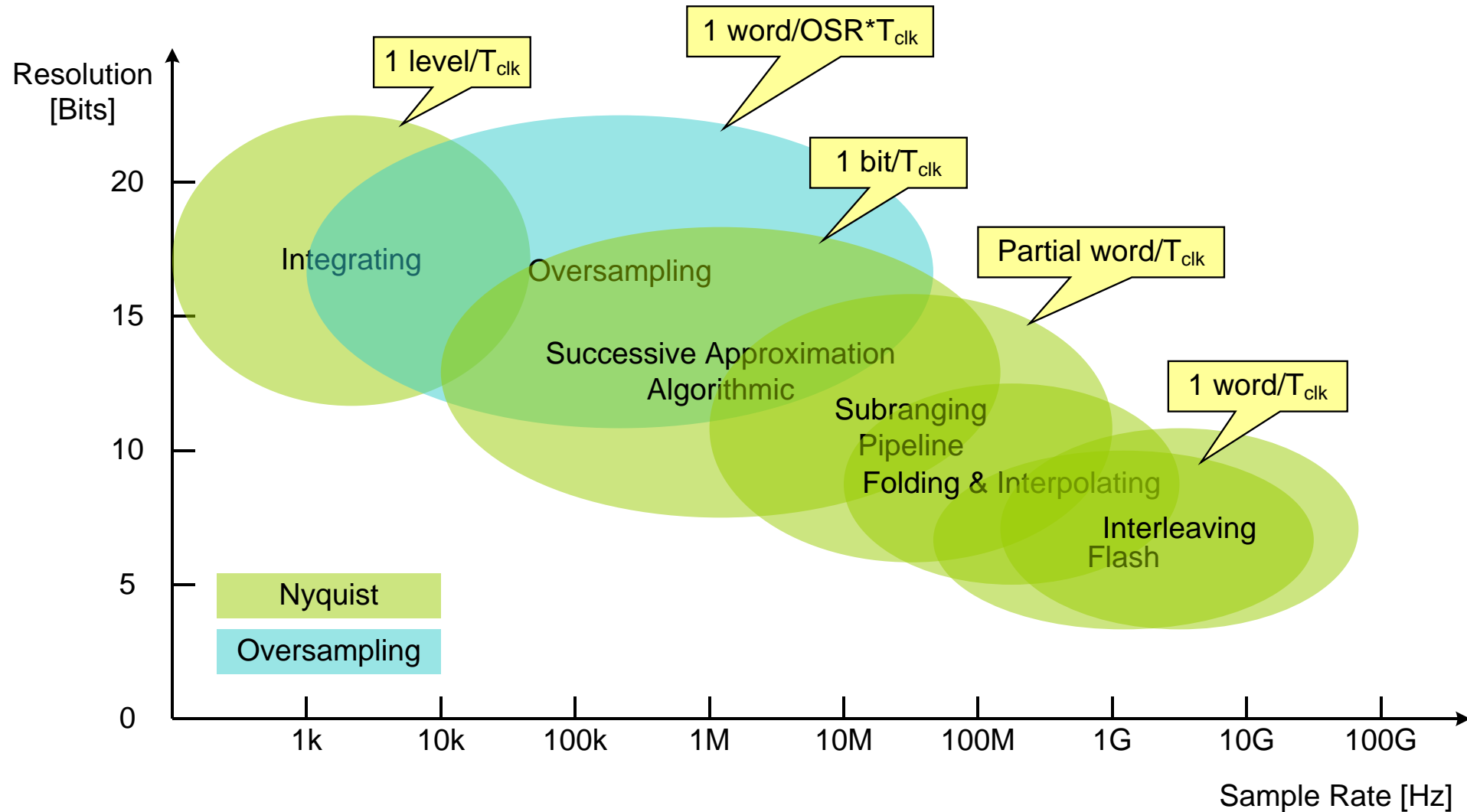

 
# Impact of ADCs (Digital Audio example)



Fairlight CMI  
1979: \$32000  
(\$132k in 2023 \$)  
Stevie Wonder



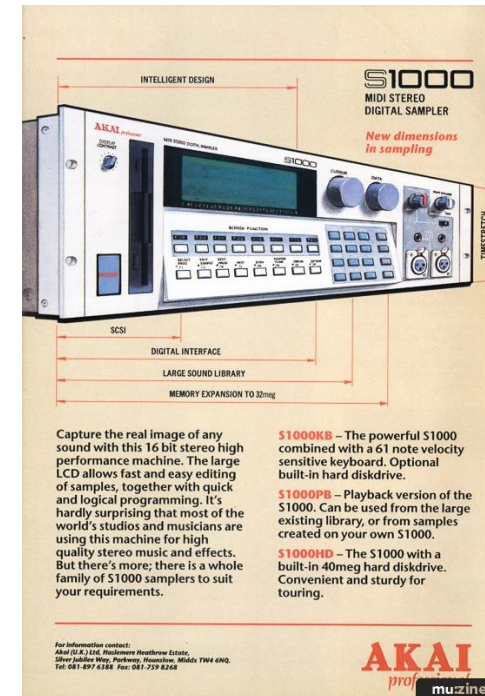E-mu Emulator II  
1984: \$8000  
(\$23k in 2023 \$)  
Depeche Mode



Akai S-1000  
1988: \$2500  
(\$6350 in 2023 \$)  
Everyone



Akai MPC-One  
2023: \$599



# ADC Architectures





# ADC Architectures

HEP Relevant ADC architectures from slowest to fastest. Note: Everything was invented by 1970.

1. Integrating (“Wilkinson”)
2. Sigma-Delta
3. Successive Approximation
4. Pipelined
5. Flash



# Integrating ADC

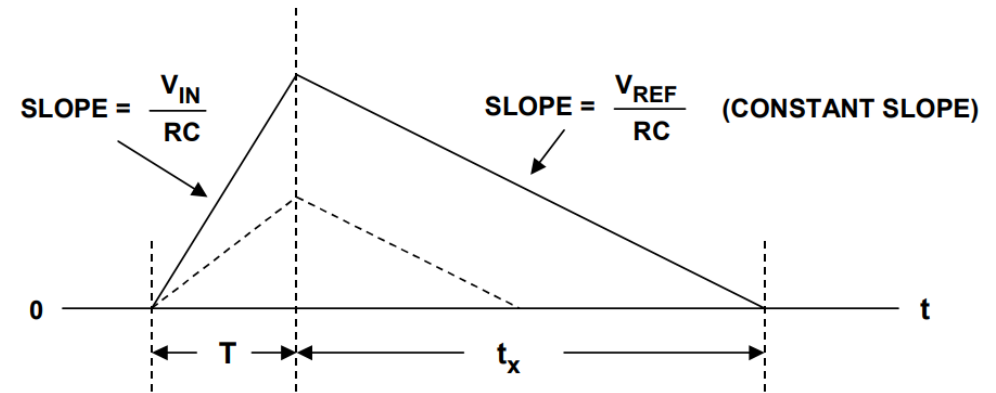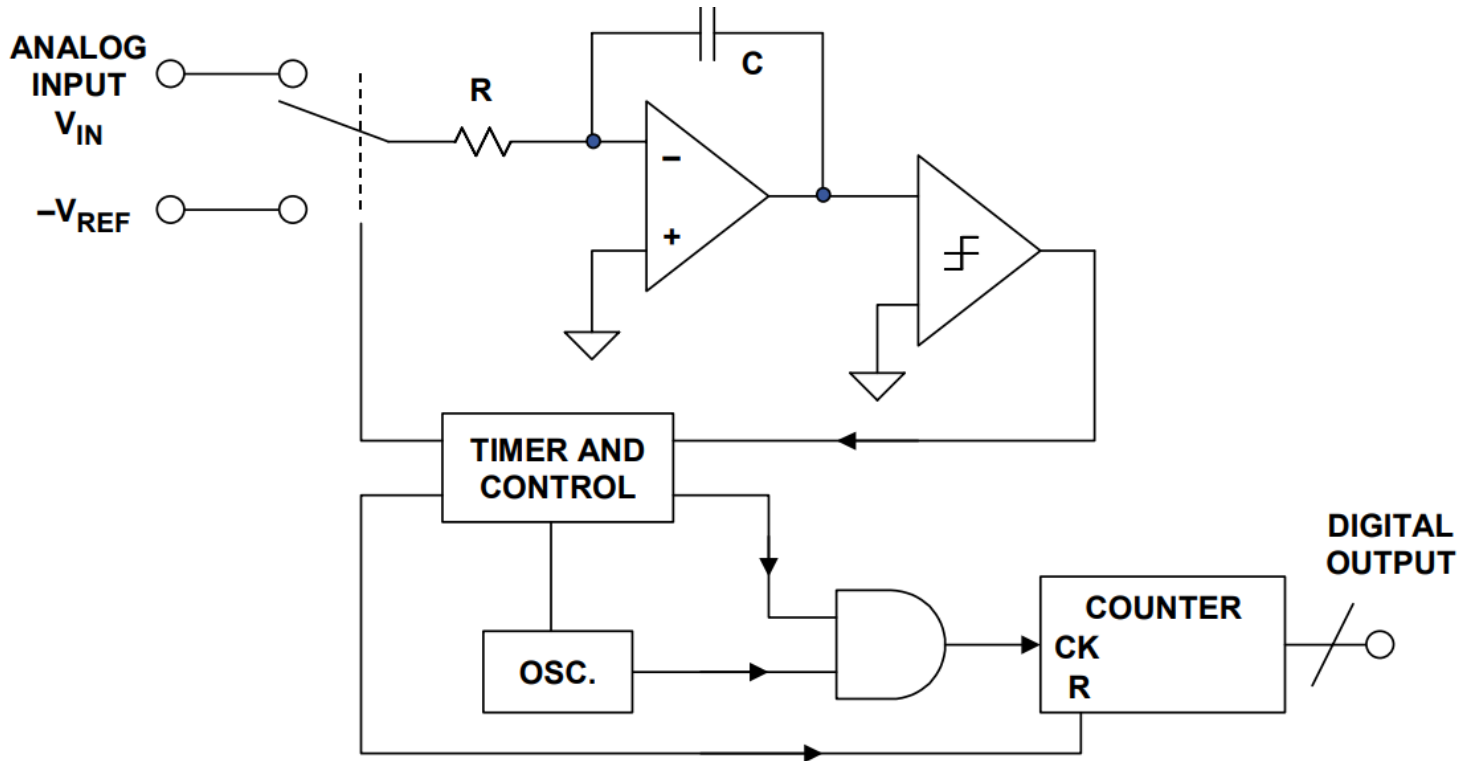


$$\frac{V_{IN}}{RC} T = \frac{V_{REF}}{RC} t_x$$

$$t_x = \frac{V_{IN}}{V_{REF}} T$$

Called “Dual Slope ADC” in industry. Remove R (direct charge readout) to make a Wilkinson

# Oversampling

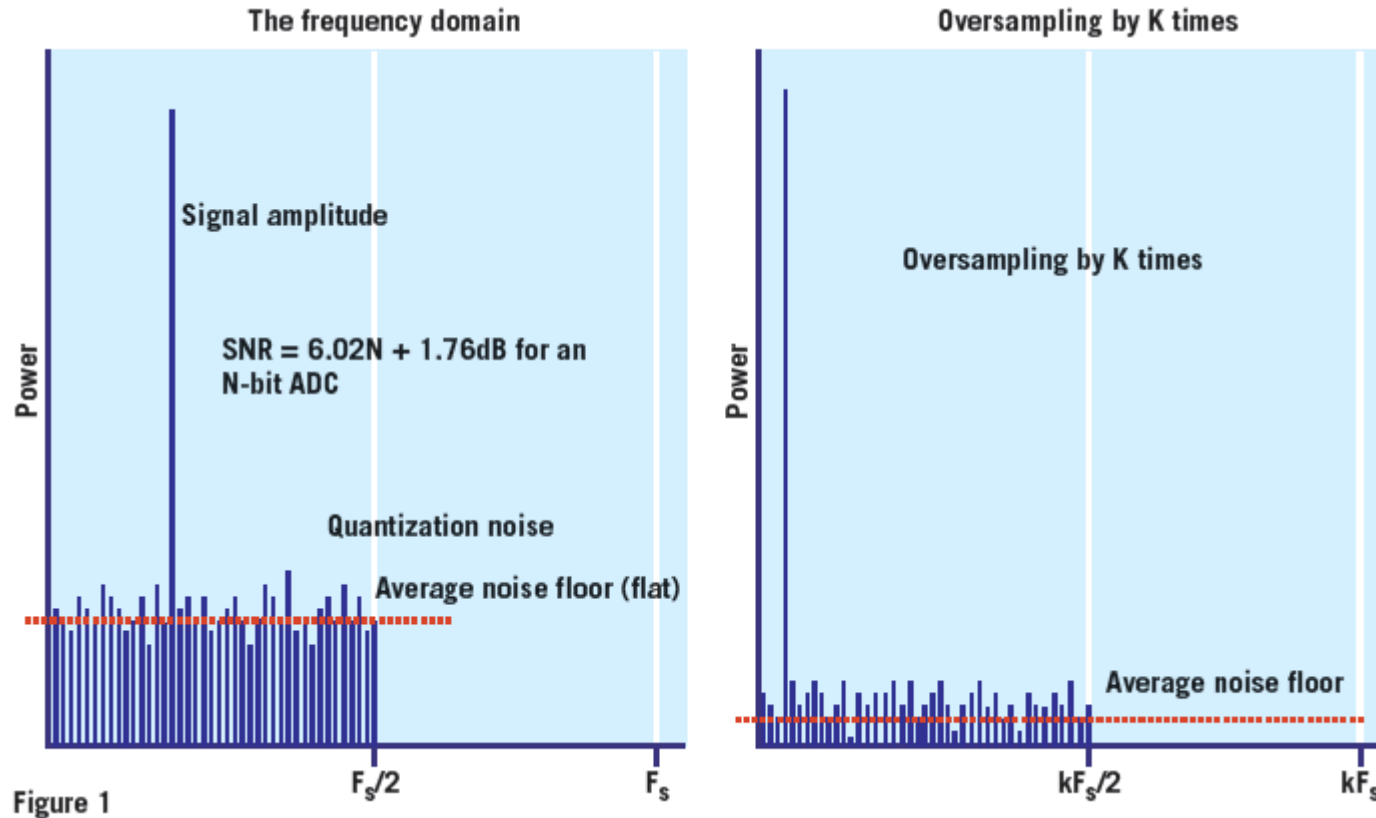


SNR increase:  
3 dB / octave

Spread constant noise power over a larger bandwidth and then digitally filter → reduced quantization noise  
Extend this by shaping the noise (pushing more of it to higher frequencies where it can be filtered)


 
# Sigma-Delta ADC

Idea: Don't just oversample, modulate the input to put more of the quantization noise power at higher frequencies



Key Idea: signal sees low-pass filter, quantization noise sees high-pass filter.

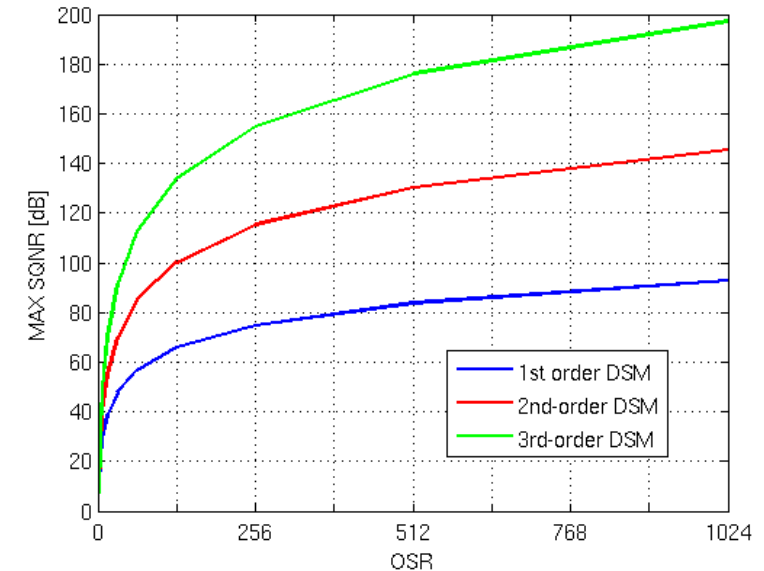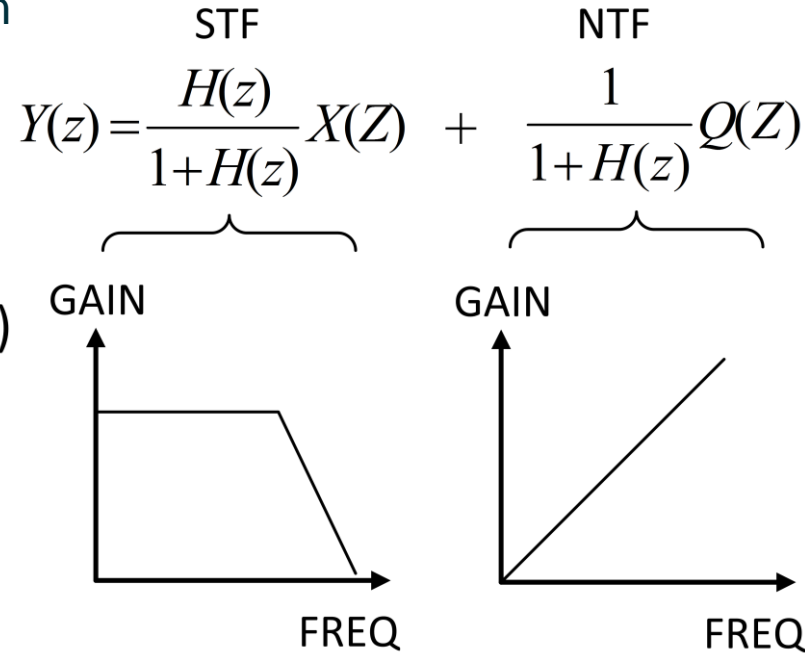Loop order is defined as number of poles in  $H(z)$



$$SNQR_{improvement} \approx 3(2L + 1) \text{ dB}$$


For  $L = 1$ , idle tones in output spectrum a problem and high OSR required

For  $L < 3$ , stability is assured → mitigates design risk


For  $L \geq 3$ , low OSR possible (simplifying clocking design)

# Successive Approximation (SAR) ADC

Simple 6-bit example

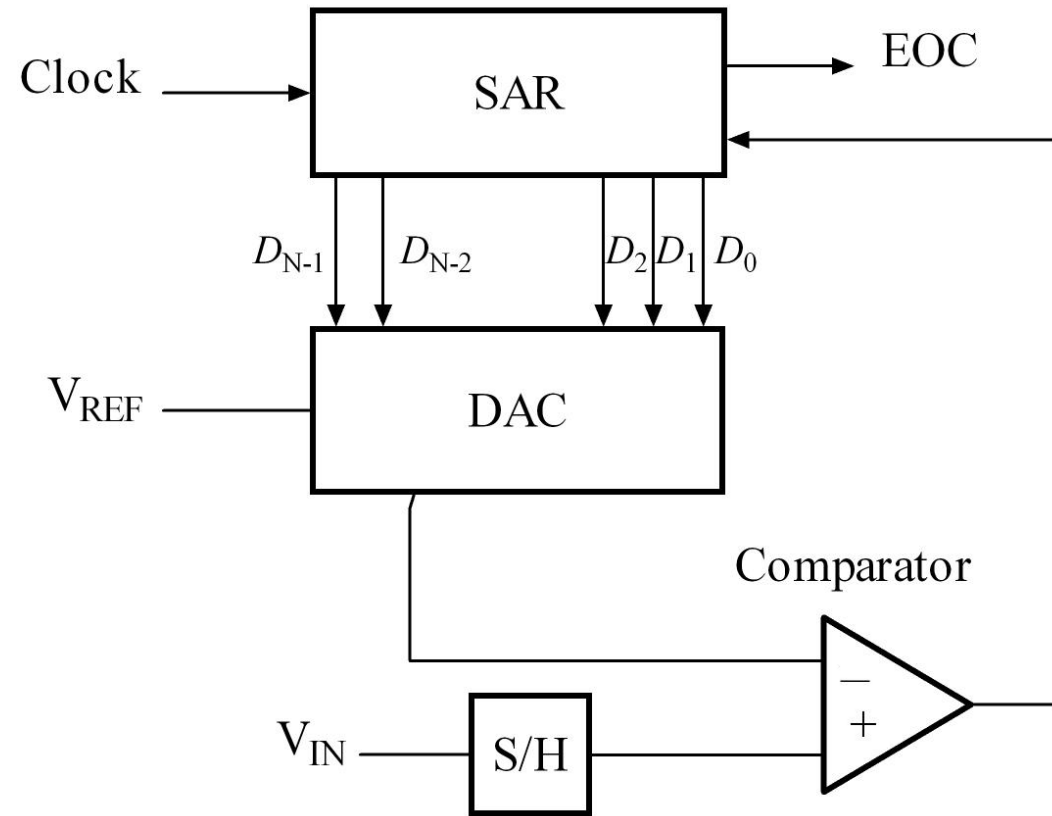

 Directly implements binary search algorithm in hardware



ADC output

Comparator output


ADC strobe

DAC output



$V_{in} = 0.865 \text{ V}$ ,  $V_{ref} = 1.5 \text{ V}$   
 $V_{cm} = 0.5 \text{ V}$ ,  $\rightarrow$  code = 23
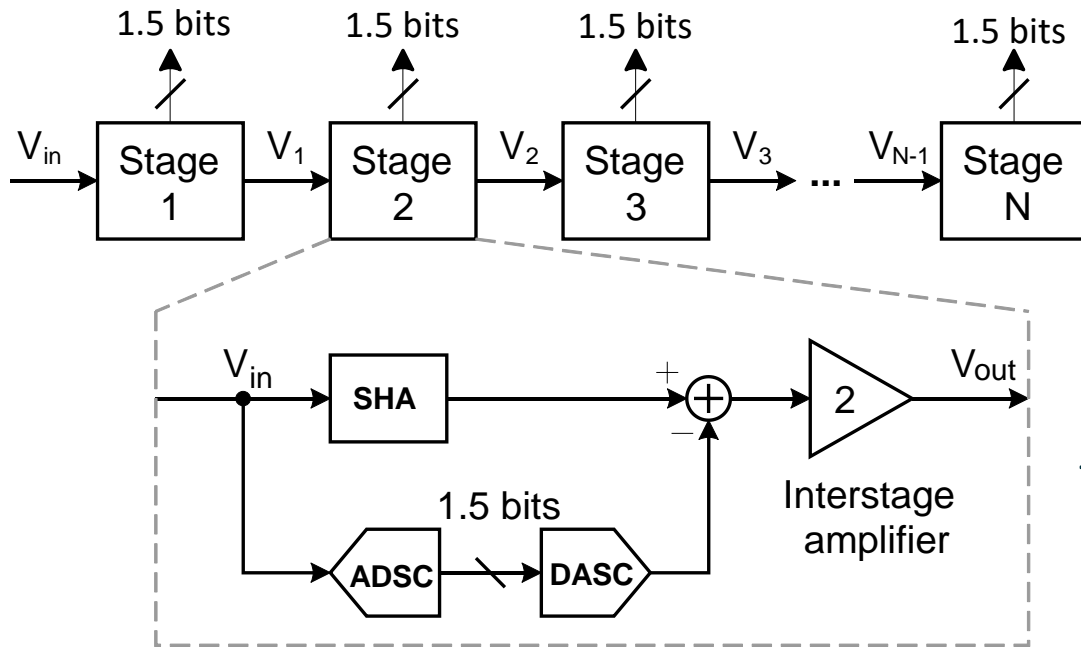
# Pipelined ADC

Multi-stage ADC, with each stage operating concurrently  $\rightarrow$  high throughput



 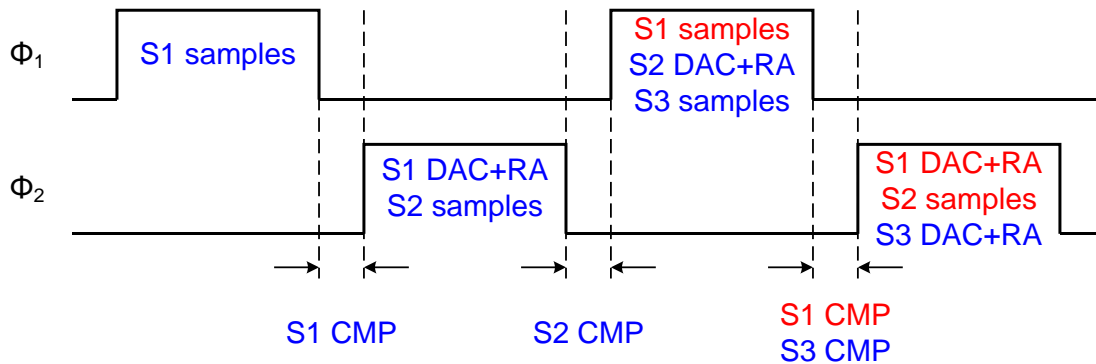Each stage processes the quantization error (residue) of previous stage.



$$V_o = 2 \cdot V_i - (b-1) \cdot V_R$$

**THE** enabling technology for Pipelined ADCs



# Pipelined ADC




**19" RACK-MOUNTED, 150W, \$10,000.00**

**\$95k in 2023 dollars!**


**INSTALLATION OF 12 ADCs  
IN EXPERIMENTAL DIGITAL  
RADAR RECEIVER**

**8 bits, 10 MS/s (1966)**

 

First high-speed Pipelined ADC (modular, not CMOS) by Computer Labs of North Carolina (later became Analog Devices High-Speed Converters Division, where I worked before LBNL).

# Flash ADC

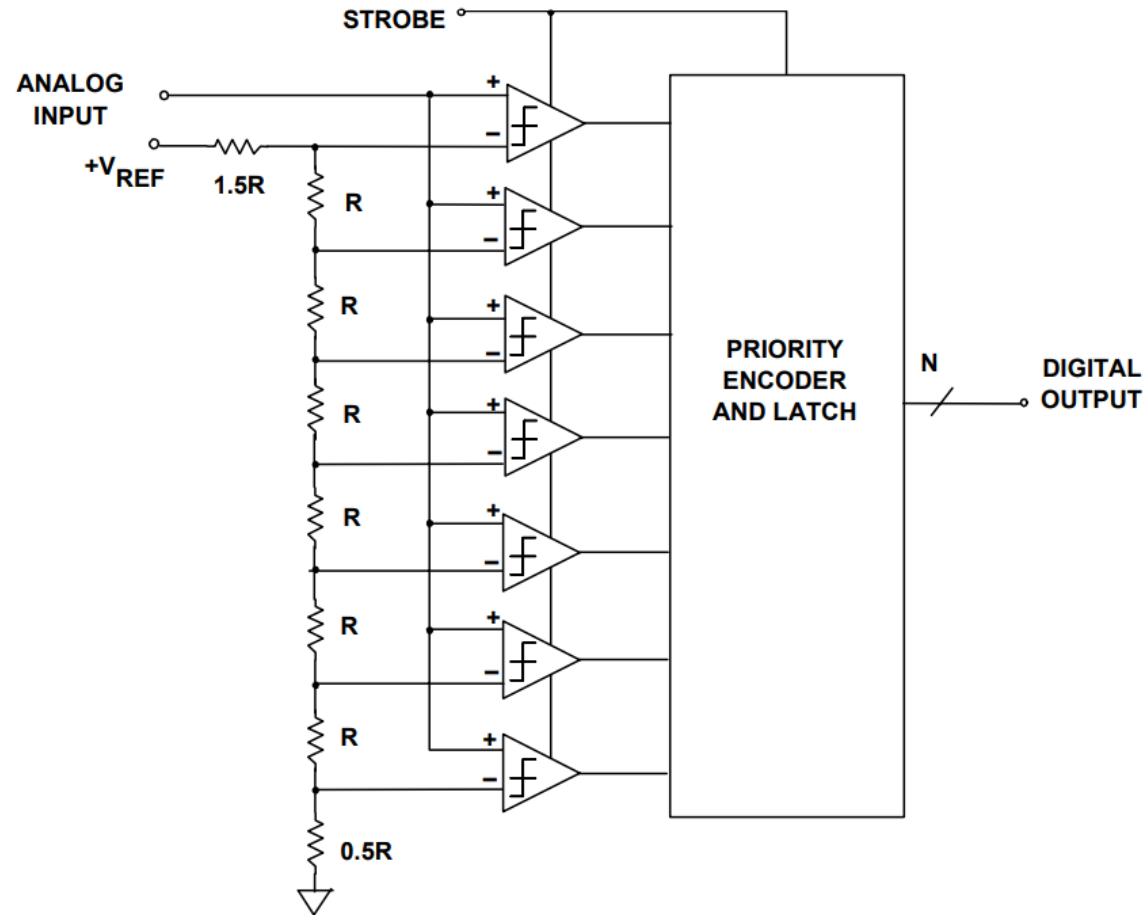


FAST.

Power Hungry.

Limited to about 8 bits.

Used as sub-ADCs in multi-stage ADCs

 

5" x 7" x 0.5", 21W, \$3,500.00

# Flash ADC



TDC1007



## Monolithic Video A/D Converter 8-bit, 20MSPS

The TDC1007 is an 8-bit fully parallel (flash) analog-to-digital converter, capable of digitizing an input signal at rates up to 20MSPS (MegaSamples Per Second). It will operate accurately without the use of an external sample-and-hold amplifier, with analog input signals having frequency components up to 7MHz.

A single CONVert (CONV) signal controls the conversion operation of the device which consists of 256 sampling comparators, encoding logic, and a latched output buffer register. The device will recover from a full-scale input step in 20ns. Control inputs are provided to format the output in binary, two's complement, or inverse data coding formats.

The TDC1007 is patented under U.S. Patent No. 3283170 with other patents pending.


### Features

- 8-Bit Resolution
- Conversion Rates Up to 20MSPS
- Sample-And-Hold Amplifier Not Required
- Bipolar Monolithic Construction
- TTL Compatible Inputs and Outputs
- Binary or Two's Complement Mode
- Differential Phase = 1.0 Degrees
- Differential Gain = 1.7%
- Evaluation Boards Available: TDC1007E1C or TDC1007P1C

### Applications

- Video Systems 3x or 4x Subcarrier, NTSC or PAL
- Radar Systems
- High-Speed Multiplexed Data Acquisition
- Digital Signal Processing

### Functional Block Diagram

 

TRW TDC1007 8-bit,  
20 MS/s Flash ADC  
enabled new field of  
“digital video”



Won technical Emmy in 1989!  
ADC designers are creative.



# ADCs for High-Energy Physics







# In the dark ages\*...

## IC Development at UC Berkeley

The Microlab was located on the 4<sup>th</sup> floor of Cory Hall, facing Hearst Avenue.



Hodges Flip-Flop (1963)

  

David Hodges William Black





Paul Gray Paul McCreary  
First all-MOS ADC (1975)!

\*1960s – 1970s

HEPIC – Analog-to-Digital Converters

Mask Camera

  

Stephen Lewis – First CMOS Pipelined ADC (1986)

# The rise of the Custom ASIC




1960s : Only a few Universities made chips

Late 70s : Technology for Multi-Project Wafers (Mead and Conway)

1981 : Founding of MOSIS with DARPA support

1987 : MOSIS commercialized (first large-scale eCommerce application on the Internet)

   
Also 1987 : TSMC founded (and Fabless Semi industry was born!)




 
# First Physics ASICs

Microplex – first custom ASIC for Physics Research




NMOS process (no P-channel devices) - SLAC - 1984

**128 channels**  
**3 mW / channel**

Walker, Parker, Hyams, Shapiro, "Development of High Density Readout for Silicon Strip Detectors," NIM 226 (1984)

 SVX – First CMOS ASIC for Physics Research



**11,000 transistors**

CDF experiment used 240 SVX chips → 30720 channels

Already at discrete limit



CMOS process (with P-channel devices) - LBNL - 1987

**128 channels**  
**1.25 mW / channel**


Kleinfelder, et al.; "A Flexible 128-Channel Silicon Strip Detector Instrumentation Integrated Circuit with Sparse Data Readout", TNS 35 (1988)



# Unique Challenges for HEP ADCs


Physics experiments often create extreme environments for their readout ASICs

## High Radiation

 

ATLAS Detector

## Cold Temperature

 


ProtoDUNE LAr TPC

## Liquid Argon

 
# Unique Challenges for HEP Custom ADCs - Radiation

Two main types of radiation damage to integrated circuits that concern us (Single Event Latchup and Single Event Transients of less importance in HEP experiments)

Total Integrated Dose – structural damage to silicon structure that leads to failures




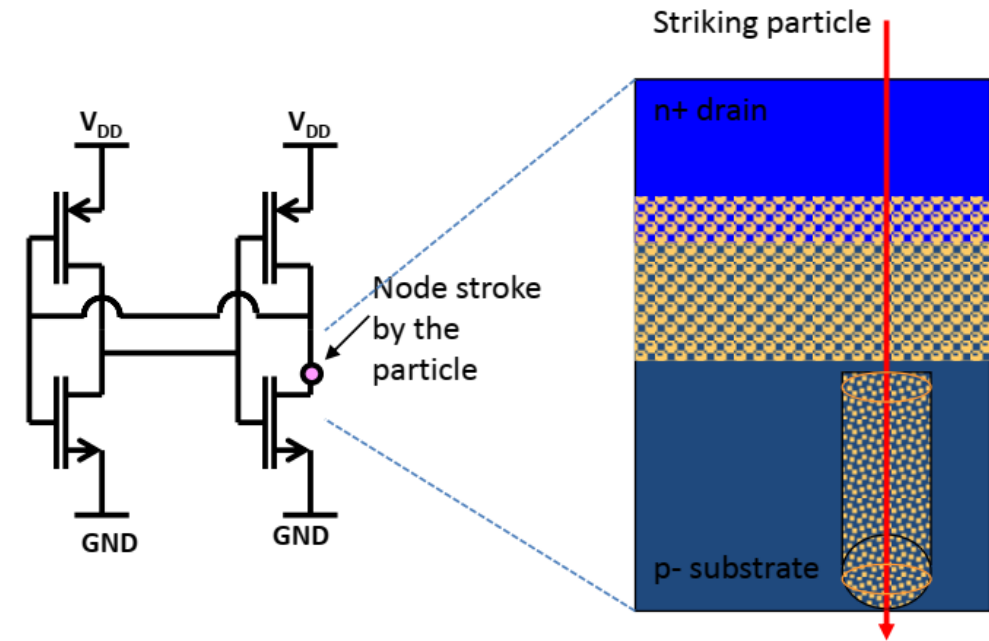
Single Event Upset – transient effects that could modify data or lead to incorrect data




  
# Radiation -- Total Integrated Dose (TID)

Requirements for TID radiation tolerance for physics far exceed any commercial application




# Radiation -- Total Integrated Dose (TID)



Key mitigations:

- use scaled technologies (Microplex and SVX only radiation tolerant to 10s of krad)
- “Hardness-By-Design” techniques (long devices / enclosed layout / guard rings / etc)
- Annealing

 Source-Drain leakage is eliminated by the Enclosed Layout Transistor (ELT)...



  
Inter-diffusion leakage is eliminated by p+ guard rings...




F. Faccio
 
# Radiation – Single Event Effects (SEE)

Scaling devices makes ASICs more resilient to TID, but *less* resilient to SEE



C. Zamantzas

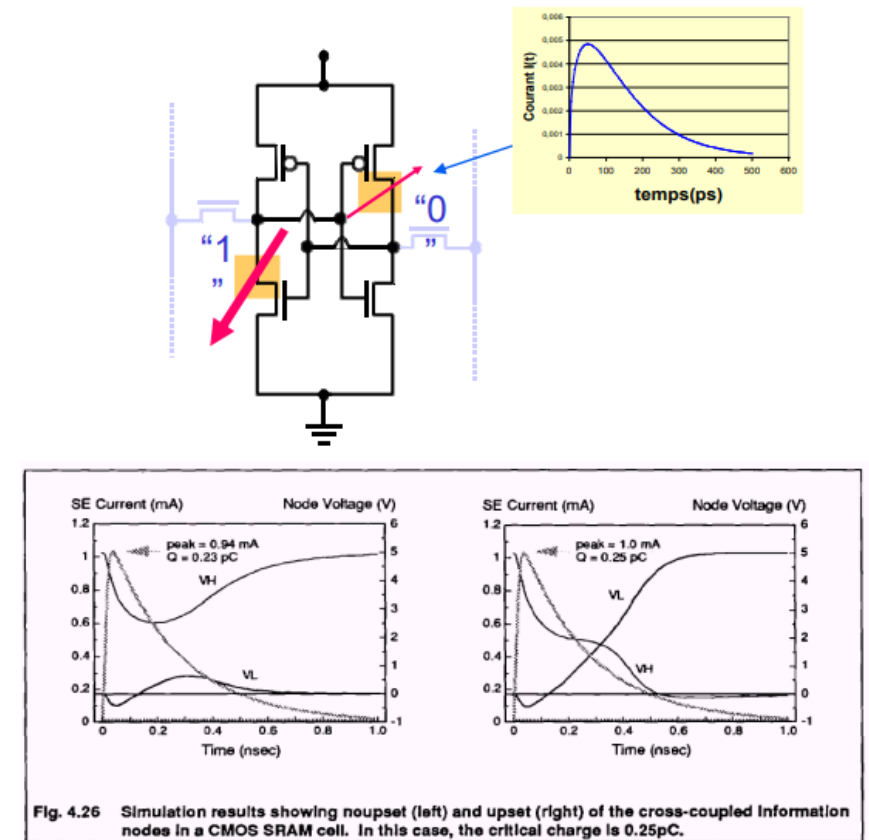


R. Gaillard




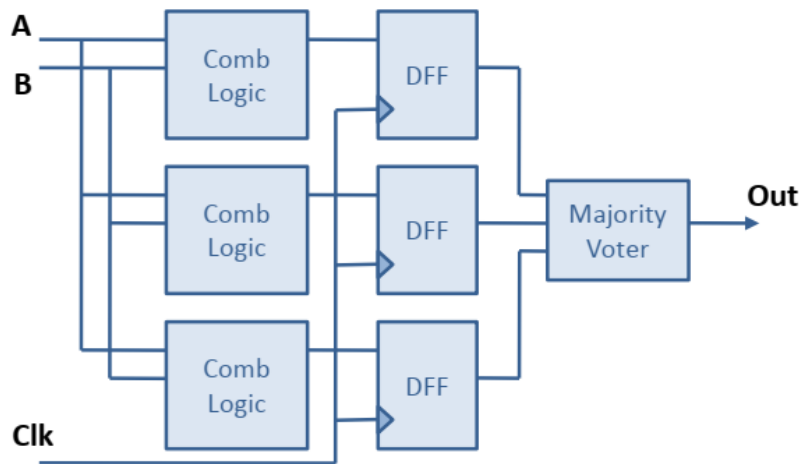
# Radiation – Single Event Effects (SEE)

Key mitigations: Triple Modular Redundancy (TMR), Hamming encoding, continuous reconfiguration




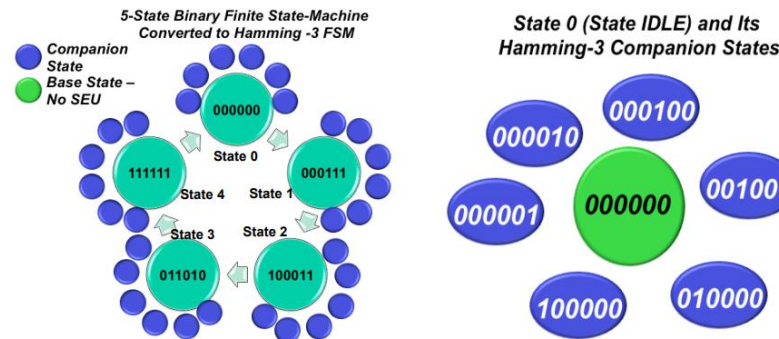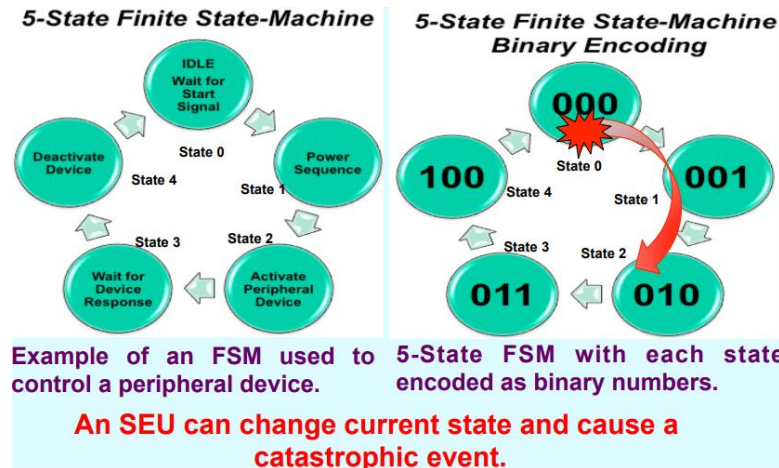Triple Modular Redundancy (TMR)  
- Device level? Circuit? Module?





Hamming encoding

K. Berg

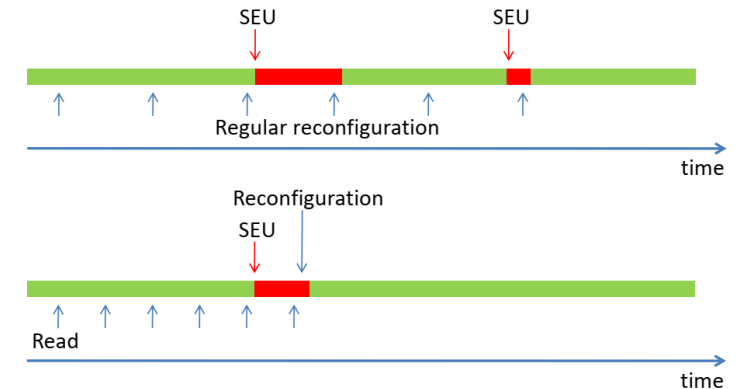


Continuous Reconfiguration

# Cryogenic Operation

  

“Hot” carriers cause early device aging

# Reliability and biasing drift

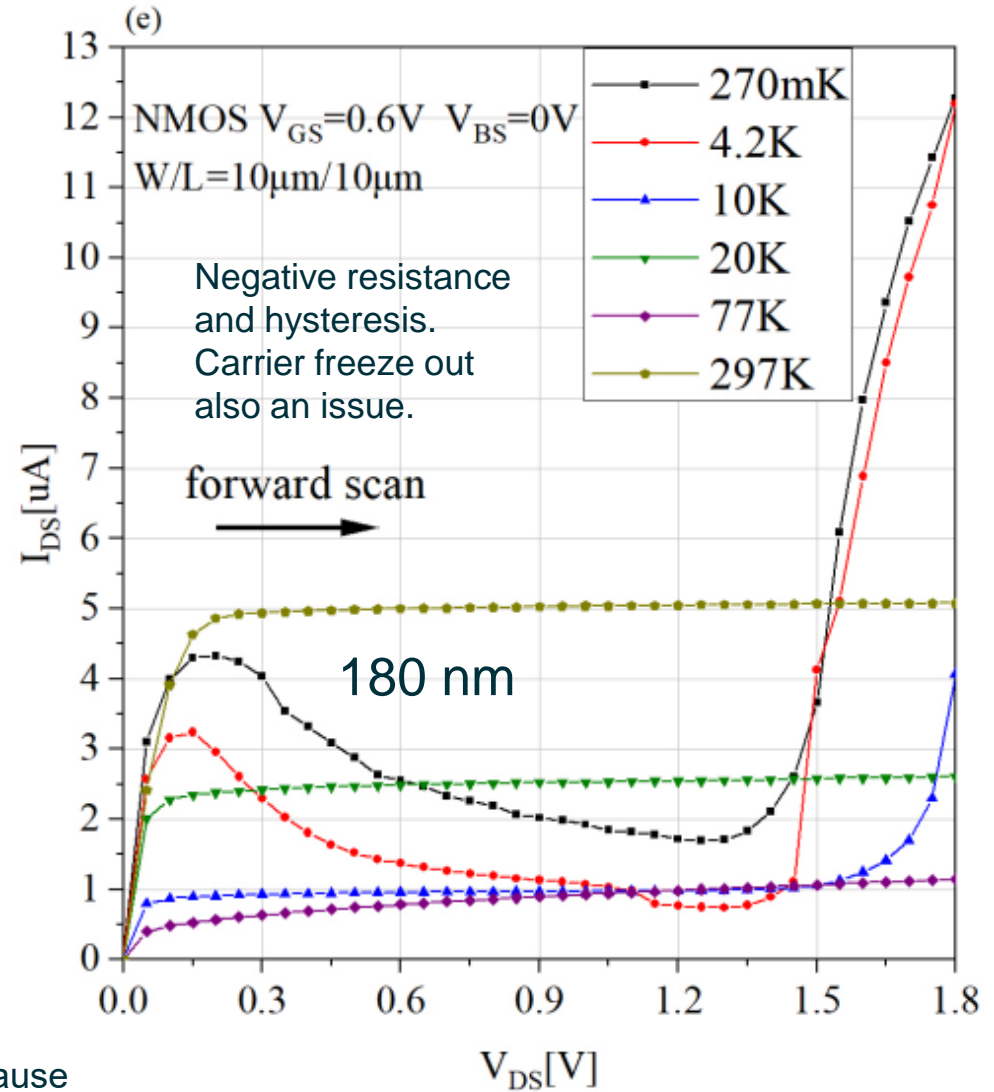


# Design Example




 
# Design Example – Sigma-Delta ADC

Goal: 12b – 100 kHz ADC for power monitoring




Doubling OSR improves SQNR by  $(6L+3)$  dB  
 or  $L + 0.5$  bits  
 Choose 2<sup>nd</sup> order modulator

 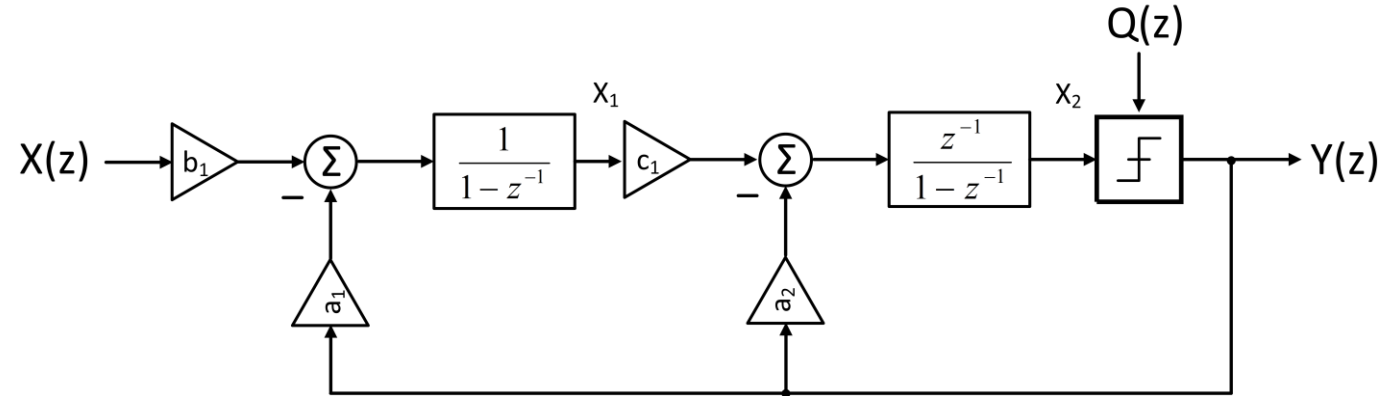Synthesize ADC transfer function in MATLAB or Python






# Design Example – Sigma-Delta ADC

 

Synthesized modulator close to ideal
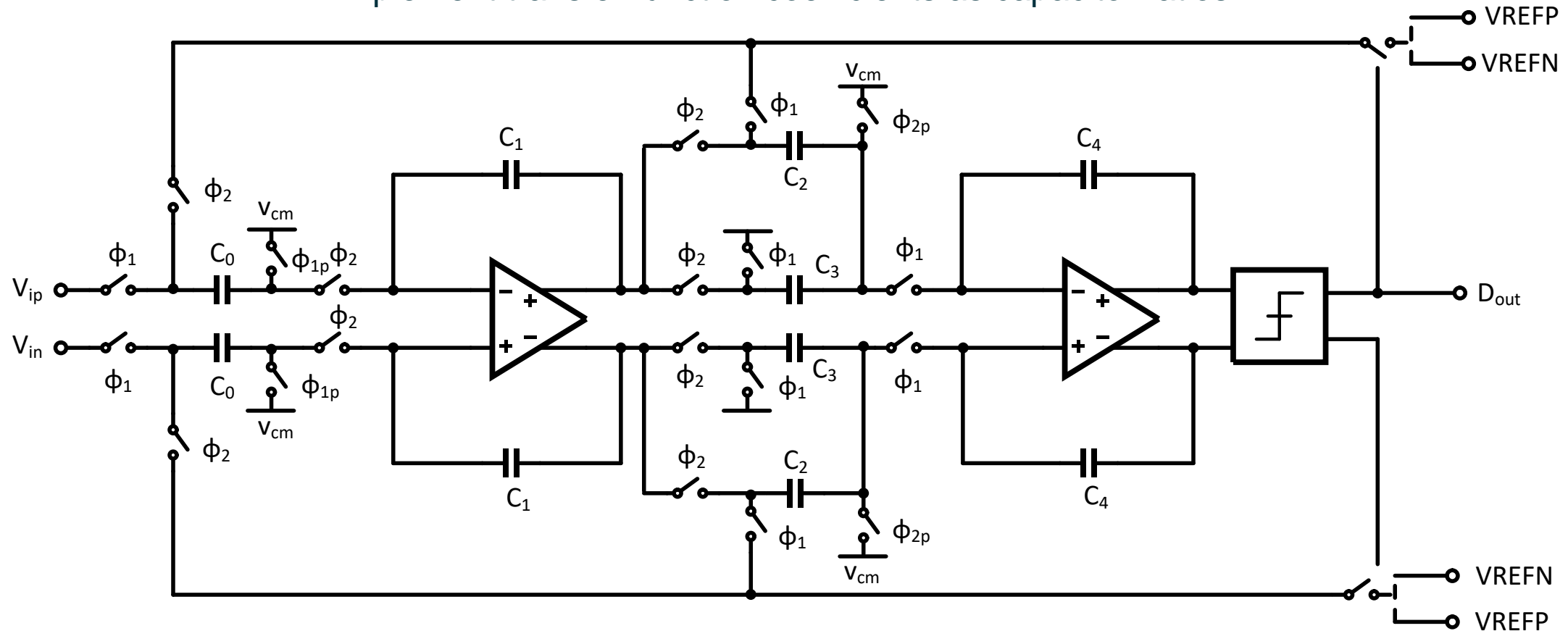
# Design Example – Sigma-Delta ADC


Implement transfer function coefficients as capacitor ratios



Modulator Schematic



# Design Example – Sigma-Delta ADC

 


1<sup>st</sup> int

2<sup>nd</sup> int

Vinput

Digital  
out
 
# Design Example – Sigma-Delta Digital Filter



Structure called Cascaded Integrator Comb (CIC) filter

For sinc<sup>3</sup> filter:

$$H(z) = \left( \frac{1 - z^{-OSR}}{1 - z^{-1}} \right)^3$$



Filter implemented with Verilog HDL

```

25
26
27 /*Perform the Sinc3 ACTION*/
28 always @ (in_bit)
29   if(in_bit==0)
30     ip_data <= -1; /* change from a 0 to a -1 for 2's comp */
31   else
32     ip_data <= 1;
33
34 /*INTEGRATOR Perform the accumulation (IIR) at the speed of the modulator.
35  Z = one sample delay MCLKOUT = modulators conversion bit rate */
36
37 always @ (posedge clk or posedge reset)
38   if (reset) begin
39     /*initialize acc registers on reset*/
40     acc1 <= 0;
41     acc2 <= 0;
42     acc3 <= 0;
43   end else begin /*perform accumulation process*/
44     acc1 <= acc1 + ip_data;
45     acc2 <= acc2 + acc1;
46     acc3 <= acc3 + acc2;
47   end
48
49 /*DECIMATION STAGE (MCLKOUT/ WORD_CLK) */
50 always @ (negedge clk or posedge reset)
51   if (reset)
52     word_count <= 0;
53   else
54     word_count <= word_count + 1;
55
56 always @ (word_count) word_clk <= word_count[6];
57
58 /* DIFFERENTIATOR Perform the comb filtering (FIR) at a lower speed.
59  WORD_CLK = output word rate */
60
61 always @ (posedge word_clk or posedge reset)
62   if(reset) begin
63     acc3_d2 <= 0;
64     diff1_d <= 0;
65     diff2_d <= 0;
66     diff1 <= 0;


```

# Design Example – Sigma-Delta ADC

 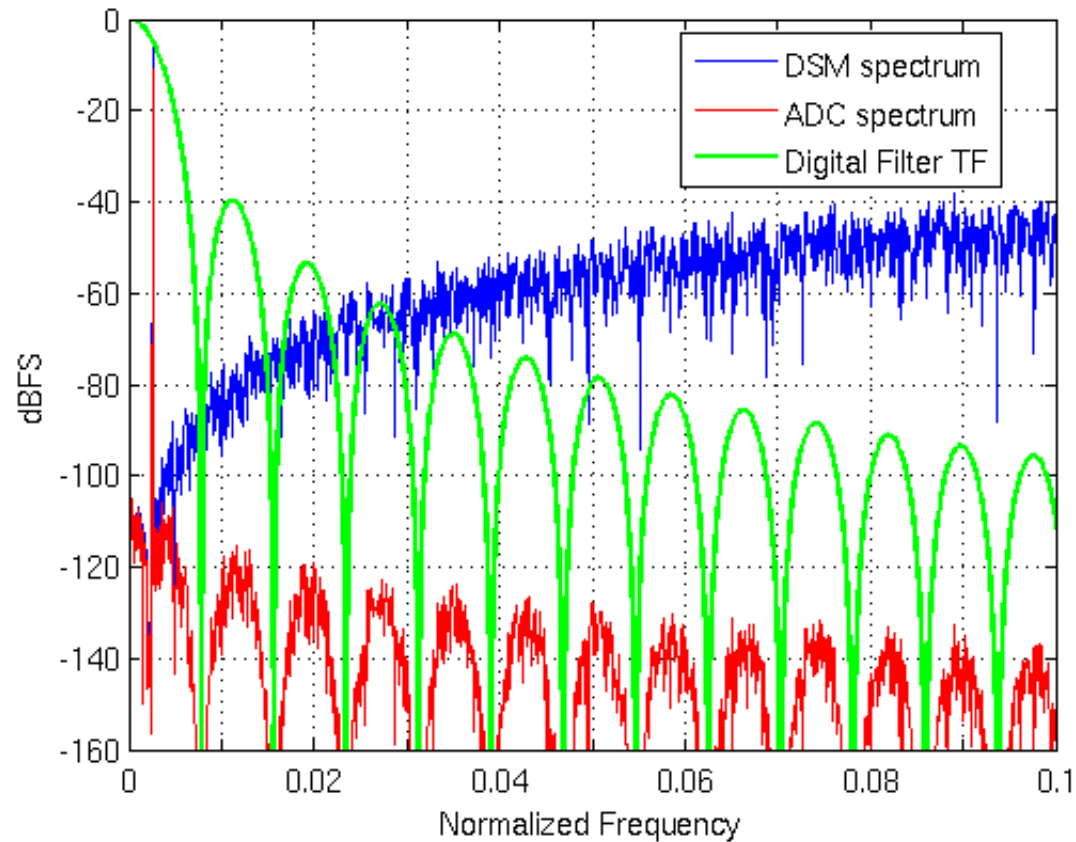


 
# Design Example – Sigma-Delta ADC filter layout






# What's Next?


Architectures that harness the unique capabilities of scaled CMOS to improve efficiency

## Examples

### Pipelined SAR

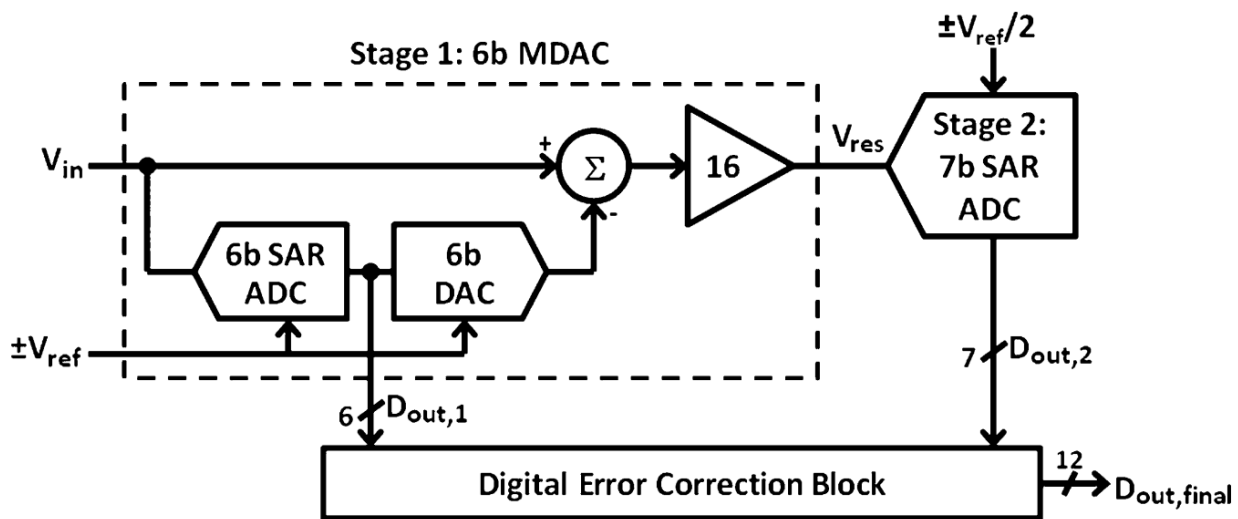

### Asynchronous SAR

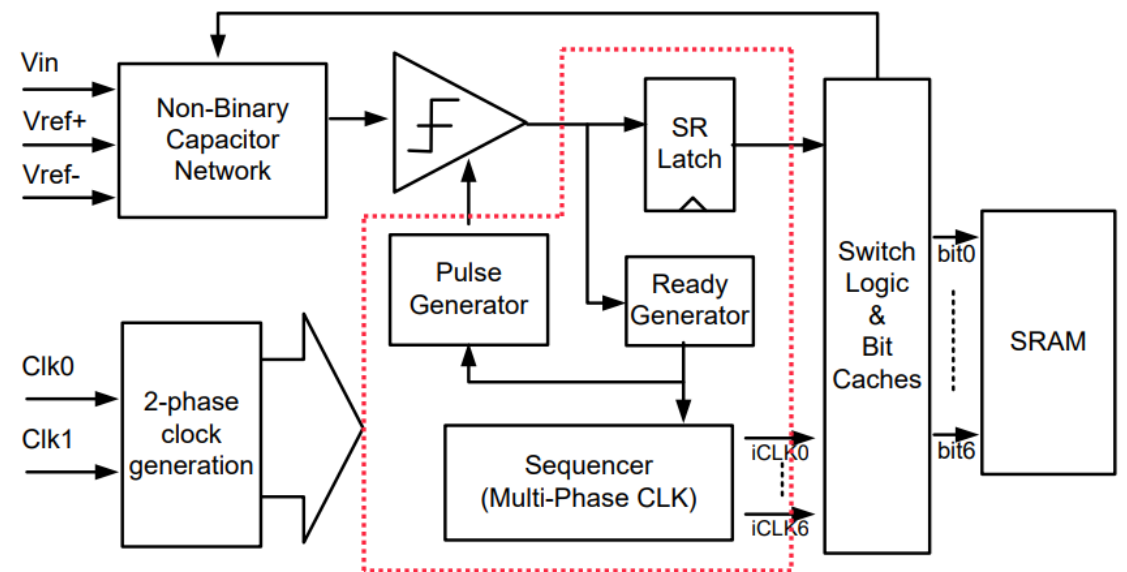



# Thank You



This work was supported in part by the U.S. Department of Energy under Contract No. DE-AC02-05CH11231